

Closed book and notes.

Show your work for credit and **put a box around each of your answers.**

1. Find the current that flows in R1 in each of the following circuits. (5 points)

