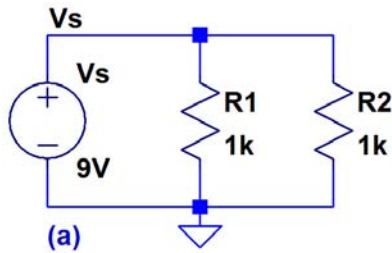



Closed book and notes.

Show your work for credit and put boxes around your answers.

1. Determine the current through R_2 . (1 point)



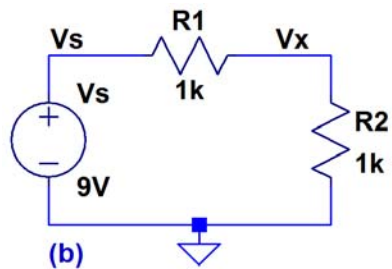2. Find V_x in the following circuit. Again, show your work for credit. (2 points)



3. Find V_x and the current through R_1 in the following circuit. (3 points)

