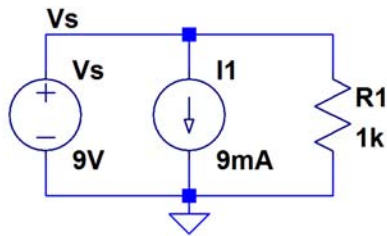


Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Determine the current through V_s . Again, show your work for credit. (2 points)



2. Find V_x in the following circuit. (5 points)

