

Quiz #6 EE 220 Spring 2017 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Determine  $V_x$  in the following circuit and the current through  $R_3$ . (5 point)

