

Quiz #8 EE 220 Spring 2017 Name: _____

Closed book and notes.

Show your work for credit!

1. Find V_{out} in the following circuit. Note that $G1$ is a voltage-dependent current source. (5 points)

