

Quiz #9 EE 220 Spring 2017 Name: _____

Closed book and notes.

Show your work for credit!

1. Find the voltages across $R1$ and $R2$. As always, show your work for credit. (5 points)

