

H.W. #2 EE 220 Summer 2014

1. Find all voltages and currents in the following circuits. Verify your answers with LTspice. Make sure your hand calculations are concise, complete, and easy to follow.

