

- Find all voltages and currents in the following circuits. Verify your answers with LTspice. Make sure your hand calculations are concise, complete, and easy to follow.

