

H.W. #4 EE 220 Summer 2014

- 1. Find all voltages and currents in the following circuits. Verify your answers with LTspice. Make sure your hand calculations are concise, complete, and easy to follow.

