

H.W. #5 EE 221 Spring 2019

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

1. Find the output voltages for each of the following circuits. Verify your answers using LTspice. (6 points)

