

Quiz #1 EE 221 Spring 2019

Name: \_\_\_\_\_

Closed book and notes.

**Show your work for credit and place a box around each of your answers.**

1. What are  $V_s$  and  $V_x$  in the following circuit? (4 points)

