

Closed book and notes.

**Show your work for credit and place a box around each of your answers.**

1. Find the AC current that flows in the following circuit and sketch, along with VS, to show the magnitudes and phase shift. (4 points)

