

H.W. #19 EE 221 Spring 2020

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

1. Find the voltages and currents in the following circuit. Verify your answers using LTspice. (5 points)

