

H.W. #5 EE 221 Spring 2020

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

1. Find the output voltages for each of the following circuits. As usual show your hand calculations (work) for credit. Verify your answers using LTspice. (6 points)

