

H.W. #11 EE 221 Spring 2021

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

1. Examine the frequency response plots seen below. If the input to each of the corresponding circuits is a 2.2V peak signal with a frequency 30 Hz hand sketch the input and output of the circuits. (2 points each)

