

H.W. #3 EE 221 Spring 2021

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

- Find the voltages V1-V12, in the following circuits anyway you would like. Verify your answers using LTspice. (8 points)

