

Closed book and notes.

Show your work for credit and place a box around each of your answers.

1. Find V_{out} in the following circuit. (5 points)

