Closed book and notes.

Show your work for credit and place a box around your answer.

1. Find the current flowing in Vin (write an equation in the time domain). (5 points)

$$V_{1} = \frac{N_{1}}{N_{2}} = \frac{1}{N_{2}} = \frac{$$