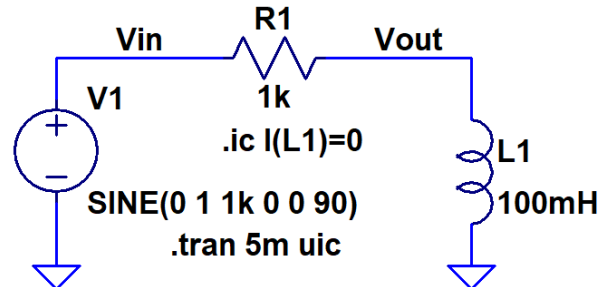


H.W. #19 EE 221 Spring 2023

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

1. Solve for both V_{out} and the current that flows in the flowing circuit using the Laplace transform. Verify your answers using LTspice. (5 points)



2. Repeat problem 1 for the following circuit. (5 points)

