

H.W. #2 EE 221 Spring 2023

Show your work for credit and put a box around each of your answers (follow the hw guidelines!)

1. Find the voltages V1-V12, in the following circuits using mesh analysis. Verify your answers using LTspice. (8 points)

