


Hand Calculations

Given parameters:

CD4007 models

NMOS: $V_{THN} = 1.6V$
 $k_{pN} = 6\mu A/V^2$
 $\lambda = 0.01$
 $W = 500\mu m$
 $L = 5\mu m$
 $\frac{W}{L} = 100$

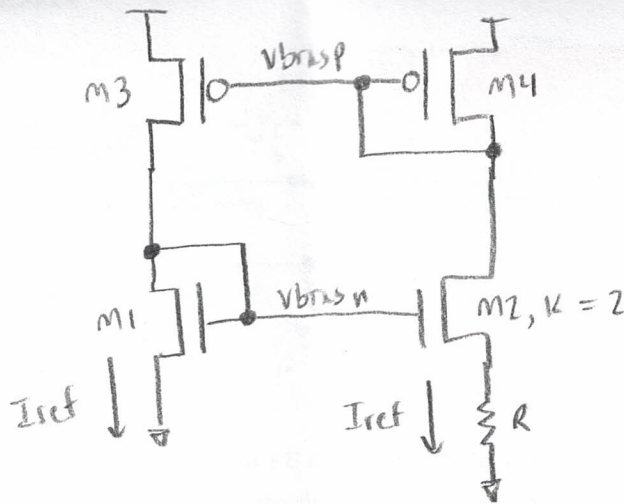PMOS: $V_{THP} = 1.5V$
 $k_{pP} = 5\mu A/V^2$
 $\lambda = 0.03$
 $W = 500\mu m$
 $L = 5\mu m$
 $\frac{W}{L} = 100$



From eq. (20.23) in CMOS book, we can write the equation for I_{ref} by:

$$① \quad I_{ref} = \frac{2}{R^2 \cdot k_{pN} \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{k}}\right)^2$$

and the equation for g_m by:

$$② \quad g_m = \sqrt{2 \cdot k_{pN} \cdot \frac{W}{L} \cdot I_{ref}}$$

from ②, $\frac{(g_m)^2}{2 \cdot k_{pN} \cdot \frac{W}{L}} = I_{ref}$

$$I_{ref} = \frac{(20\mu A/V)^2}{2 \cdot (6\mu A/V^2) \cdot 100}$$

$$I_{ref} = 0.333\mu A = 333\text{ nA}$$


Rearranging ①,

$$R = \sqrt{\frac{2}{I_{ref} \cdot k_{pN} \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{k}}\right)}$$

$$R = \sqrt{\frac{2}{333\text{ nA} \cdot 6\mu A/V^2 \cdot 100} \left(1 - \frac{1}{\sqrt{2}}\right)}$$

$$R = 29\text{ k}\Omega$$

Designed circuit:

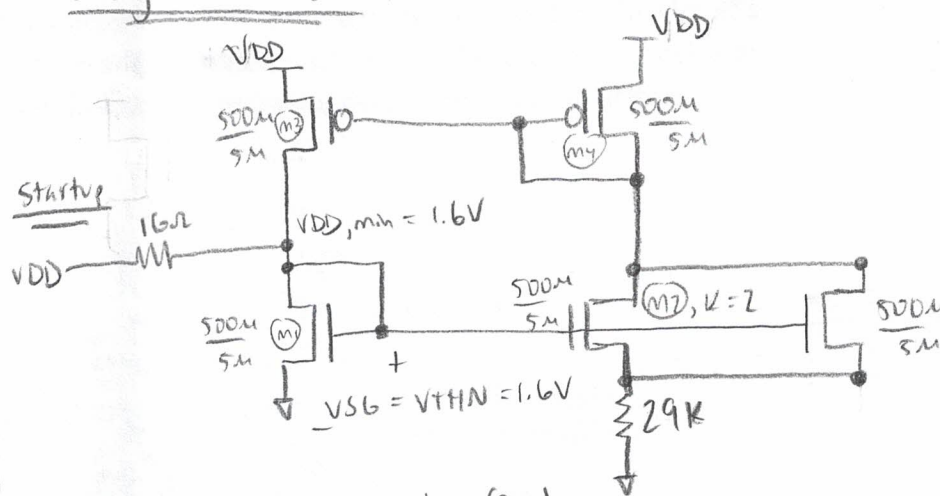

• The minimum V_{DD} can be found assuming that the $V_{GS}/V_{SB} = V_{THN}/V_{THP}$; Because device $M1$ is diode connected, and because there is a very small voltage drop across the 16Ω resistor, $V_{DDmin} = V_{THN}$. Once $V_{DD} = 1.6V = V_{THN}$, $M1$ begins sinking the desired amount of current and the BMR begins operating.