

Quiz 6, EE 420L
Spring 2020
Closed book and notes

Name: _____

1. At what frequency is the magnitude of the input equal to the magnitude of the output in the following circuit? As always, show your work for credit. (10 points).

