

Quiz 7, EE 420L

Spring 2020

Closed book and notes

Name: _____

1. Design a circuit that will convert a 10 kHz square-wave that oscillates between 2 V and 3 V into a triangle-wave that oscillates also at 10 kHz between 2 V and 3 V. (10 points).