

Quiz 9, EE 420L

Spring 2020

Closed book and notes

Name: _____

1. Show how to determine the gain (a number) of the following circuits. Note that VDD is 9V. Use the parameters from the SPICE model seen below to calculate the DC operating point. (10 points).

* W/L=1 (this doesn't mean that $W = L = 1$)

.MODEL N3306M NMOS VTO=1.824 KP=.1233

.MODEL P3306M PMOS VTO=-2.875 KP=.145

