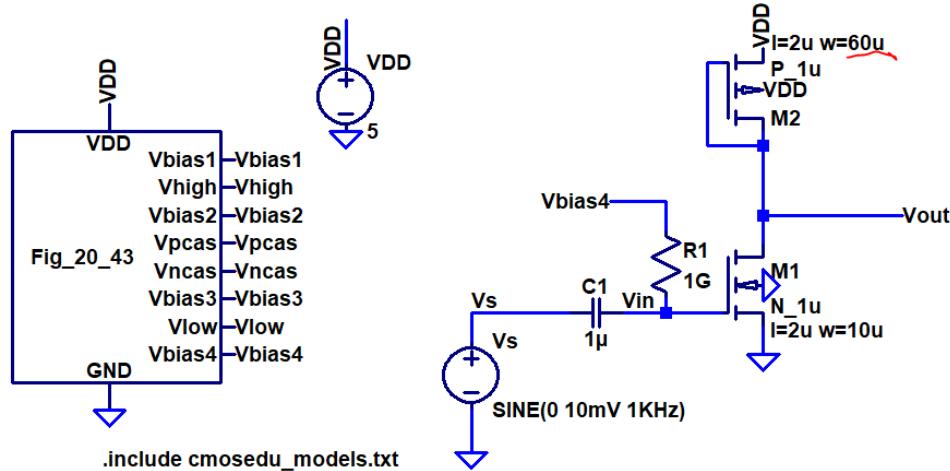



H.W. #12 EE 420/ECG 620 Spring 2020

Show your work for credit and put a box around each of your answers (follow the hw guidelines!) Unless otherwise indicated use the book's long-channel (1 um) process.

- Determine the AC current and voltages in the following circuit. Verify your hand calculations using LTspice (3 points)



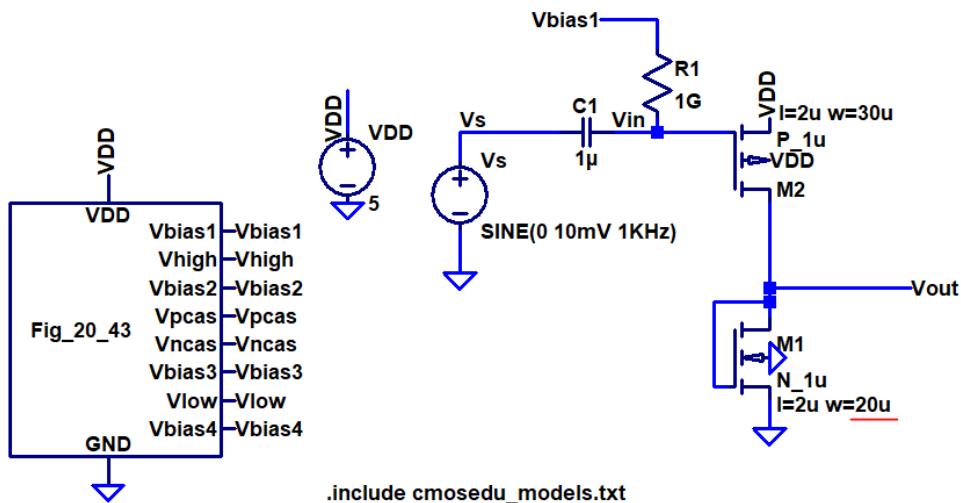- Determine the AC current and voltages in the following circuit. Verify your hand calculations using LTspice (3 points)



- Replace the gate-drain connected transistors in the above schematics with a 100k resistor and determine the output voltage, both DC and AC. Verify your answers with LTspice. (4 points)