
H.W. #9 EE 420/ECG 620 Spring 2020

Show your work for credit and put a box around each of your answers (follow the hw guidelines!) Unless otherwise indicated use the book's long-channel (1 um) process.

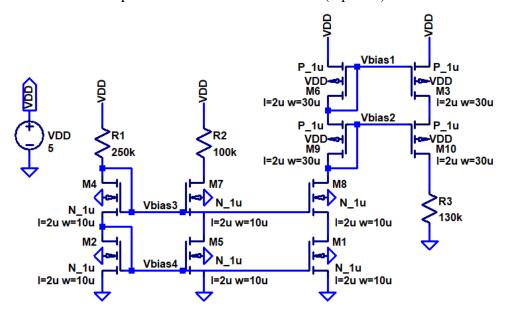1. Hand calculate the DC currents and voltages in the following circuit. Compare your hand calculated values to LTspice simulations and comment. (4 points)



- 2. If R2, in the circuit used in problem 1, is replaced with a 10 mV sinusoid at 1 kHz, estimate the resulting sinusoidal drain current in M5/M7. Verify your hand calculated answer using transient simulations. (1 point)
- 3. Repeat problem 2 if R3 is replace with a 10 mV sinusoid at 1 kHz. (1 point)