
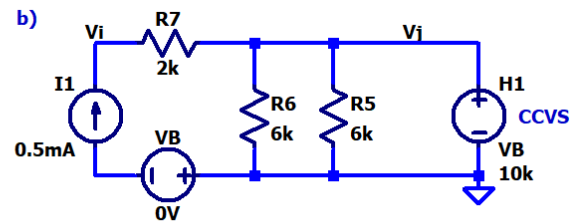


**HW10 – Due Wednesday, March 23**  
**EE220 – Circuits I**  
**Spring 2022**

To get full credit:

- Show your work.
- Put a box around each of your answers.
- Make sure to **follow all instructions**.

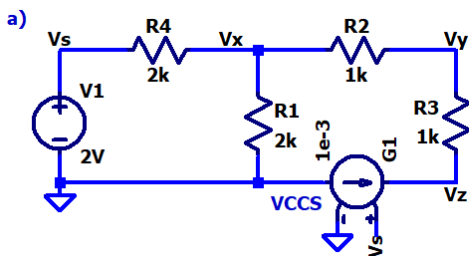1. Determine the **total instantaneous power dissipation** in each of the circuits given below. Verify your work using transient simulations in LTspice. (Note: VCCS – Voltage-Controlled Current Source, CCVS – Current-Controlled Voltage Source) (6 points)



2. A particular capacitor can store up to  $50\mu\text{C}$  of charge. What is the capacitance of this capacitor if its voltage rating is 50V? (2 points)
3. A different capacitor is rated for 16V. It has a capacitance of  $10\mu\text{F}$ . How much charge can this capacitor store? (2 points)
4. A capacitor bank is designed for the output of a 5V voltage regulator. The capacitor bank consists of a 1nF, 10nF, 100nF, and  $1\mu\text{F}$  capacitor connected in parallel. What is the equivalent capacitance of the capacitor bank (in microfarads)? Assuming the output voltage  $V_{\text{out}}$  is 5V, how much charge is stored in the capacitor bank? (2 points)

