
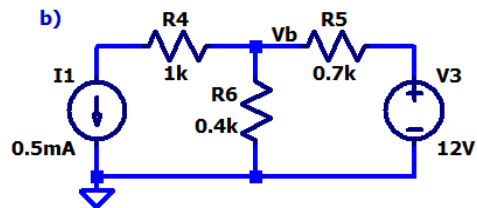


HW5 – Due Wednesday, February 9
EE220 – Circuits I
Spring 2022

To get full credit:

- Show your work.
- Put a box around each of your answers.
- Make sure to **follow all instructions**.

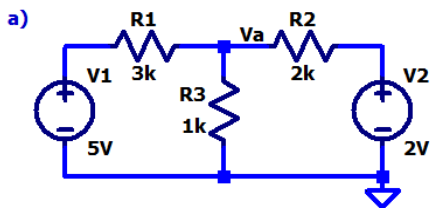1. Determine the voltages **Va** and **Vb** labeled in the circuits given below **using superposition**. Verify your work using LTspice. (4 points)



2. Determine the voltages **Vs**, **V1**, **V2**, **V3**, **V4**, and **V5** labeled in the circuit below. Verify your work using LTspice. (4 points)

