
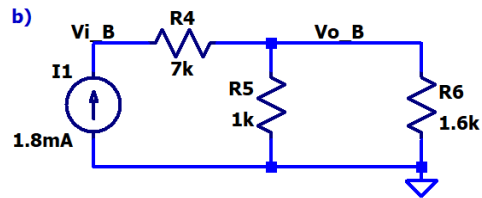


**HW9 – Due Monday, February 28**  
**EE220 – Circuits I**  
**Spring 2022**

To get full credit:

- Show your work.
- Put a box around each of your answers.
- Make sure to **follow all instructions**.

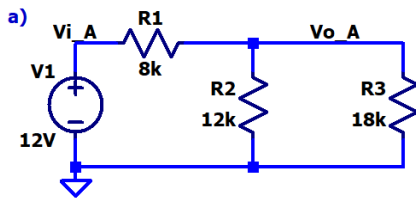1. Determine the total instantaneous power dissipation in each of the following circuits. Also, determine the percentage of the total power dissipated by each resistor. (4 points)



2. Determine **all the labeled voltages** in the circuits given below. Verify your work using LTspice. (8 points)

