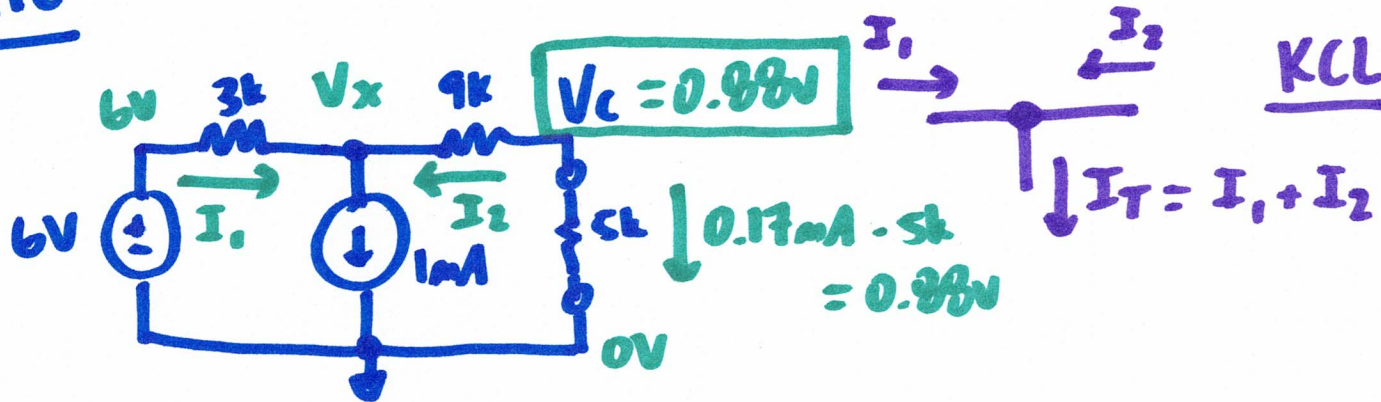



EE 220: Circuits I

HWB.1C




$$I_1 = \frac{6V - V_x}{3k} \quad I_2 = \frac{0V - V_x}{14k} = -\frac{2.47V}{14k} = -0.17mA$$


$$\frac{6V - V_x}{3k} + \frac{0 - V_x}{14k} = 1mA \rightarrow \boxed{V_x = 2.47V}$$

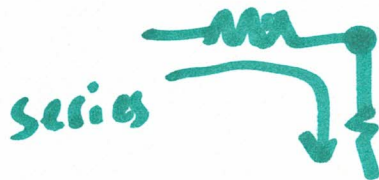

HW 8.1C (cont.)

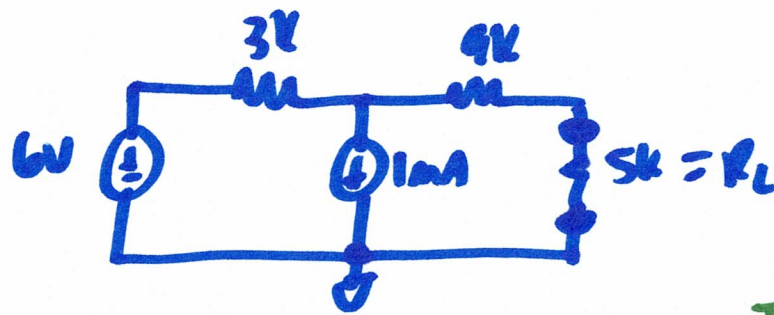
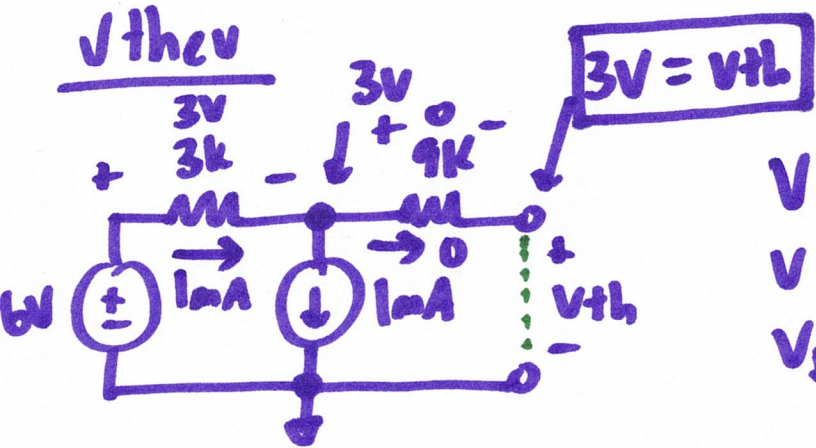
$$I_N = \frac{V_{th}}{R_N} = \frac{3V}{12k} = 0.25mA \quad \checkmark$$




$$V = I \cdot R$$

$$V = 0 \cdot R$$

$$V_{drop} = 0$$

R_{th} $\rightarrow R_N$

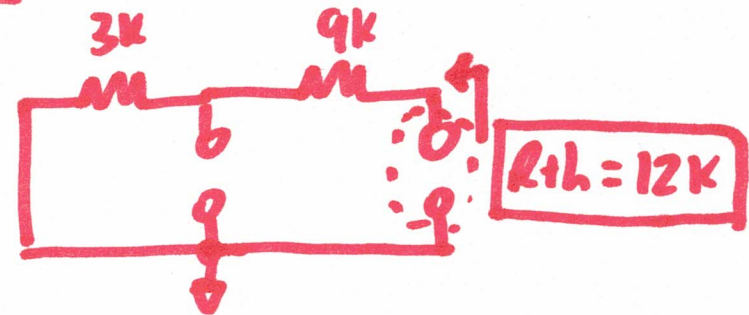

EE Toolkit:

Ohm's Law

$$V = I \cdot R$$

$$I = V/R$$


$$R = V/I$$

$$P = I \cdot V$$

$$P = V^2/R$$

$$P = I^2 \cdot R$$

Power (Instantaneous)

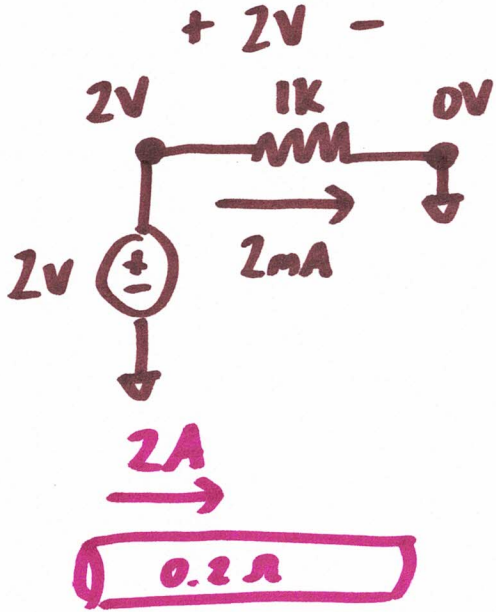


$$P = V \cdot I = 2V \cdot 2mA = 4mW$$

$$P = V \cdot I \rightarrow P = V \cdot \left(\frac{V}{R}\right) = \frac{V^2}{R}$$


↑
V/R

$$P = V \cdot I \rightarrow P = (I \cdot R) \cdot I = I^2 \cdot R$$

↑
I · R

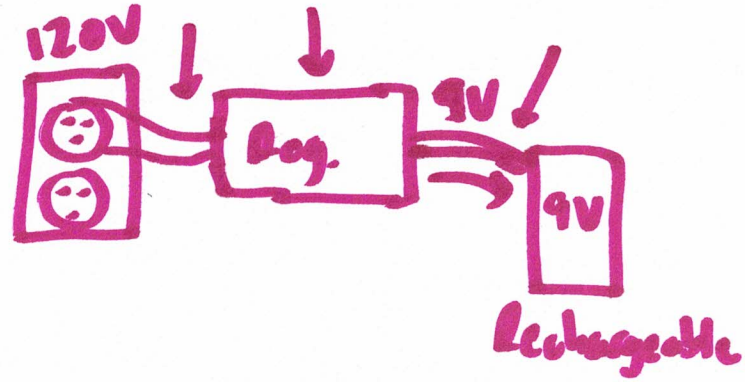

Example

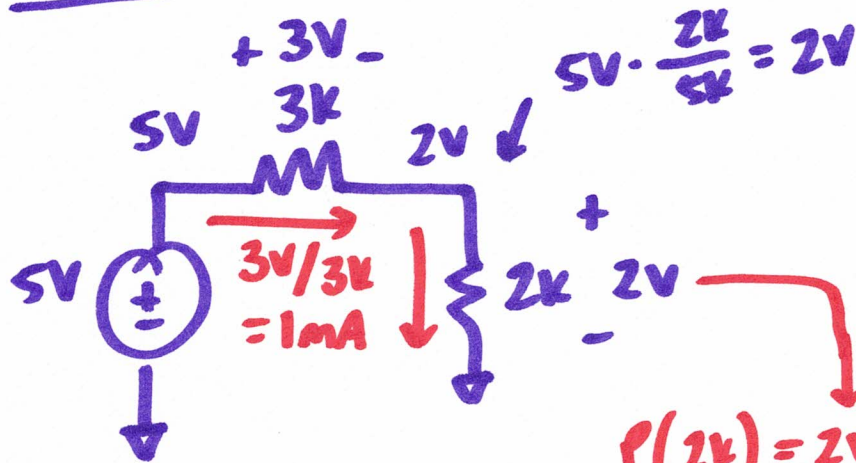

Watts

$$P(2k) = 2V \cdot 1mA = 2mW$$

$$P(3k) = 3V \cdot 1mA = 3mW$$


$$= 5mW$$

$$\frac{2mW}{5mW} \cdot 100\% = 40\%$$

$$\frac{3mW}{5mW} \cdot 100\% = 60\%$$

Dependent Sources

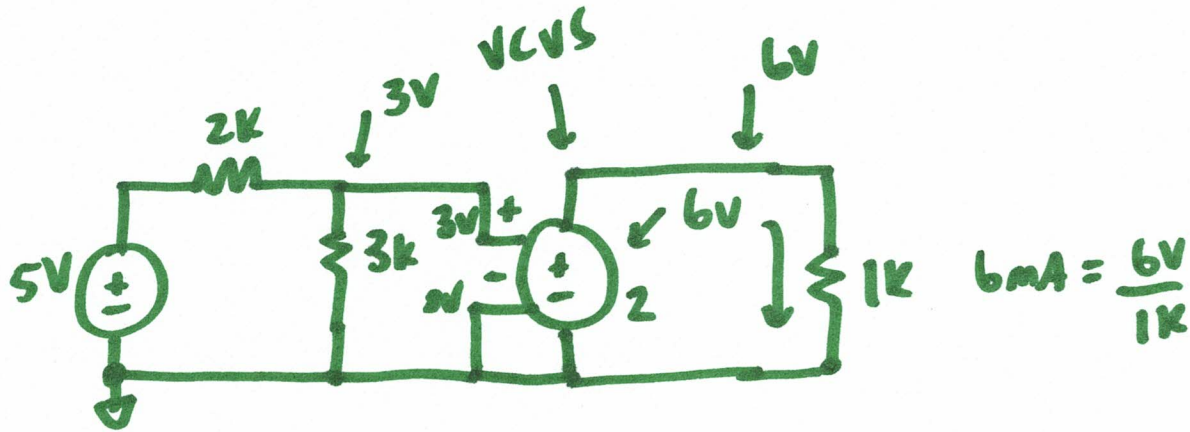4 types: Current \rightarrow Current
 Current \rightarrow Voltage
 Voltage \rightarrow Current
 Voltage \rightarrow Voltage



Operational amplifier (op-amp)

