


EE 220: Circuits 1

- 0 • Ohm's Law (Power)
- 0 • Series & parallel equivalents
- * a lot • KVL, KCL ✓
- * 6 • Nodal analysis
- * 5 • voltage, current dividers
- * lots • superposition, mesh analysis
- * lots • Thevenin & Norton
- * 5 • source transformation
- 0 • power dissipation
- * 5 • dependent sources ✓




Quiz #9

$V_f = 6V$

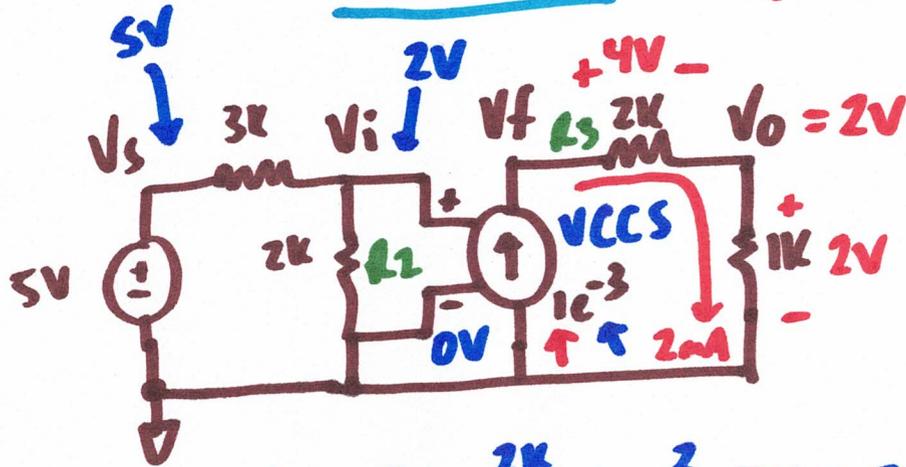


$$V_i = 5V \cdot \frac{2k}{5k} = \frac{2}{5} \cdot 5V = 2V$$
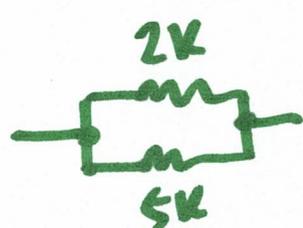
$$I(s) = 2 \cdot [1 \cdot 10^{-3}] = 2mA$$




$$2k // 5k = 1.2k$$

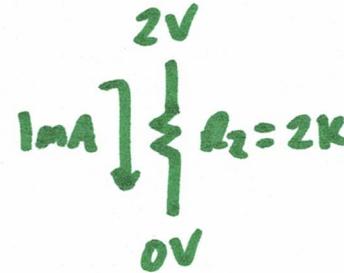

$$P(R_2) = 2V \cdot 1mA$$

$$P(R_2) = 2mW$$


X

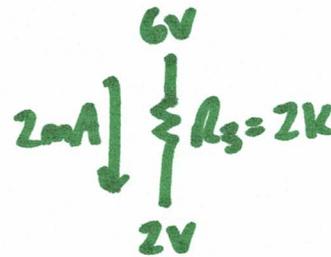

$$P(R_3) = 4V \cdot 2mA$$

$$P(R_3) = 8mW$$

HW6:1C

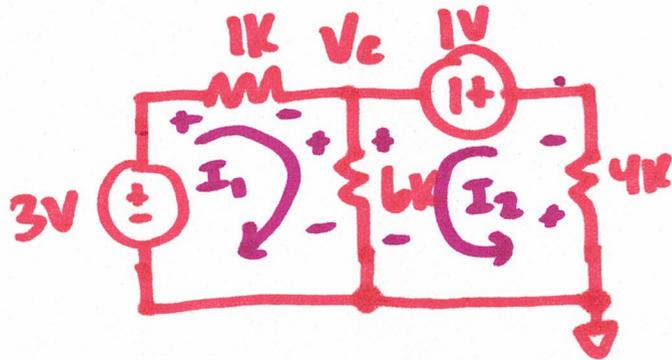

$$(1) +3V - I_1 \cdot 1k - (I_1 + I_2) \cdot 6k = 0 \rightarrow 3V - I_1 \cdot 1k - I_1 \cdot 6k - I_2 \cdot 6k = 0$$

$$(2) -1V - (I_1 + I_2) \cdot 6k - I_2 \cdot 4k = 0$$

$$3V - I_1 \cdot 7k - I_2 \cdot 6k = 0$$

$$\frac{3V - I_1 \cdot 7k}{6k} = \frac{I_2 \cdot 6k}{4k}$$

$$-1V - I_1 \cdot 6k - I_2 \cdot 6k - I_2 \cdot 4k = 0$$

$$-1V - I_1 \cdot 6k - I_2 \cdot 10k = 0$$




$$\frac{-1V - I_2 \cdot 10k}{6k} = \boxed{I_1 = -0.1667mA - 1.667I_2}$$

$$\boxed{0.5mA - 1.167I_1 = I_2}$$

$$\uparrow$$

$$0.5mA - 1.167I_1$$



BAKER ^F Q. 21, HW8.26

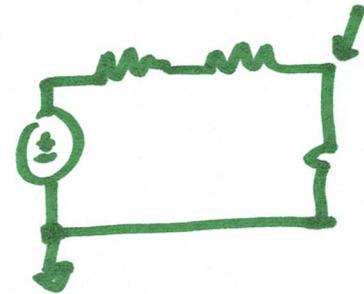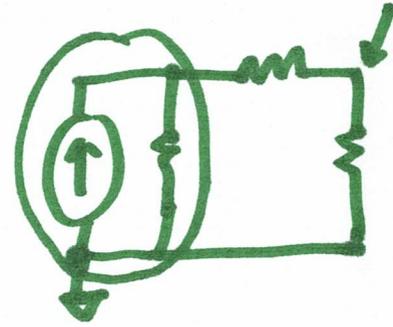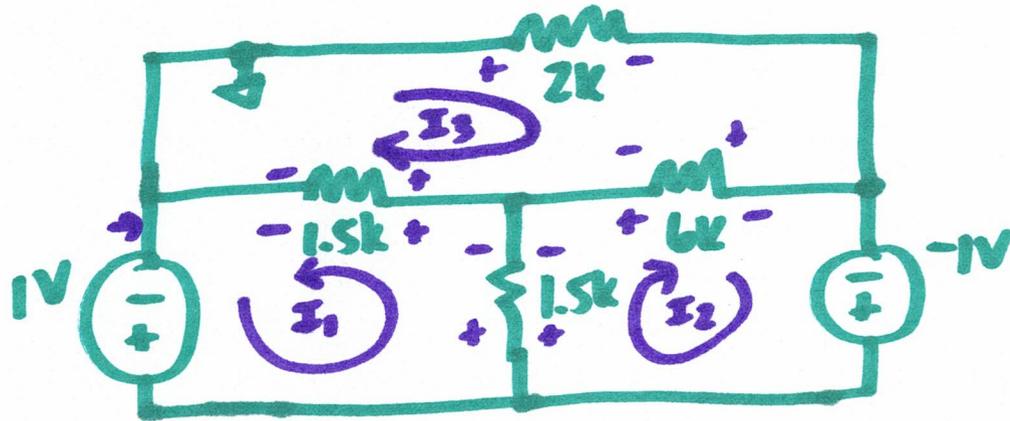



$$\textcircled{1} +1V - (I_1 + I_2) \cdot 1.5K - (I_1 + I_3) \cdot 1.5K = 0$$

$$\textcircled{2} -1V - (I_1 + I_2) \cdot 1.5K - (I_2 - I_3) \cdot 6K = 0$$

$$\textcircled{3} -I_3 \cdot 2K - (I_3 - I_2) \cdot 6K - (I_1 + I_3) \cdot 1.5K = 0$$

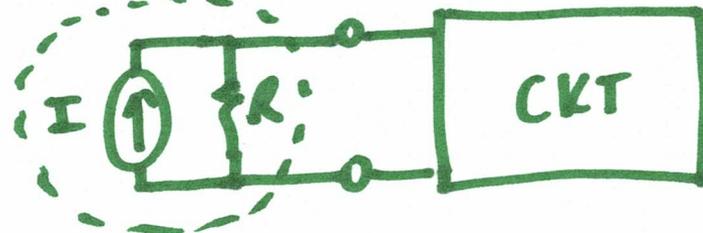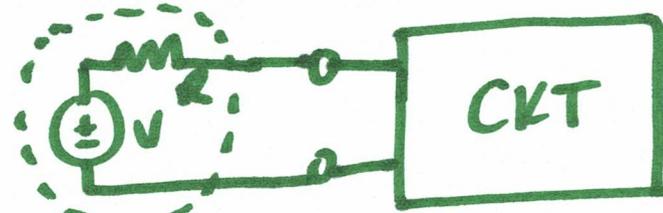

HW8: 1A

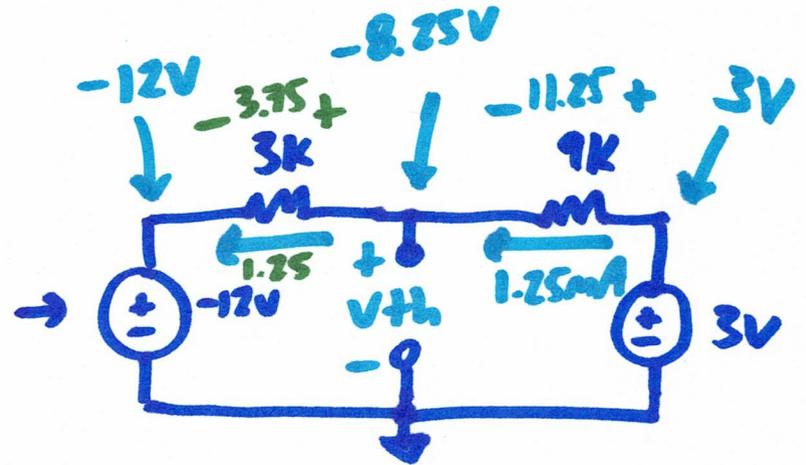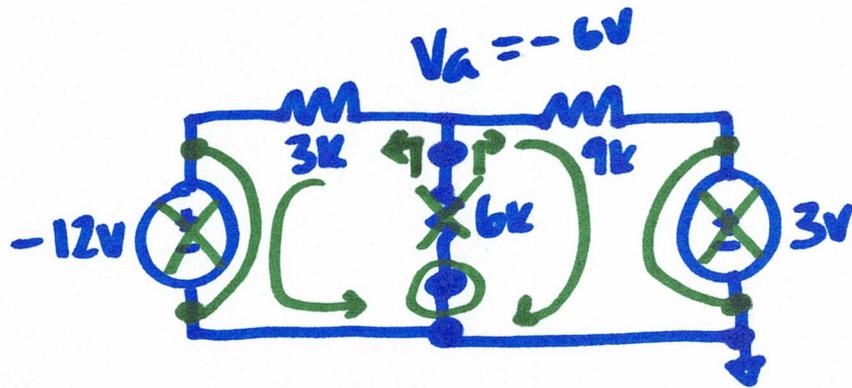


$$I = V/R$$

$$I_N = V_{th}/R_{th}$$


$$I_N = \frac{-8.25V}{2.25k}$$

$$V_{th} = -8.25V$$

$$V_{th} = -8.25V$$

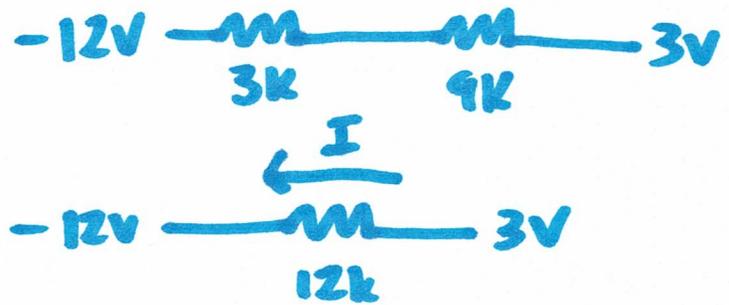
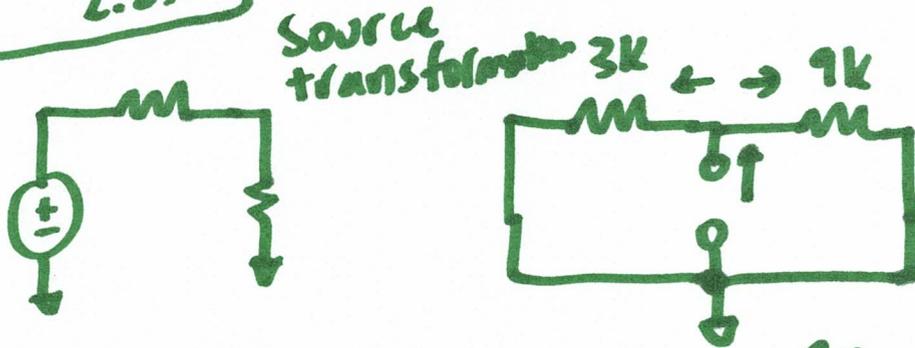
$$I = \frac{3V - (-12V)}{12k} = \frac{15V}{12k}$$




$$R_{th} = 3k // 9k = \frac{3k \cdot 9k}{3k + 9k} =$$


$$I = 1.25mA$$

$$R_{th} = 2.25k$$


BAKER EE220 F21 MT, P.2

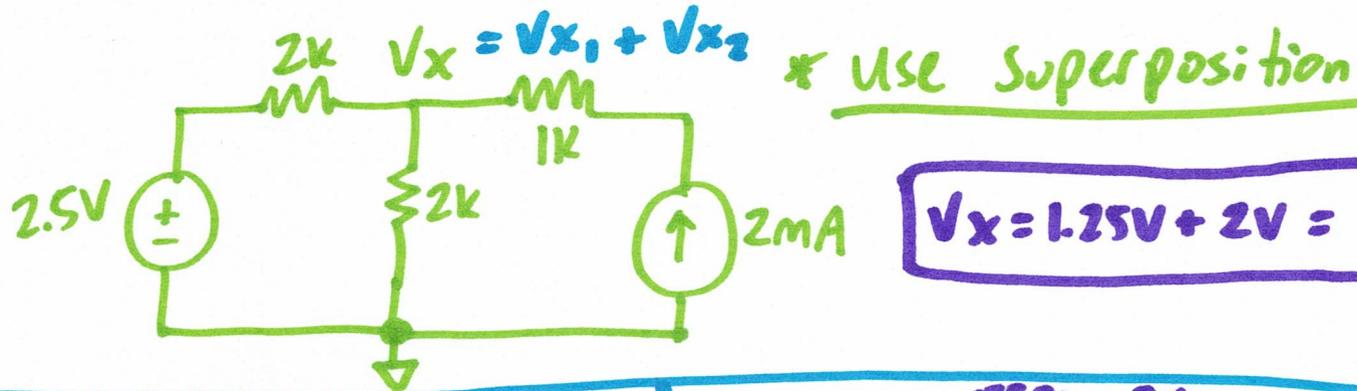

$$V_x = 1.25V + 2V = 3.25V$$

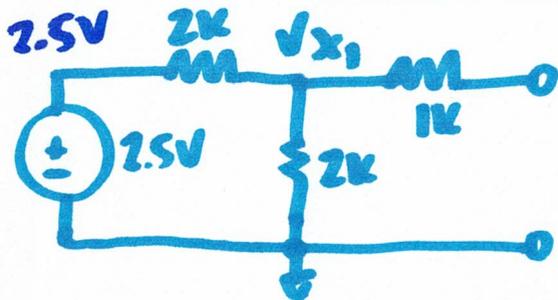

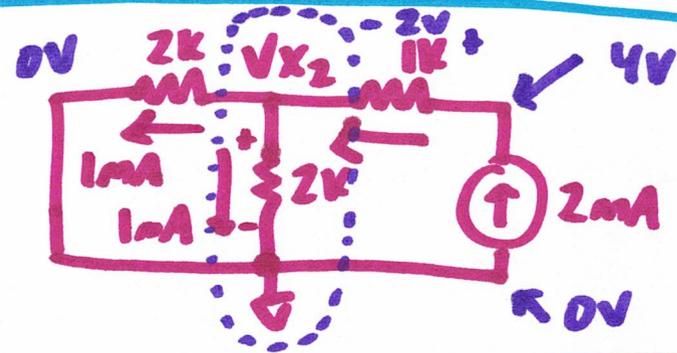
$$V_{x_1} = 2.5V \cdot \frac{2k}{4k} = 1.25V = V_{x_1}$$



$$V_{x_2} = 1mA \cdot 2k = 2V = V_{x_2}$$

BAKER MT SP.17, P.6

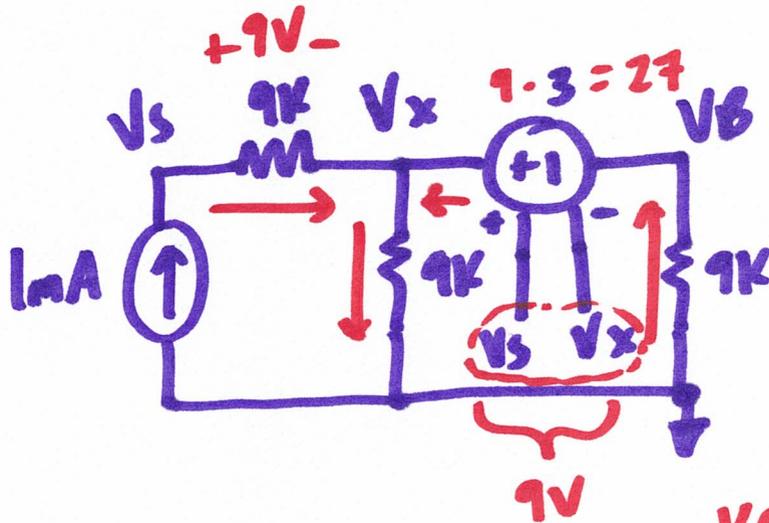

$$V_x = V_b + 27V$$

$$\text{KCL: } \frac{0 - V_b}{9k} + \frac{V_s - V_x}{9k} = \frac{V_x}{9k}$$

$$-\frac{V_b}{9k} + 1mA = \frac{V_x}{9k}$$