

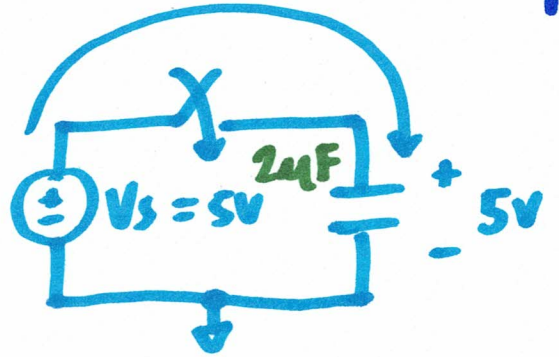


EE 220: Circuits I

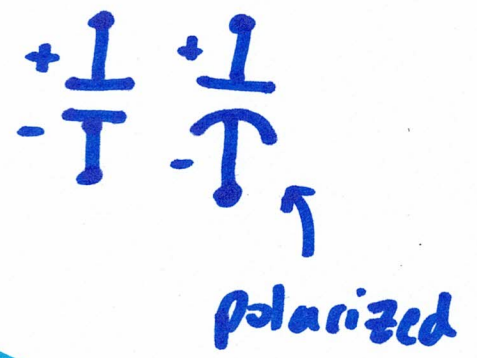

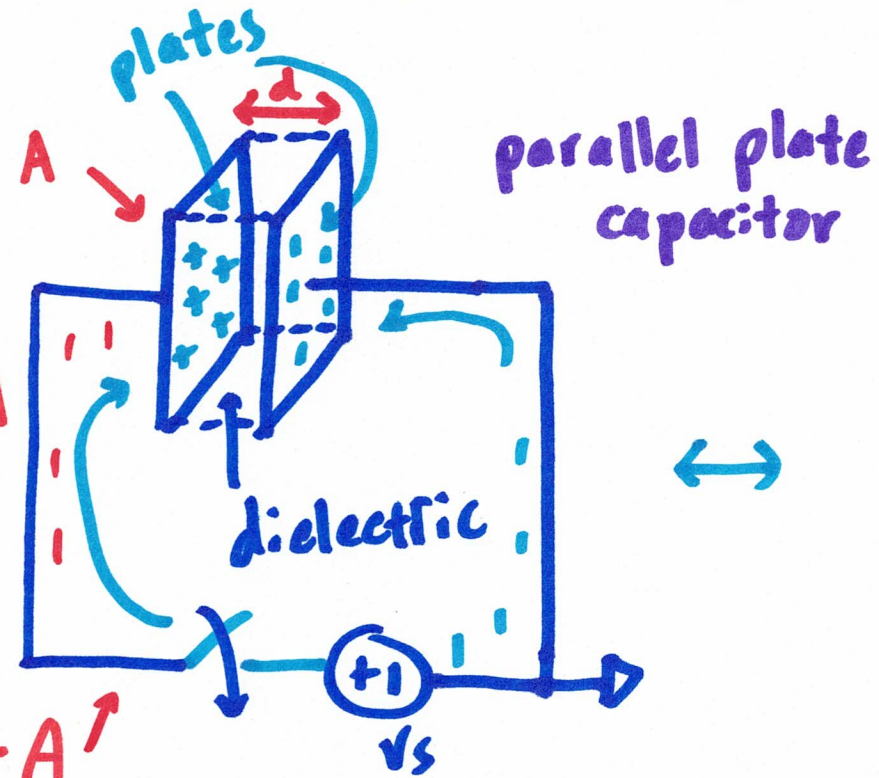capacitor: stores electrical energy in the form of an electric field.



Permittivity

$$C = \frac{\epsilon \cdot A}{d}$$

charge stored

$$C \cdot V = Q$$

voltage across cap. capacitance

$$Q = 2\mu\text{F} \cdot 5\text{V}$$

$$Q = (2 \cdot 5)\mu\text{C} = 10\mu\text{C}$$


Capacitor equivalents

Series



$$R_{eq} = R_1 + R_2$$

Series

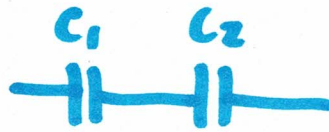


C_{eq}




$$C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

parallel

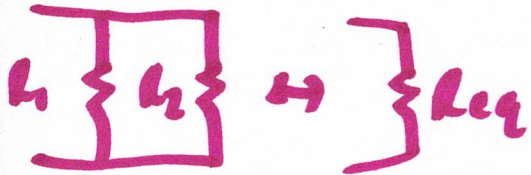



$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

parallel

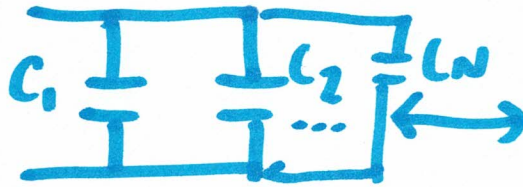

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

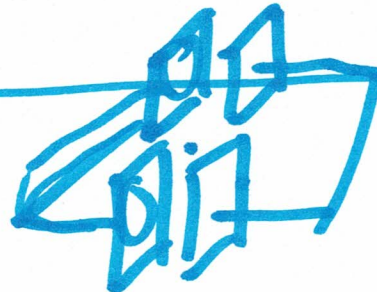

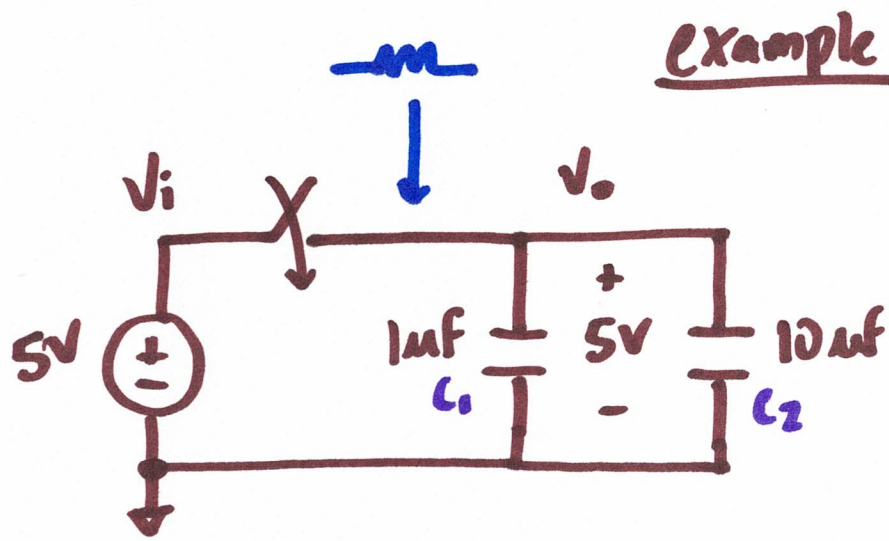


charge stored

① $C V = Q$

$$E(C_1) = \frac{1}{2} \cdot 1\mu\text{f} \cdot (5\text{V})^2 = 12.5\mu\text{J}$$
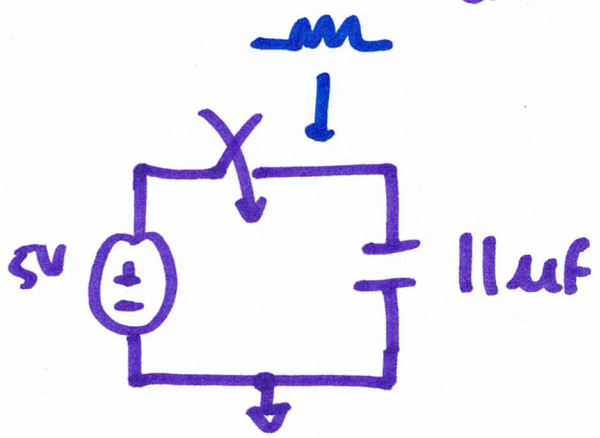
$$\left. \begin{aligned} Q(C_1) &= 1\mu\text{f} \cdot 5\text{V} = 5\mu\text{C} \\ Q(C_2) &= 10\mu\text{f} \cdot 5\text{V} = 50\mu\text{C} \end{aligned} \right\} 55\mu\text{C}$$



~~5V~~

$$5\text{V} \cdot 11\mu\text{f} = Q = 55\mu\text{C}$$

$$V \cdot C = Q$$

② $E = \frac{1}{2} \cdot C \cdot V^2$

Energy stored