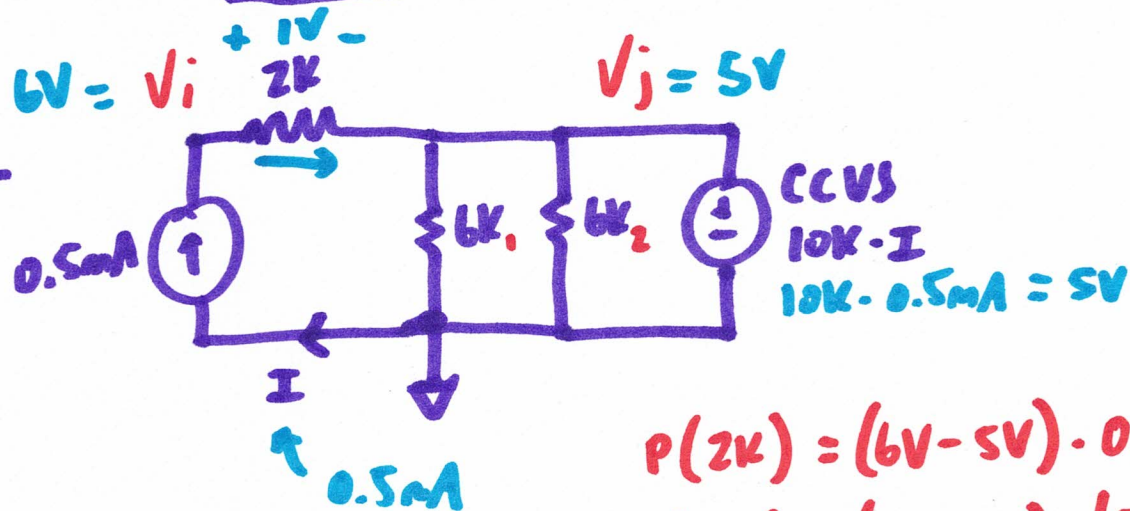


# EE 220: Circuits I

HW10.16



$$P(2k) = (6V - 5V) \cdot 0.5mA = 0.5mW$$

$$P(6k_1) = (5V - 0V) \cdot \left( \frac{5V - 0V}{6k} \right) = 4.16mW$$


$$P(6k_2) = P(6k_1) = 4.16mW$$

$$P_{TOT} = 8.82mW$$
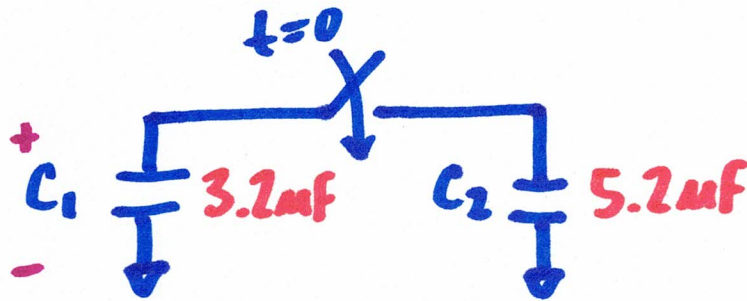
# charge sharing

initial conditions

$$\begin{aligned} V(C_1, i) &= 2V \\ V(C_2, i) &= 1V \end{aligned}$$



$$Q = C \cdot V$$

$$\begin{aligned} Q(C_1) &= 2V \cdot 3.2\mu F = 6.4\mu C \\ Q(C_2) &= 1V \cdot 5.2\mu F = 5.2\mu C \end{aligned} \left. \vphantom{\begin{aligned} Q(C_1) \\ Q(C_2) \end{aligned}} \right\} 11.6\mu C$$

\* conservation of charge

- total charge stored before sw closes = total charge stored after the switch closes.

$$(2V \cdot 3.2\mu F) + (1V \cdot 5.2\mu F) = (V_f \cdot 8.4\mu F)$$


$$\frac{11.6\mu C}{8.4\mu F} = \frac{V_f \cdot 8.4\mu F}{8.4\mu F}$$

$$V_f = 1.38V \quad \checkmark$$


$$(v) V = \frac{Q (C)}{C (F)}$$

$$E = \frac{1}{2} C \cdot V^2$$

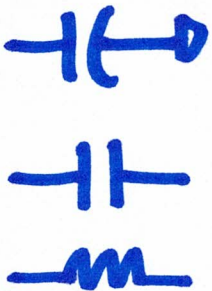Annotations:  $2.4\mu F$  (pointing to  $C$ ),  $1.38V$  (pointing to  $V$ )




# charge sharing in memory (DRAM)

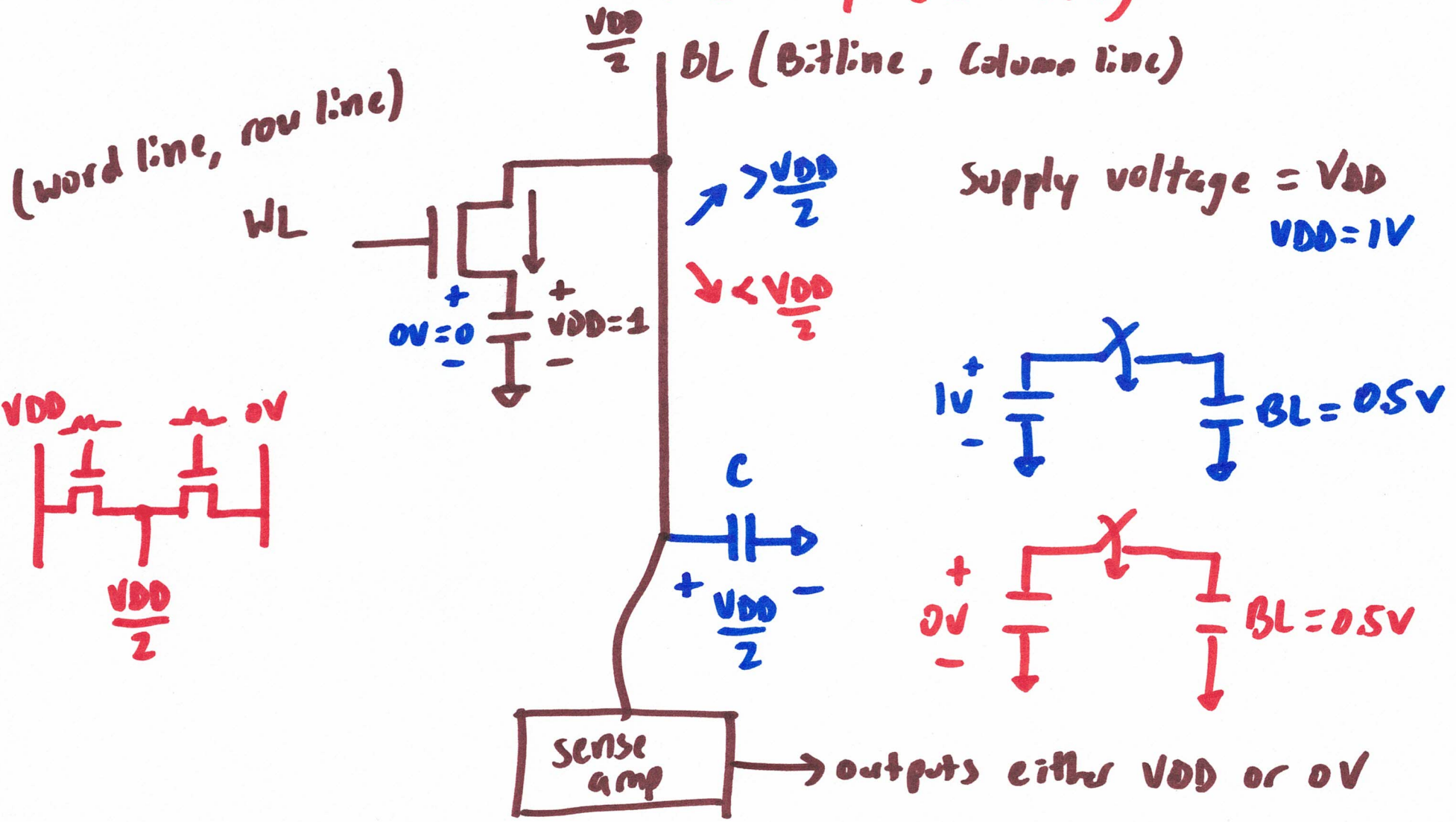


# intro to RC circuits

Charging

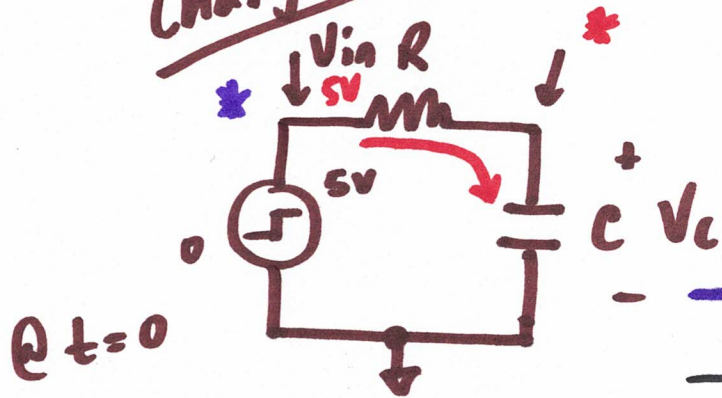

$$\tau \approx 2\text{ms}$$
$$C = 1\mu\text{F}$$
$$R = 2\text{k}\Omega$$
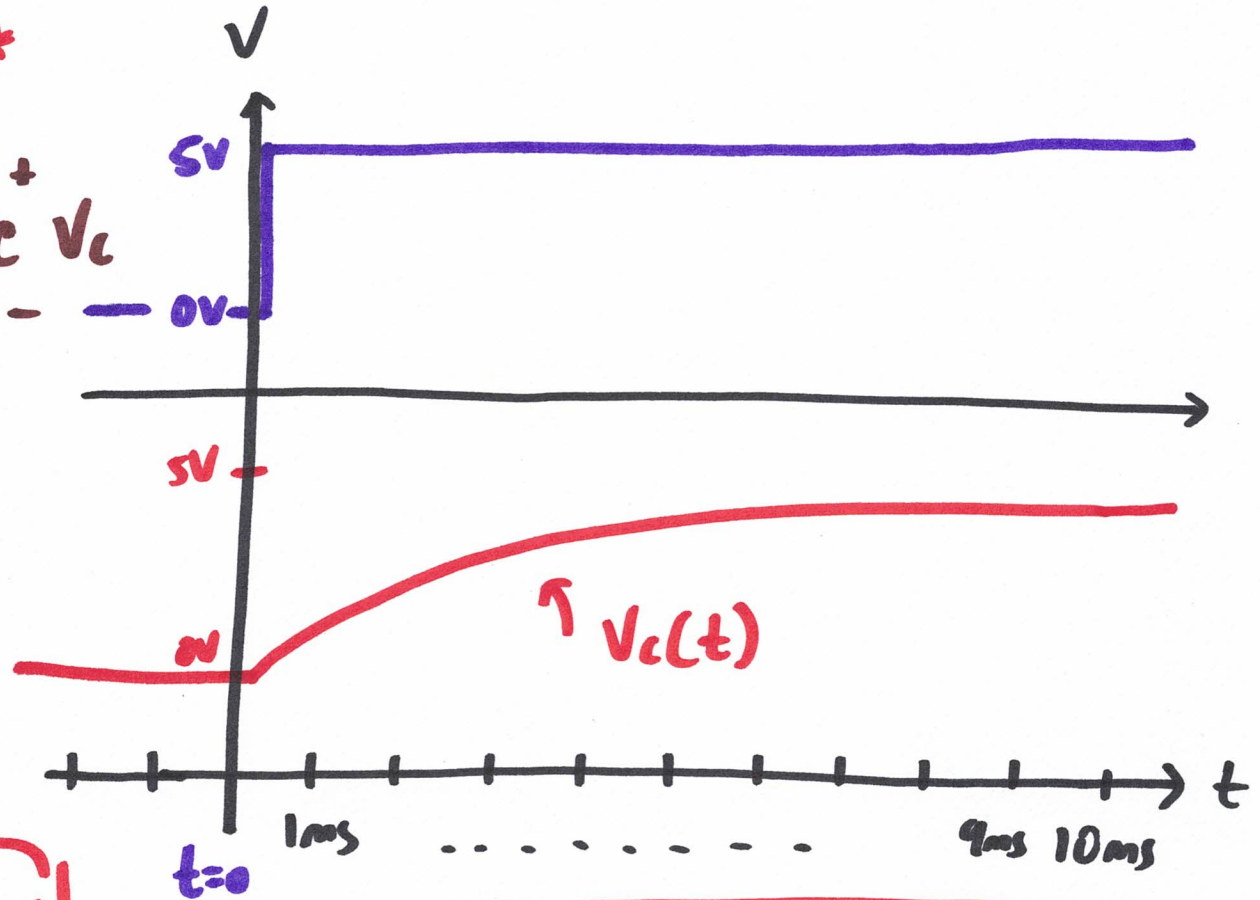
$$\tau = R \cdot C = 2\text{k} \cdot 1\mu = 2\text{ms}$$



\* takes  $\approx 5$  time constants to charge to 99%.

$$\text{time constant } \tau = R \cdot C$$