

EE 220: Circuits I

1.) $C \cdot V' = Q'$
 (capacitors)

$$C \cdot v(t) = q(t)$$


$$C \cdot \frac{dv(t)}{dt} = \frac{dq(t)}{dt}$$

$$I(t) = C \cdot \frac{dv(t)}{dt}$$

2.) $I = \frac{dQ}{dt}$



$$I = \frac{dQ}{dt}$$

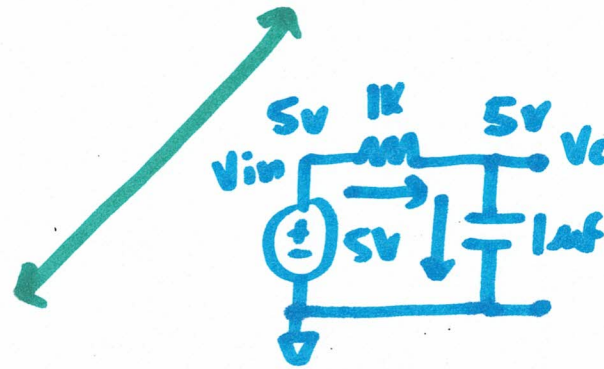


$$I = \frac{V_{in} - V_c}{1k} = 0$$

$$I = C \cdot \frac{dv}{dt} \Rightarrow I = 0$$

→ capacitors act like an open for DC

charging a cap. (RC circuits)

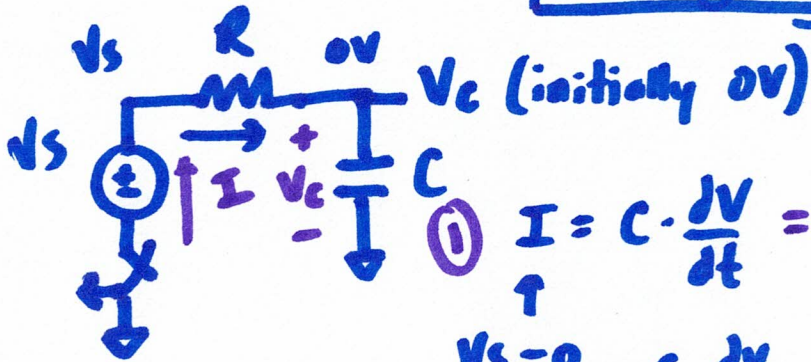

$$\textcircled{1} \quad I = C \cdot \frac{dV}{dt} = \frac{dq}{dt}$$

$$\frac{V_s - 0}{R} = C \cdot \frac{dV}{dt}$$

Non-zero
non-zero

rate of change of charge w.r.t. time

$$\textcircled{2} \quad C \cdot V = q$$

$$V_c = \frac{q}{C}$$

$$V_s - I \cdot R - V_c = 0 \quad (\text{KVL})$$

$$V_s - \frac{dq}{dt} \cdot R - \frac{q}{C} = 0$$

~~$$V_s - \frac{dq}{dt} \cdot R - \frac{q}{C} = 0$$~~

$$V_s - \frac{q}{C} = R \cdot \frac{dq}{dt}$$

$$\frac{1}{R} (V_s - \frac{q}{C}) = \frac{dq}{dt}$$

$$\frac{1}{R} (V_s - \frac{q}{C}) dt = dq$$

$$\frac{1}{R \cdot C} (V_s \cdot C - q) dt = dq$$

$$(-1) \frac{1}{R \cdot C} dt = \frac{1}{V_s \cdot C - q} dq \quad (-1)$$

$$\int_0^t -\frac{1}{RC} dt = \int_0^q \frac{1}{q - V_s \cdot C} dq$$

$$-\frac{t}{RC} = \ln |q - V_s \cdot C| \Big|_0^q \quad \longrightarrow$$

$$\frac{-t}{RC} = \ln \left| \frac{q - Vs \cdot C}{0 - Vs \cdot C} \right|$$

$$\frac{-t}{RC} = \ln |q - Vs \cdot C| - \ln |0 - Vs \cdot C|$$

$$e^{\frac{-t}{RC}} = \frac{q - Vs \cdot C}{-Vs \cdot C}$$

$$-Vs \cdot C e^{-t/RC} = \frac{q - Vs \cdot C}{-Vs \cdot C} (-Vs \cdot C)$$

$$-(Vs \cdot C) e^{-t/RC} = q - Vs \cdot C$$

$$+Vs \cdot C \quad \quad \quad +Vs \cdot C$$

$$\frac{(Vs \cdot C) - (Vs \cdot C) e^{-t/RC}}{C} = \frac{q}{C} \quad \swarrow V_c$$


charging a cap.

$$V_c(t) = Vs (1 - e^{-t/RC})$$

$$\ln|a| - \ln|b| = \ln\left|\frac{a}{b}\right|$$

$$q \cdot V = \frac{q}{C}$$


$$V = \frac{q}{C}$$

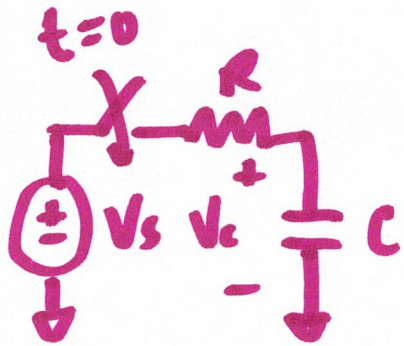

equation: charging a capacitor

$$V_c(t) = V_{in}(1 - e^{-t/\tau})$$

$$\tau = RC$$

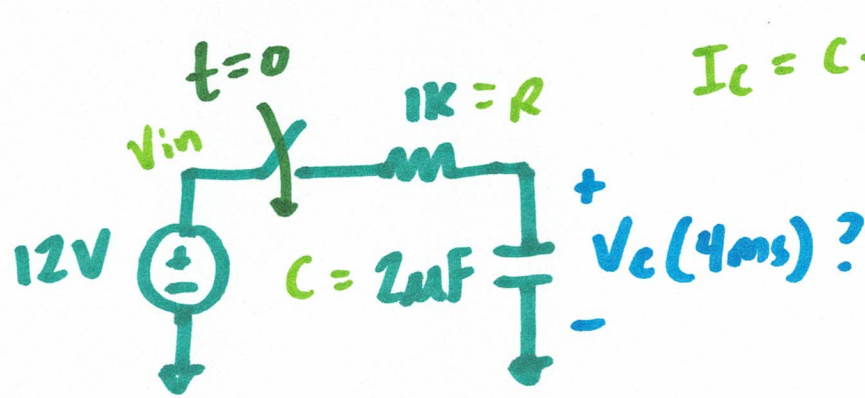

$$I_c = C \cdot \frac{dV}{dt} \Rightarrow \frac{dV}{dt} = \frac{I_c}{C}$$

~~V_{in}~~ V_c

$$\tau = 1k\Omega \cdot 2\mu F$$


$$\tau = 2ms$$

$$V_c(4ms) = 12V \cdot (1 - e^{-t/2ms})$$

$$V_c(4ms) = 12V \cdot (1 - e^{-(4ms/2ms)})$$

$$V_c(4ms) = 10.376V$$

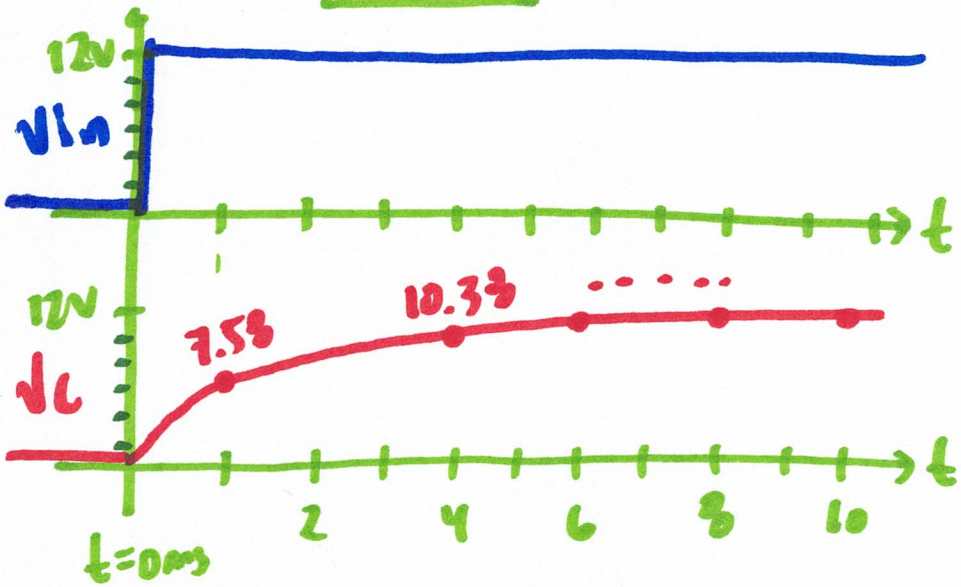
$$\frac{10.376V}{12V} = 0.865 \times 100\% = 86.5\%$$



$V_c(2ms) = 7.58V$
$V_c(4ms) = 10.38V$
$V_c(6ms) = 11.40V$
$V_c(8ms) = 11.78V$
$V_c(10ms) = 11.92V$

discharging a capacitor: $V_c(t) = V_{ci} \cdot e^{-t/\tau}$

$$\tau = RC$$

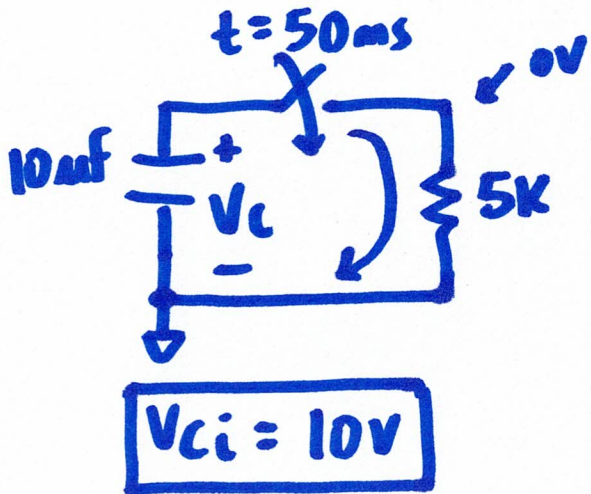

* what is the cap. voltage at $t = 150\text{ms}$?

$$V_c(t) = V_{ci} \cdot e^{-t/\tau}, \quad \tau = 5\text{K} \cdot 10\mu\text{f} = 50\text{ms}$$

$$V_c(t) = V_{ci} \cdot e^{-t/50\text{ms}}$$

$$V_c(t) = V_{ci} \cdot e^{-(t - 50\text{ms})/50\text{ms}}$$

$$V_c(150\text{ms}) = 10\text{V} \cdot e^{-(150\text{ms} - 50\text{ms})/50\text{ms}}$$

$$V_c(150\text{ms}) = 1.353\text{V}$$