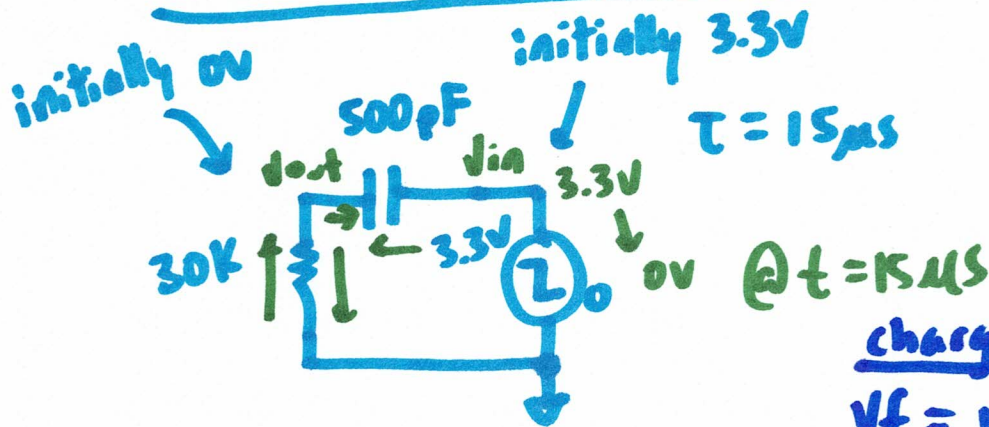


EE 220: Circuits I




"FIFE" equation

$$V_c(t) = V_f + (V_i - V_f)e^{-t/\tau}$$

charging:


$$V_f = V_f, \quad V_i = 0$$

$$\tau = R \cdot C$$

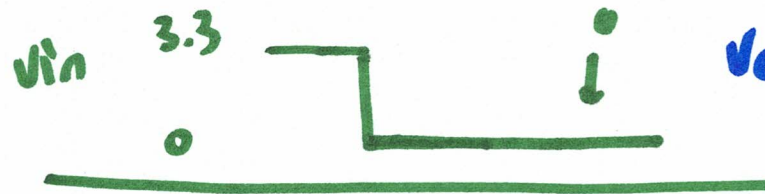

$$V_c(t) = V_f - V_f e^{-t/\tau}$$

$$= V_f(1 - e^{-t/\tau})$$


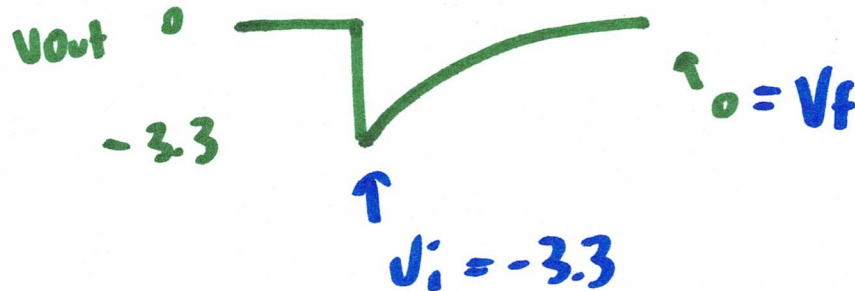


discharging:

$$V_f = 0, \quad V_i = V_i$$





$$V_c = V_i \cdot e^{-t/\tau}$$

using KVL to solve RC circuits

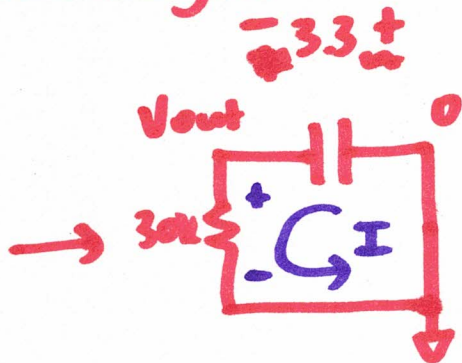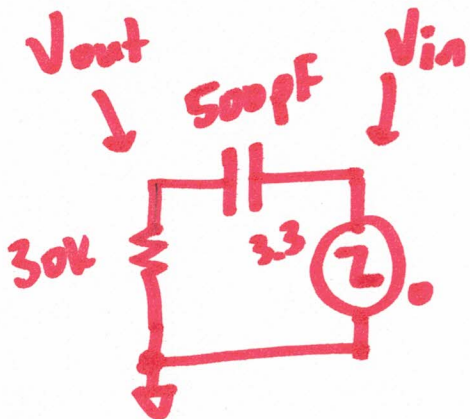



$$-3.3V - I \cdot 30k = 0$$
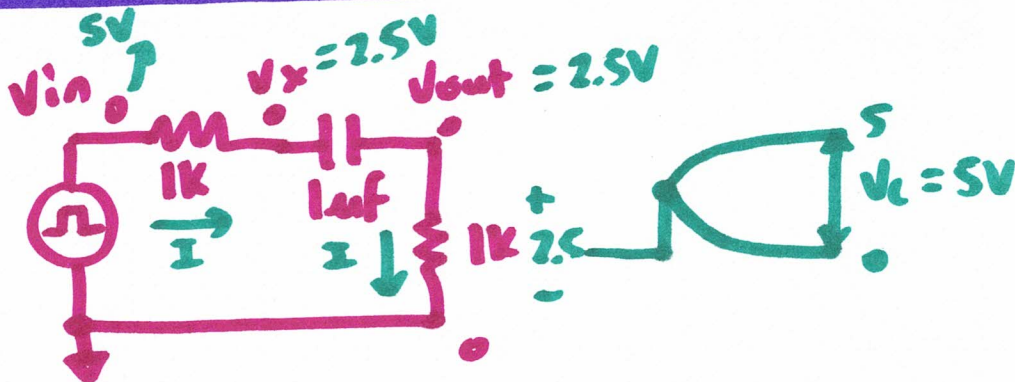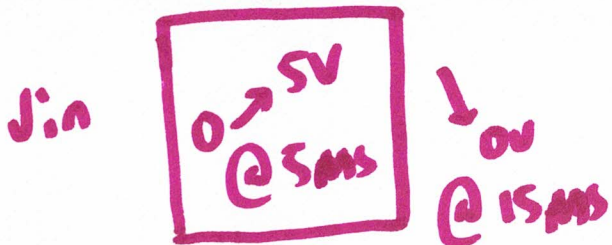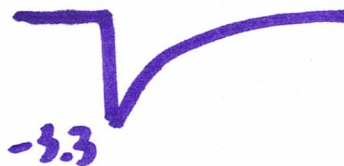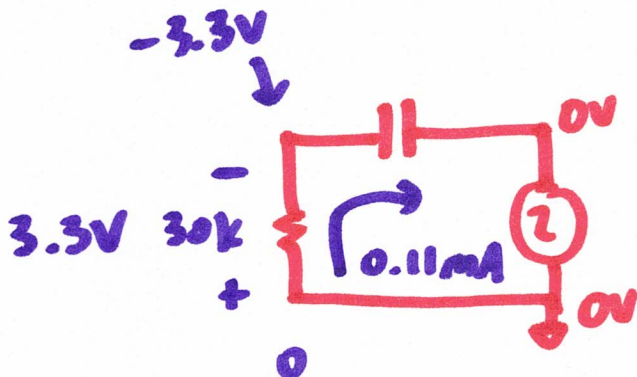
$$-\frac{3.3V}{30k} = \frac{I \cdot 30k}{30k} \rightarrow I = -0.11mA$$



$$5V - I \cdot 1k + 0 - I \cdot 1k = 0$$

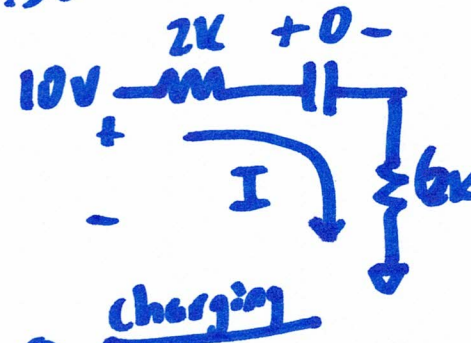
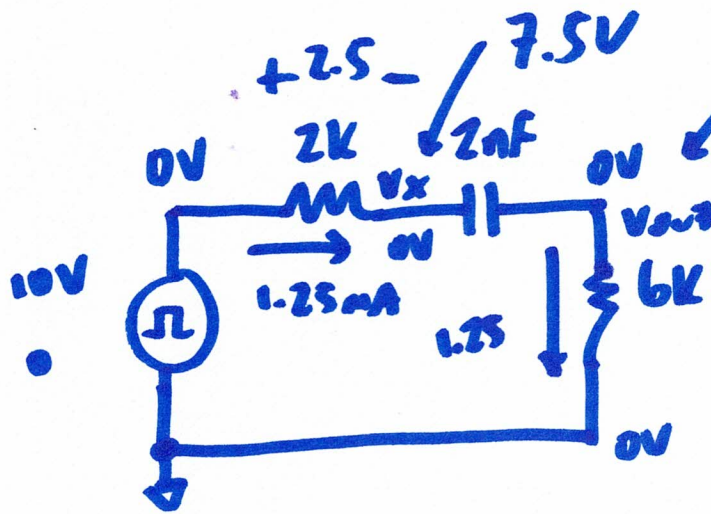
$$\frac{5V}{2k} = \frac{I \cdot 2k}{2k} \rightarrow I = 2.5mA$$



① charging
 KVL: $10V - I \cdot 2k - I \cdot 6k = 0$

$$\frac{10V}{8k} = \frac{I \cdot 8k}{8k}$$

$$I = 1.25mA$$

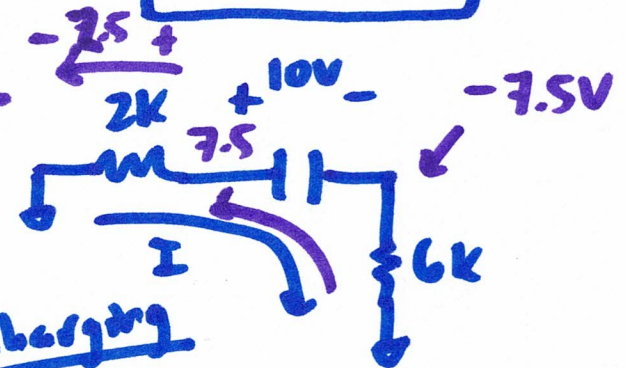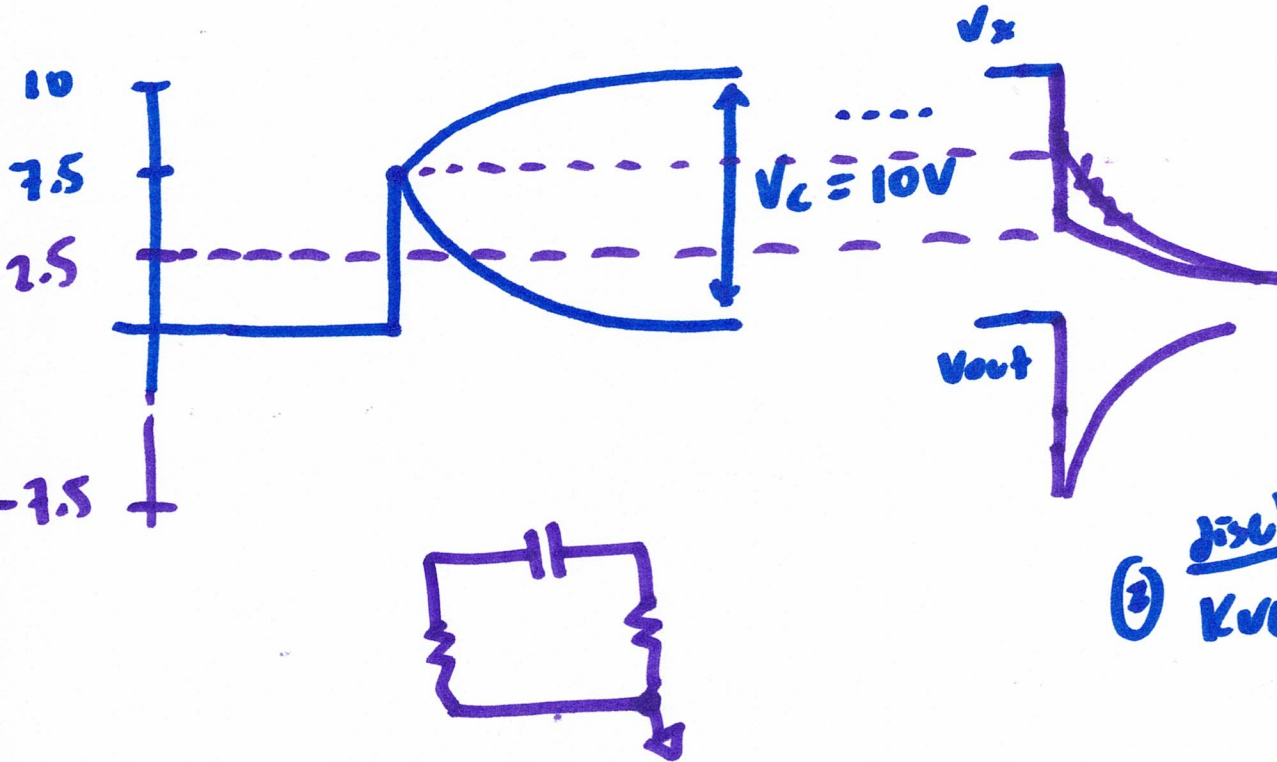

② discharging
 KVL: $-I \cdot 2k - 10V - I \cdot 6k = 0$


$$-10V = +I \cdot 8k$$

$$I = -1.25mA$$

$$-1.25 \cdot 2k$$





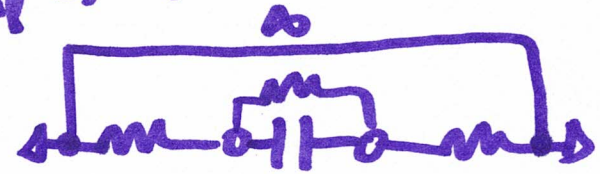DC: $C \rightarrow \infty \rightarrow \text{open}$



~~$V_L = L \cdot \frac{di}{dt}$~~


~~$V_C = C \cdot \frac{dv}{dt}$~~

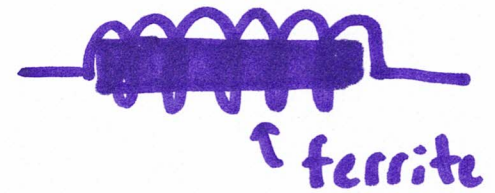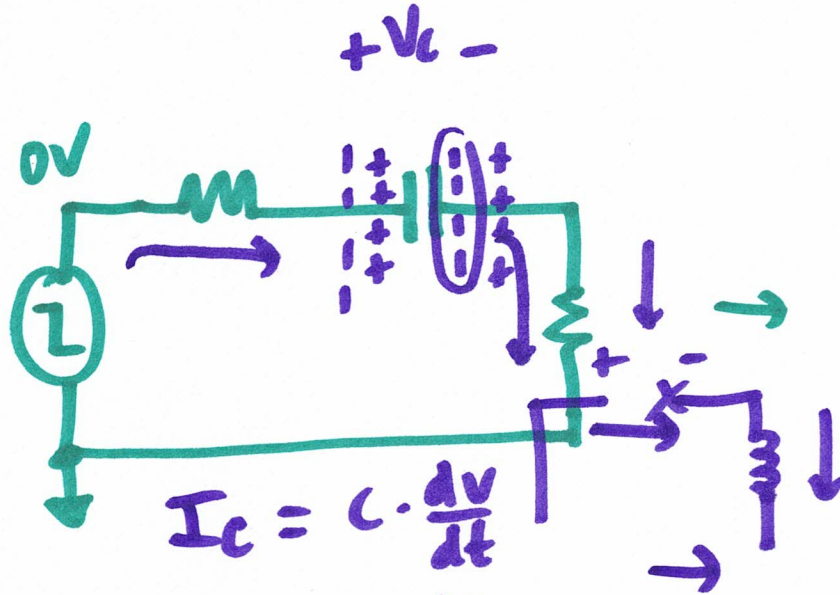

Resistors

$$V_L = L \cdot \frac{di}{dt}$$

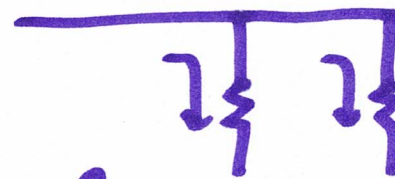Impedance Impedance $\rightarrow Z_R = R$



Inductor $2\pi \cdot f$
 \downarrow
 $Z_L = j\omega L$



Impedance $\rightarrow Z_C = \frac{1}{j \cdot 2\pi \cdot f \cdot C} \rightarrow \infty$
 \uparrow
 $i = \sqrt{-1}$

$$E_C = \frac{1}{2} \cdot C \cdot V^2$$

$$E_L = \frac{1}{2} \cdot L \cdot I^2$$