
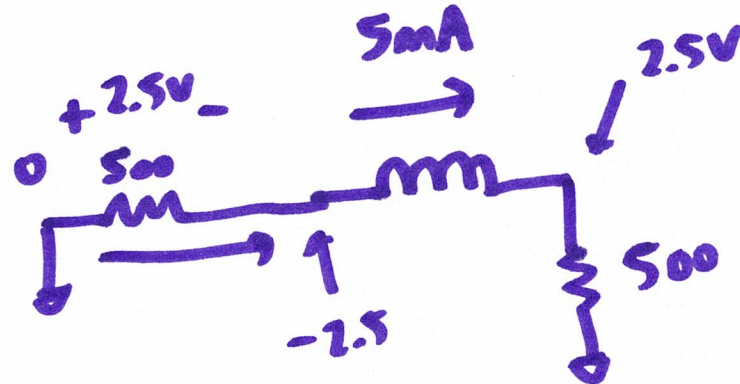
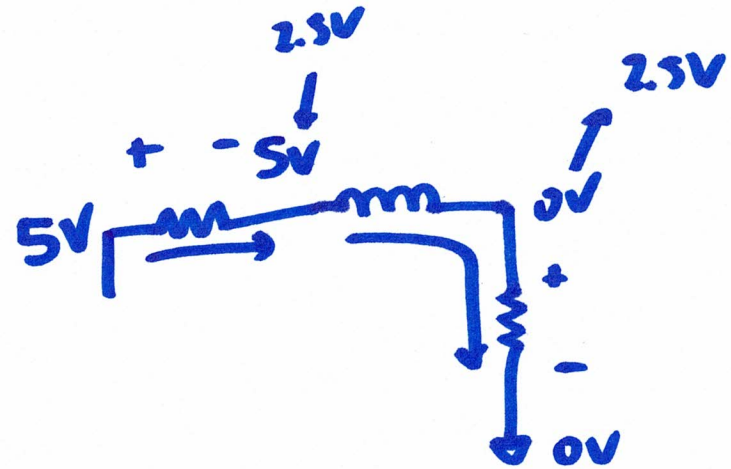
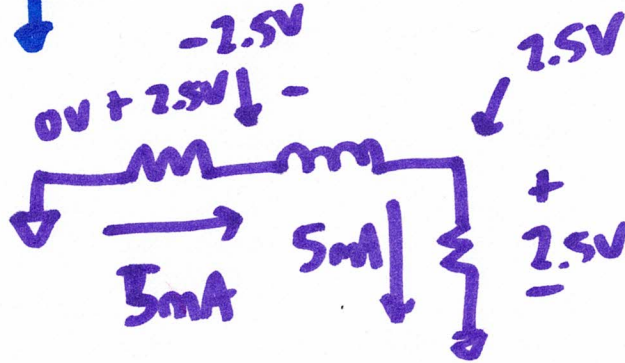
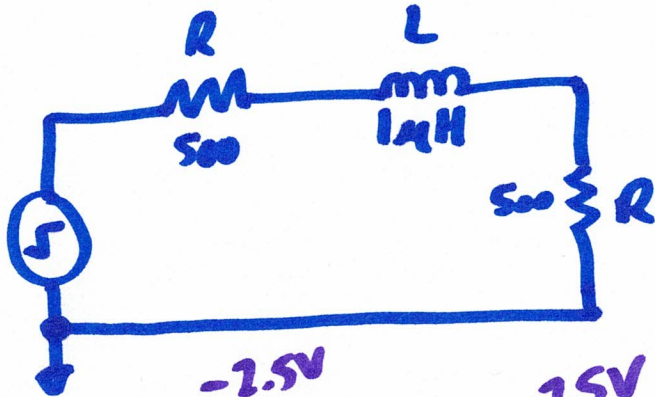


EE 220: Circuits I

$$V_L = L \frac{di_L}{dt}$$

$$\tau = \frac{L}{R} = 1 \text{ms}$$

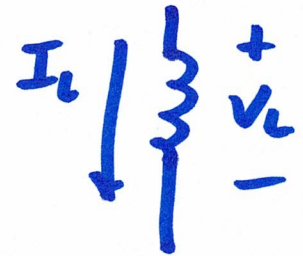

camera
sucked, only
1 page :-