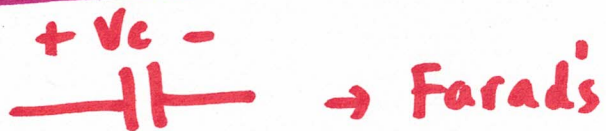


EE 220: Circuits I


Capacitors (AC short)
(DC open)




- * store energy as electric field
- * resist changes in their voltage

$$* I_c = C \cdot \frac{dV_c}{dt}$$

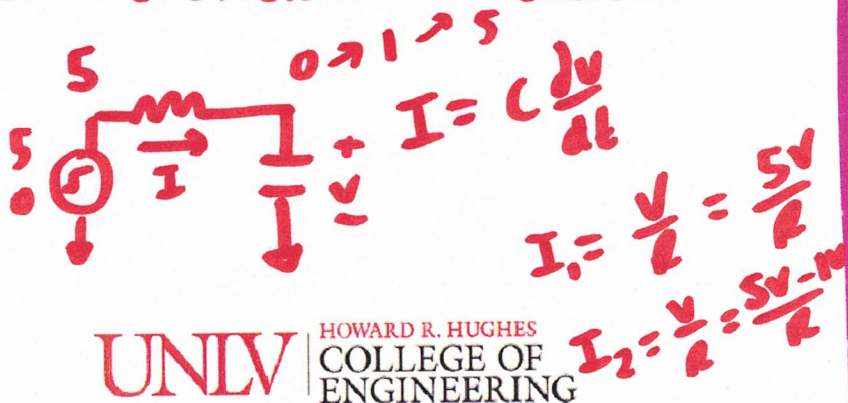* made of two conductive plates with a dielectric in between



inductors (AC open)
(DC short)

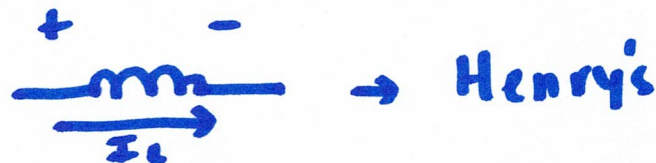


- * store energy as magnetic field
- * resist changes in their current

$$* V_L = L \cdot \frac{dI_L}{dt}$$

* made of a wire wrapped around a magnetic material

Quiz 14

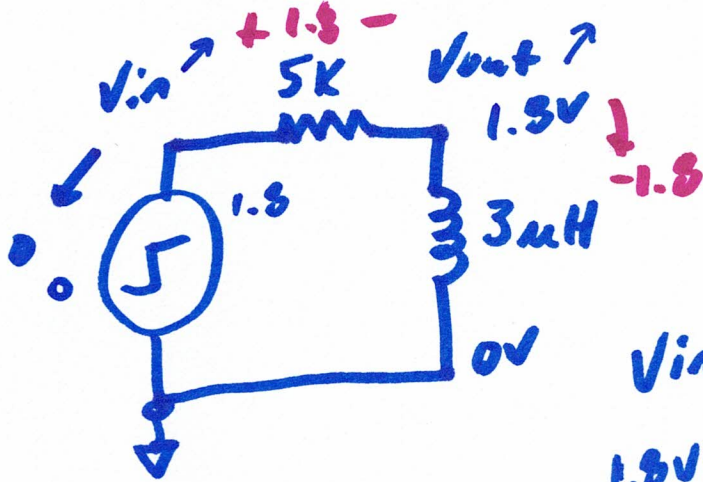



$$\tau = 0.6 \text{ ns} = \frac{L}{R} = \frac{3 \mu\text{H}}{5 \text{ k}\Omega}$$

$$V_L = L \frac{dI}{dt}$$

$$I = \frac{1.8 - 0}{5 \text{ k}} = 360 \mu\text{A}$$

$$I(t) = I_f + (I_i - I_f) e^{-t/\tau}$$
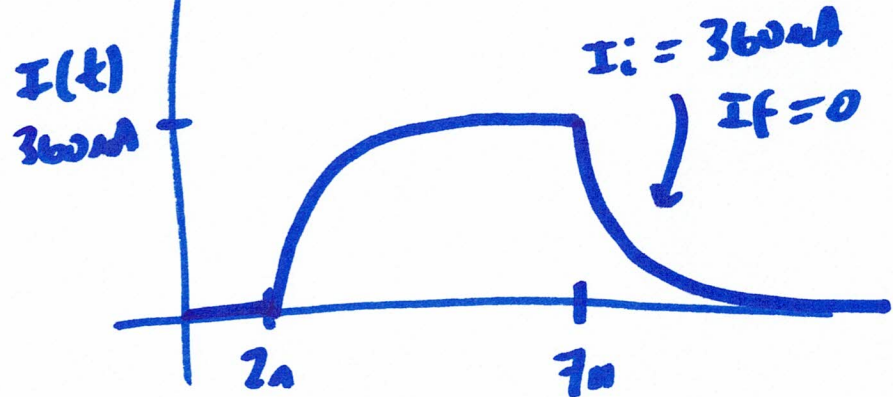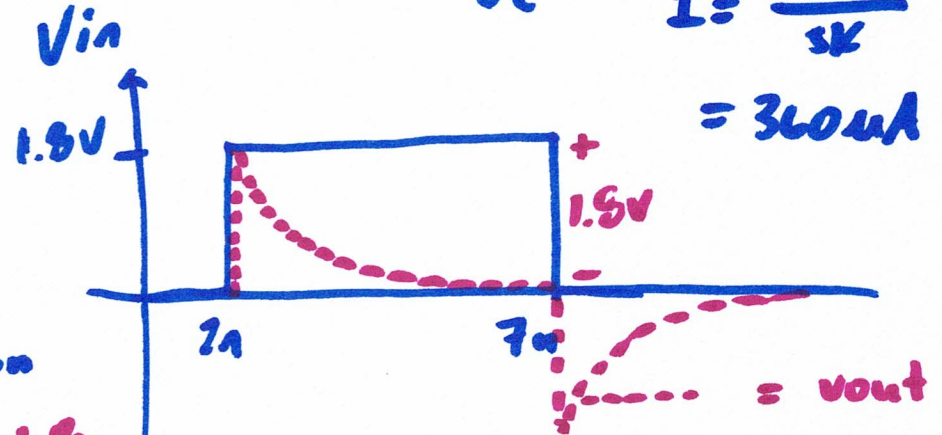
$$I_1(t) = 360 \mu\text{A} + (0 - 360 \mu\text{A}) e^{-(t - 2 \text{ ns}) / 0.6 \text{ ns}}$$



$$I(t) = \begin{cases} 0 \\ I_1(t) \end{cases}$$

$$\begin{aligned} t < 2 \text{ ns} \\ 2 \text{ ns} \leq t < 7 \text{ ns} \\ t \geq 7 \text{ ns} \end{aligned}$$

AC circuits

$f = 1\text{kHz}$

$f = \frac{1}{T} \Leftrightarrow T = \frac{1}{f}$
 (rad/s) (Hz)

types of signals:




sine angular actual



square

$\omega = 2\pi \cdot f$

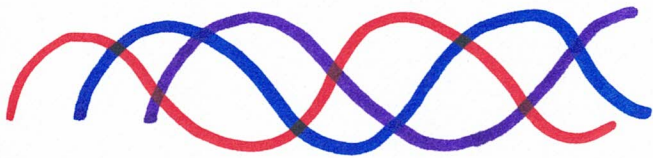

triangle



sawtooth

angular frequency (rad/s)

mainly focused on sine waves: $v(t) = V_A \sin(\omega t + \phi)$

↑
amplitude

↓
phase shift

$\sin(650t)$

$\uparrow \frac{650}{2\pi} = f$

$v(t) = V_A \sin(2\pi \cdot f \cdot t + \phi)$
 $2 \sin(2\pi \cdot 1\text{k} \cdot t + \phi)$