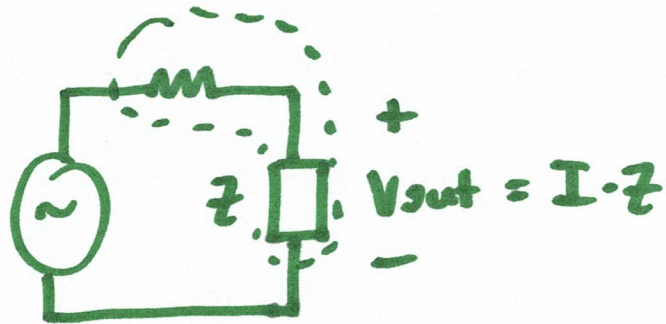


EE 220: Circuits I



$$R + j\omega L$$

↑ ↑

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\phi = \tan^{-1}\left(\frac{Y}{X}\right)$$

$$Z = X + jY$$

$$Z_R = R = R + j0 \rightarrow \phi = \tan^{-1}\left(\frac{0}{R}\right)$$

$$Z_C = \frac{1}{j\omega C} = -j \cdot \frac{1}{\omega C} \rightarrow \phi = \tan^{-1}\left(\frac{-Y}{X}\right) = -90^\circ$$



$$Z_L = j\omega L \Rightarrow \phi = \tan^{-1}\left(\frac{+Y}{X}\right) = 90^\circ$$

RLC Circuit Example

impedance

$R + jZ$
 ↑ resistance ↗ reactance

$f = 10\text{kHz}$

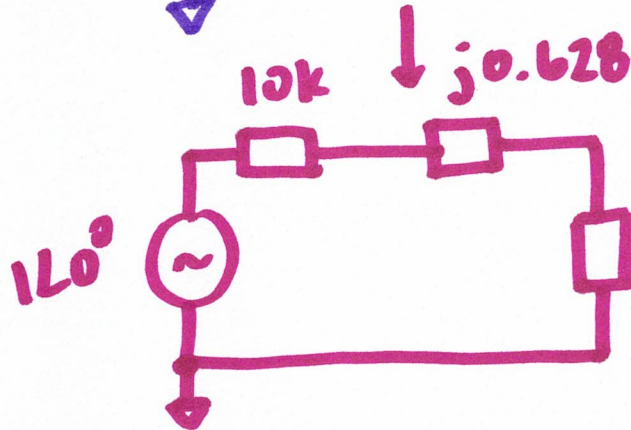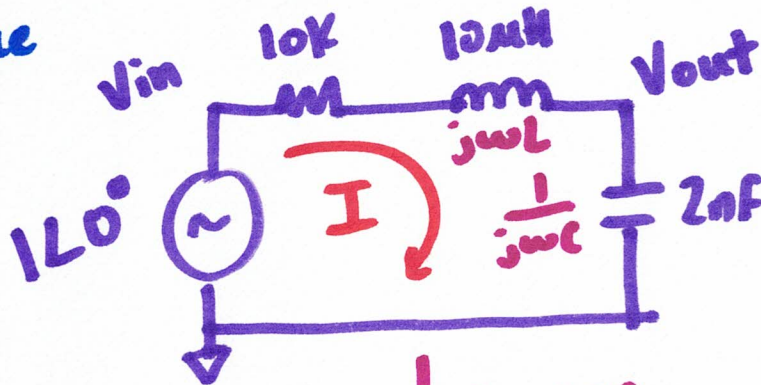

$$I = \frac{V_{in}}{Z_T} = \frac{1 \angle 0^\circ}{12.78\text{k} \angle -38.5^\circ}$$

$I = 78.2 \mu \angle 38.5^\circ \text{ A}$

$|V_{out}| = 622 \text{ mV}$
 $\angle V_{out} = -51.5^\circ$

$\mu \rightarrow \text{micro} \rightarrow 10^{-6}$
 $\text{m} \rightarrow \text{milli} \rightarrow 10^{-3}$

$Z_T = 10\text{k} + j0.628 - j7.957\text{k}$
 $Z_T = 10\text{k} - j7.957\text{k}$


$|Z_T| = \sqrt{(10\text{k})^2 + (7.957\text{k})^2}$
 $|Z_T| = 12.779\text{k}$
 $\phi = \tan^{-1}\left(\frac{-7.957\text{k}}{10\text{k}}\right)$

$\phi = -38.5^\circ$

$\therefore Z_T = 12.779\text{k} \angle -38.5^\circ$

RLC continued

$$I = 78.2 \angle 38.5^\circ \mu A$$

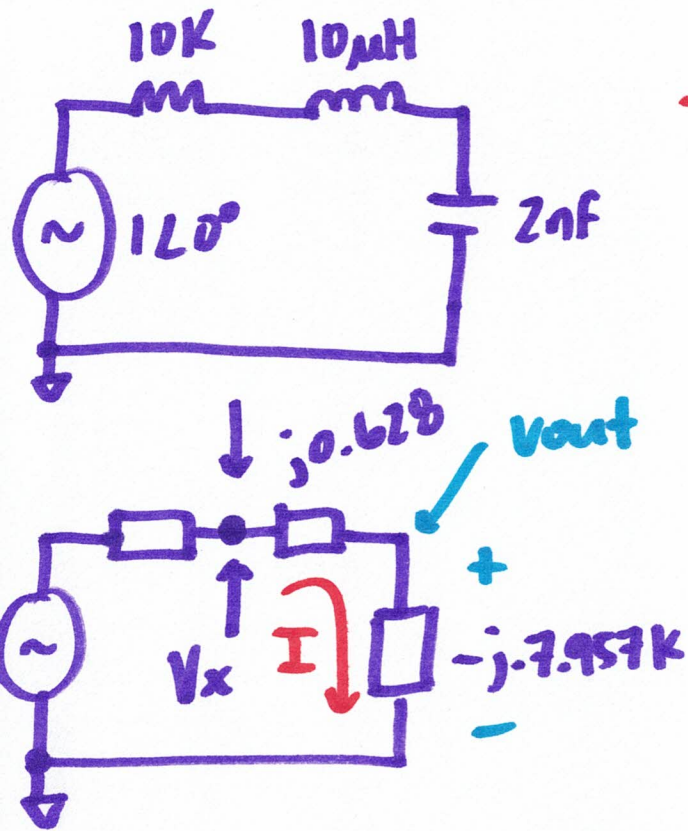

$$V_{out} = I \cdot Z_c$$

$$78.2 \angle 38.5^\circ \mu A \cdot -j 7.957 K$$

$$\tan^{-1}\left(\frac{-7.957 K}{0}\right) = -90^\circ$$

$$|Z_c| = \sqrt{0^2 + (7.957 K)^2}$$

$$|Z_c| = 7.957 K$$

$$\therefore Z_c = 7.957 K \angle -90^\circ \Omega$$

$$V_{out} = I \cdot Z_c = (78.2 \mu A \angle 38.5^\circ) \cdot (7.957 K \angle -90^\circ)$$

$$V_{out} = 0.622 \angle -51.5^\circ V$$