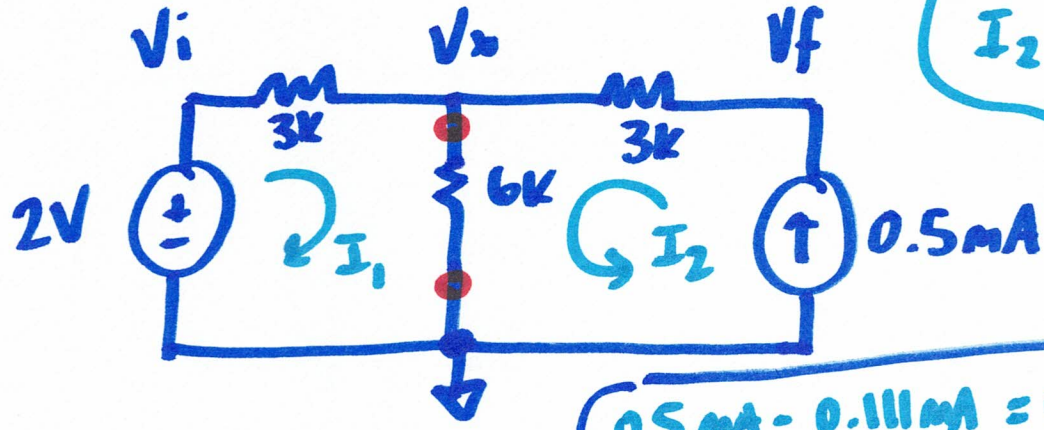


EE 220: Circuits I [Exam Review 1]

- Thevenin & Norton examples ✓
- mesh analysis / superposition ✓
- AC steady state analysis (phasor problems)
- Dependent sources ✓
- charge sharing ✓
- caps (DC open) & inductors (DC short)
- AC signals (sinusoids)

Q8



$$I_1: 2V - I_1 \cdot 3k - (I_1 + 0.5mA) \cdot 6k = 0$$

$$I_2 = 0.5mA$$

$$2V - I_1 \cdot 9k - 3V = 0$$

$$-1V = +I_1 \cdot 9k$$

$$I_1 = \frac{1V}{9k} = 0.111mA$$

$$0.5mA - 0.111mA = 0.339mA$$


$$V_x = (I_1 + I_2) \cdot 6k = 0.339mA \cdot 6k$$

~~$V_x = 2.034V$~~

✓ wrong!!
use spice!!

$$V_x = 2.33V$$

Finding V_{th} :

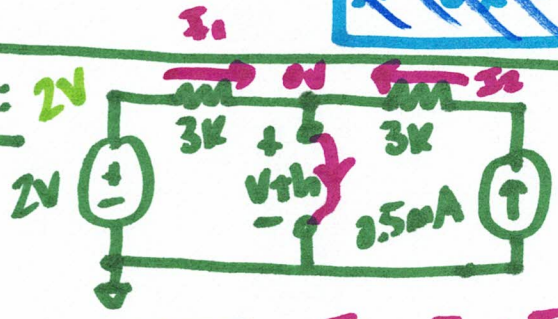


$$-1.5V + \frac{2V \cdot 3k}{3k + 3k} = V_{th}$$

$$V_{th} = 3.5V$$

$$I_1 + I_2 = I_{sc} = I_N$$

Finding R_{th} :

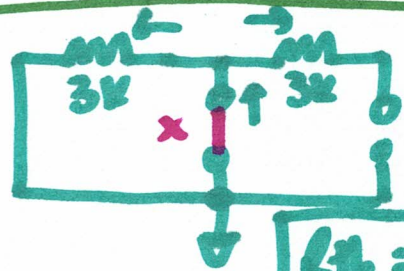


$$R_{th} = 3k$$

Finding I_N :

$$I_N = \frac{V_{th}}{R_{th}} = \frac{3.5V}{3k} = 1.166mA = I_N$$

MT-P3

$V_{L1} + V_{L2} = V_C$

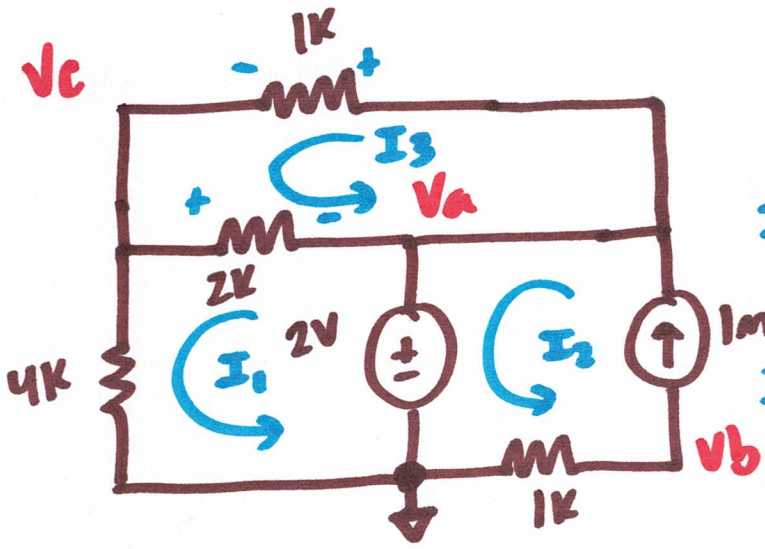

$I_2 = 1mA$

$I_3: -I_3 \cdot 1k - (I_3 - I_1) \cdot 2k = 0$

$I_1: 2V - (I_1 - I_3) \cdot 2k - I_1 \cdot 4k = 0$




⋮

$I_1 = \text{something} \cdot I_3$


Mesh

Superposition

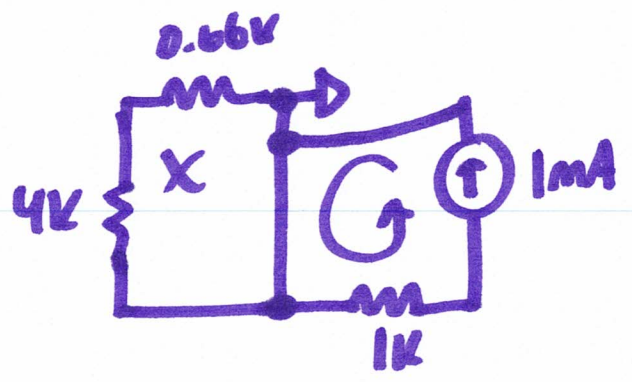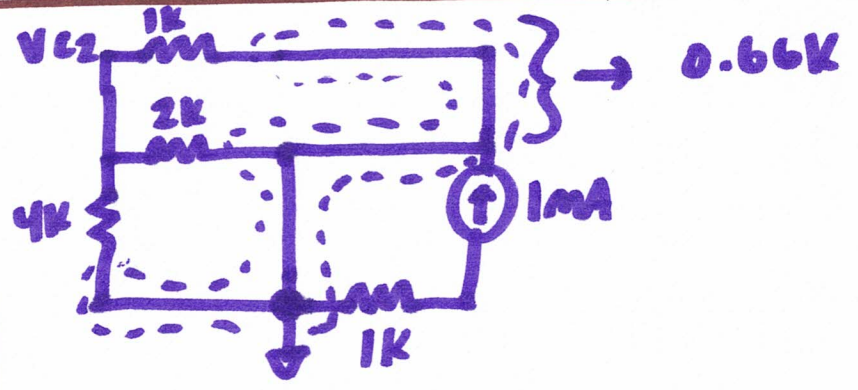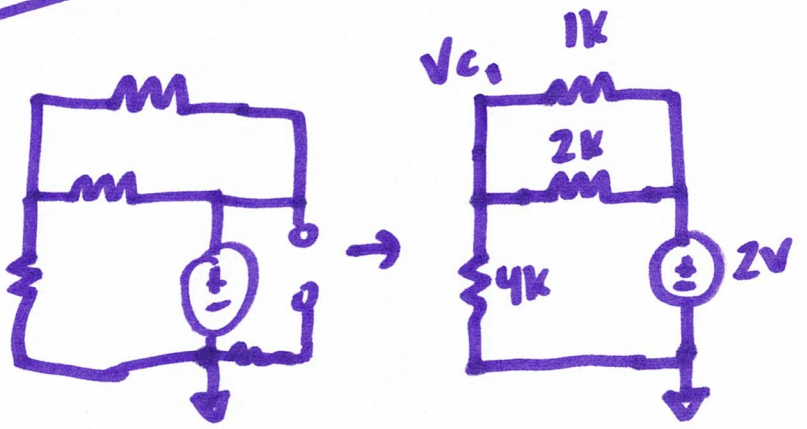$2V \left(\frac{4k}{0.66k + 4k} \right) = V_{L1}$




Calculus FI7 MT P.2

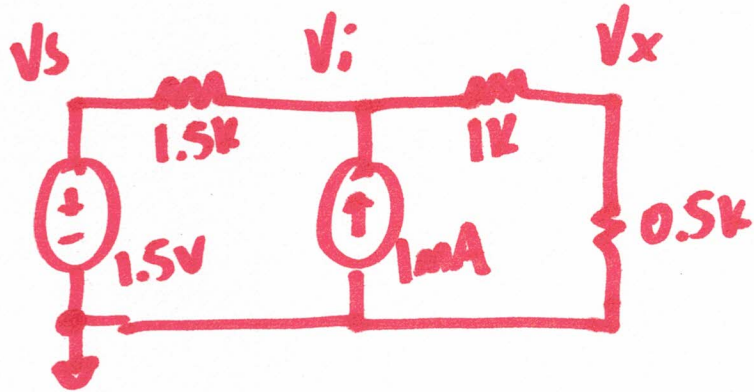


$$V_x = V_{x_1} + V_{x_2}$$
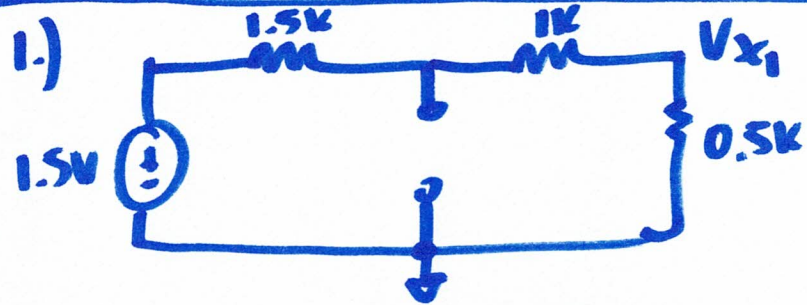
$$V_x = \underline{0.25} + \underline{0.25} = 0.5V$$



$$V_{x_1} = 1.5V \left(\frac{0.5k}{2.5k + 0.5k} \right) = 1.5V \left(\frac{1}{6} \right)$$

$$V_{x_1} = 0.25V$$

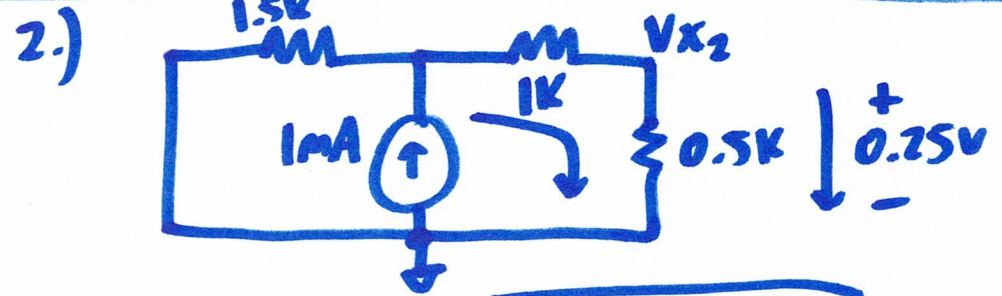


$$V_{x_2} = 0.25V$$

$$V_x = 0.25 + 0.25 = 0.5V$$

Dependent Sources


CCVS \rightarrow current controlled voltage source
CCCS \rightarrow current controlled current source
VCVS \rightarrow voltage controlled voltage source
VCCS \rightarrow voltage controlled current source

Baker F17 MT, P5

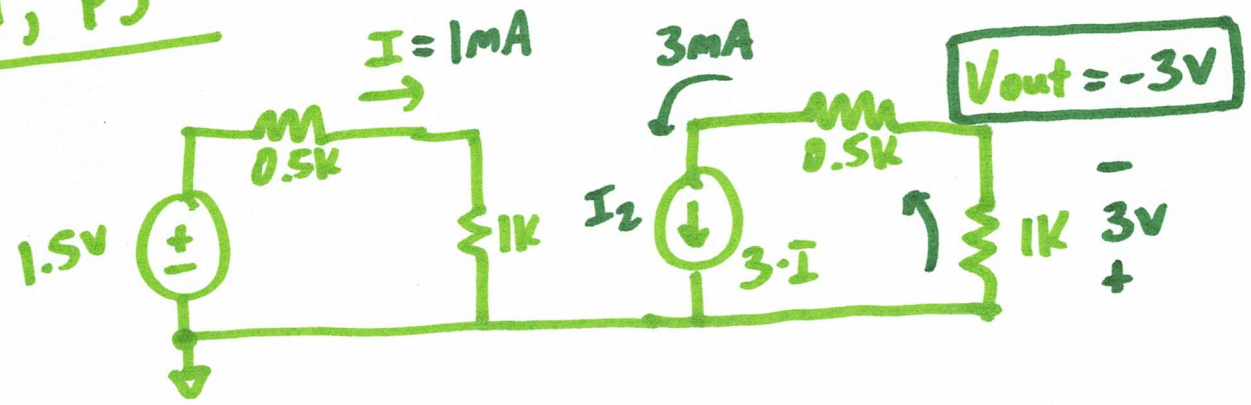


$$I = \frac{1.5V}{1.5k} = 1mA$$

Baker F16 MT, P5

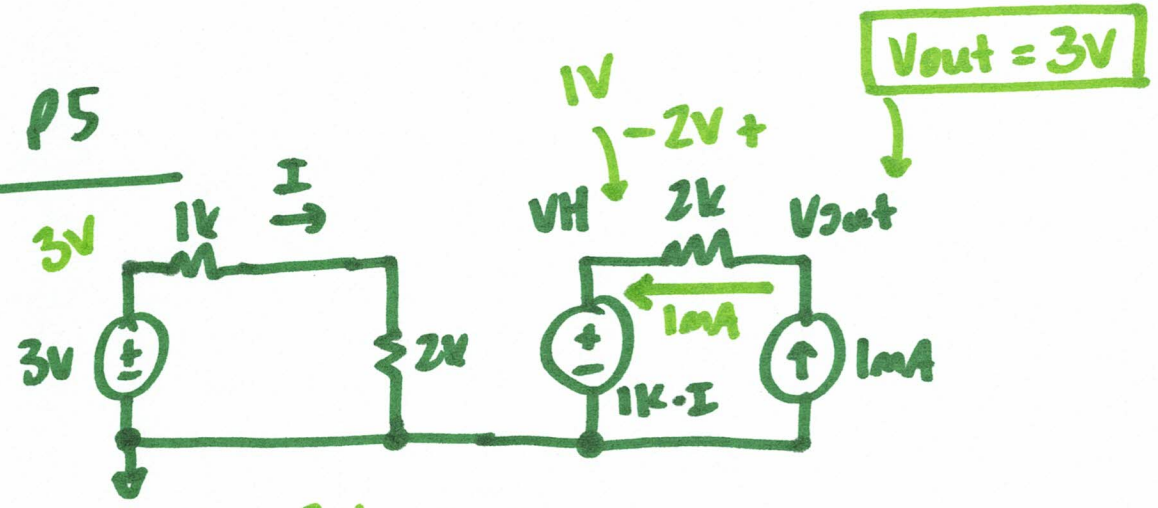

$$I = \frac{3V}{3k} = 1mA$$


Charge sharing

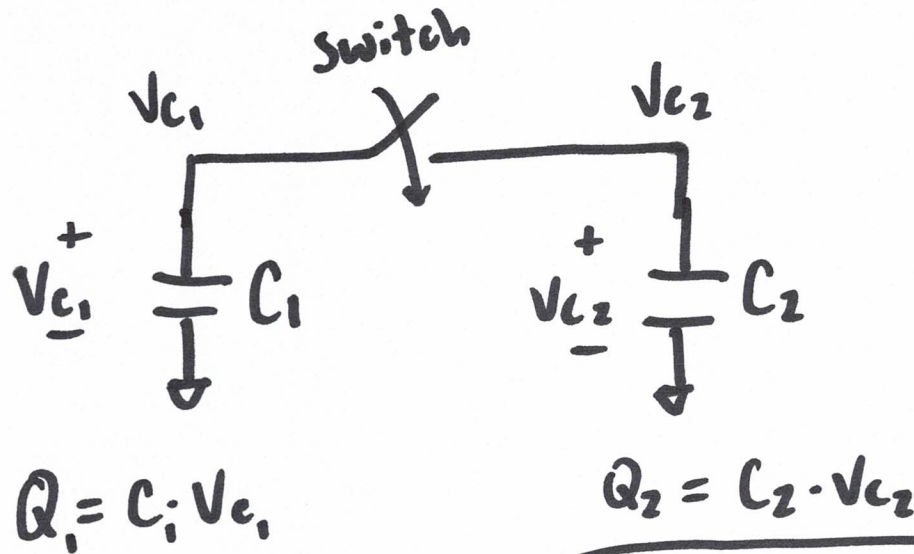

$$C_{\text{new}} = C_1 + C_2$$
$$V_{\text{new}} = \frac{Q_{\text{TOT}}}{C_1 + C_2}$$

$$C \cdot V = Q$$
$$V = \frac{Q}{C}$$

$$Q_{\text{TOT}} = Q_1 + Q_2$$

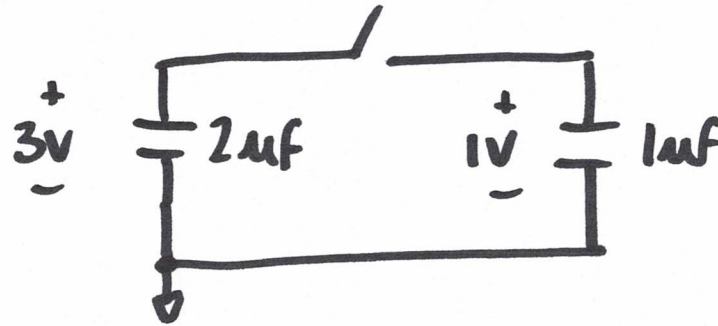

$$Q_{\text{TOT}} = 7\mu\text{C}$$
$$C_F = 3\mu\text{F}$$

$$Q_1 = 3\text{V} \cdot 2\mu\text{F} = 6\mu\text{C} \quad Q_2 = 1\text{V} \cdot 1\mu\text{F} = 1\mu\text{C}$$

$$C_F \cdot V_F = Q_{\text{TOT}} \rightarrow V_F = \frac{Q_{\text{TOT}}}{C_F} = \frac{7\mu\text{C}}{3\mu\text{F}}$$

$$V_F = 2.33\text{V}$$