
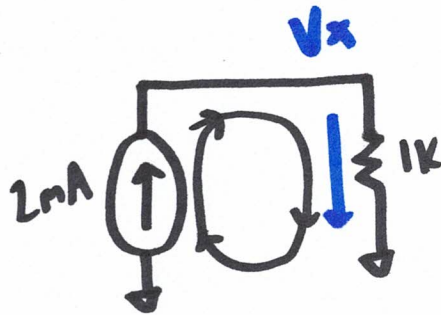


EE 220: Circuits I

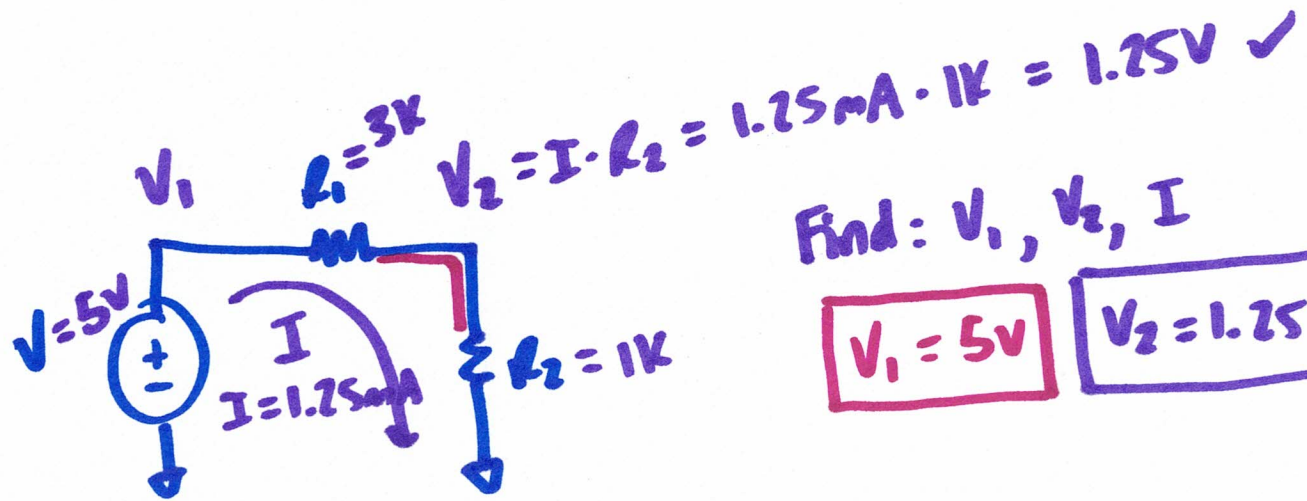- current sources
- series resistors, equivalents
- parallel resistors, equivalents
- examples



$$V = I \cdot R$$
$$V = 2\mu\text{A} \cdot 1\text{k}\Omega$$
$$V_x = 2\text{V}$$



Find: V_1, V_2, I


$V_1 = 5V$

$V_2 = 1.25V$

$I = 1.25mA$


* resistors connected in Series:

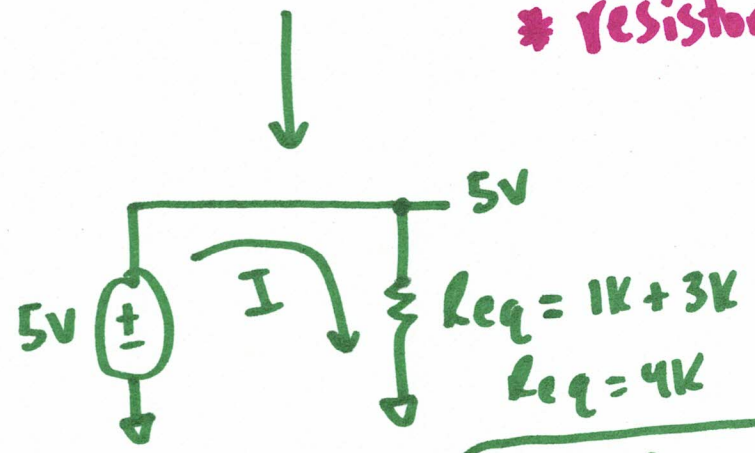- share one node
- same current through them
- To find R_{eq} , add their values




$I = V/R = \frac{5V}{4k} = 1.25mA$

$R_{eq} = R_1 + R_2 + R_3 + R_4$

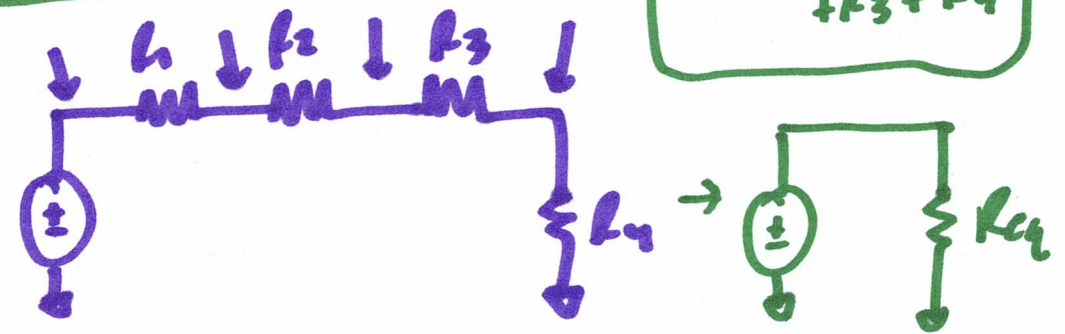


Voltage divider

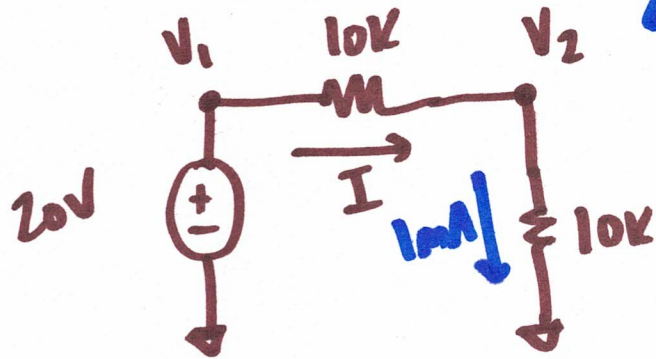

$$V_1 = 20V$$

$$V_2 = 1mA \cdot 10V$$


$$V_2 = 10V$$

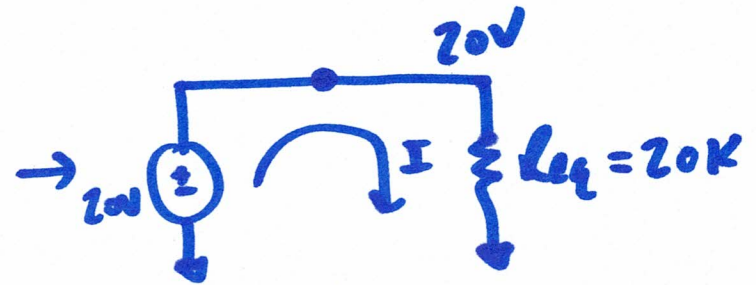

$$I = \frac{20V}{20K} = 1mA$$


Series: same current, share one node
 parallel: same voltage, share two nodes
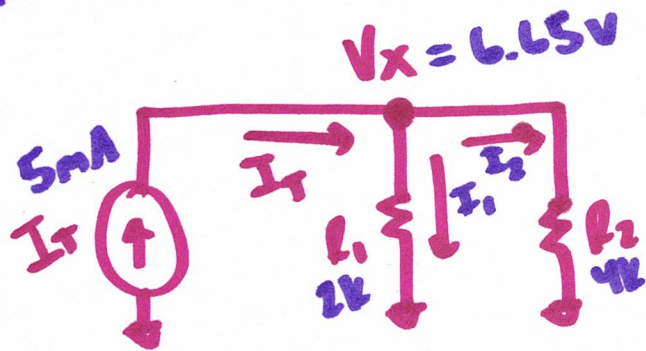
$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{eq}}$$



$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

"product over sum"

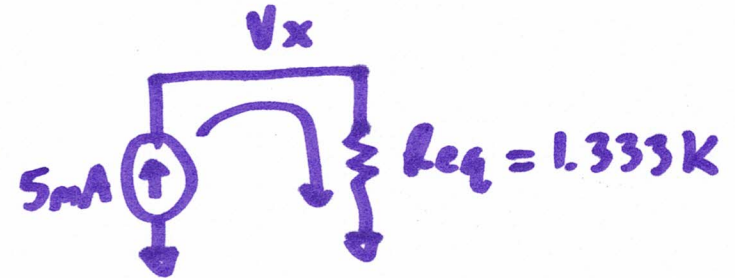


KCL: Kirchhoff's
 Current
 Law

$$I_T = I_1 + I_2$$

$$V_x = 5\mu A \cdot 1.333k$$

$$V_x = 6.65V$$
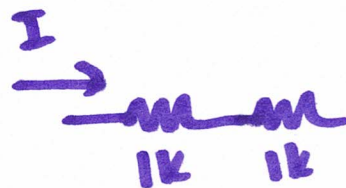
$$\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \frac{1}{R_{eq}}$$




$$R_{eq} = 2k$$

$$I_1 = \frac{6.65V}{2k} = 3.33mA$$

$$I_2 = \frac{6.65V}{4k} = 1.66mA$$

EE 220: Circuits I

HW1: 3c

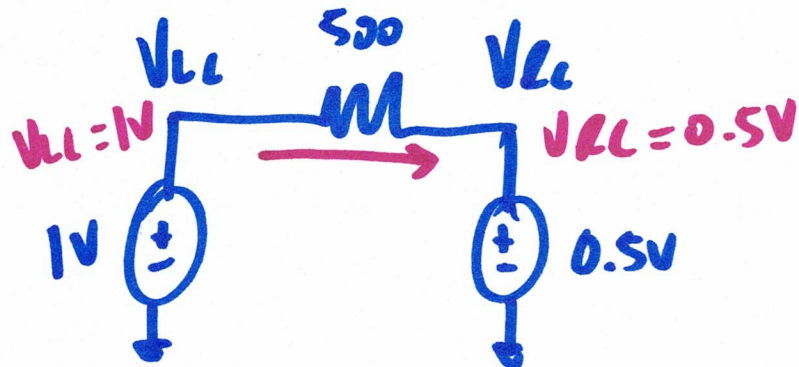

$$\frac{1V - 0.5V}{500} = \frac{0.5}{500} = 1mA$$



0.001A



HW1: 3a



$$I = \frac{V}{R}$$

HW1: 1b

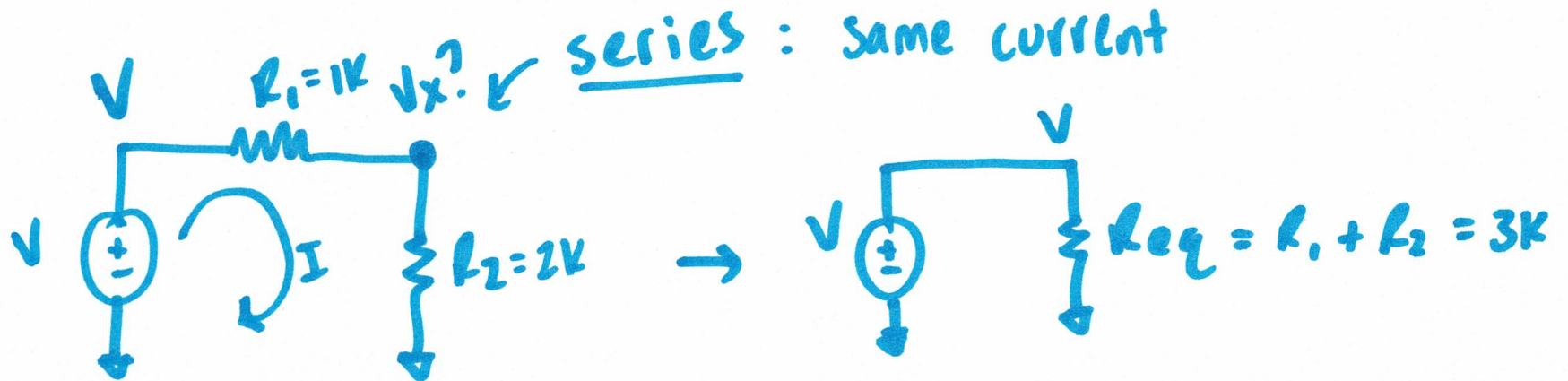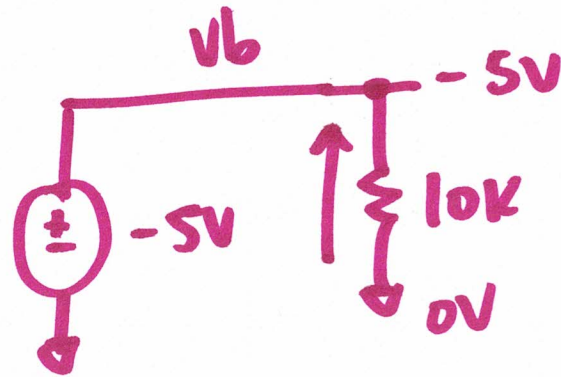


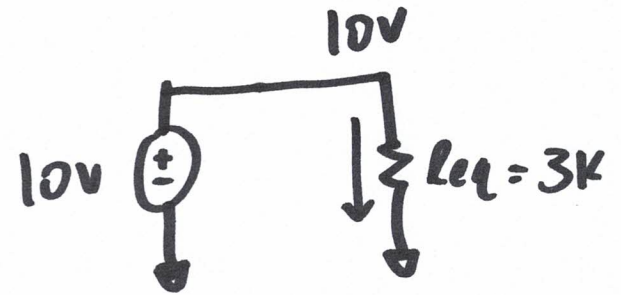
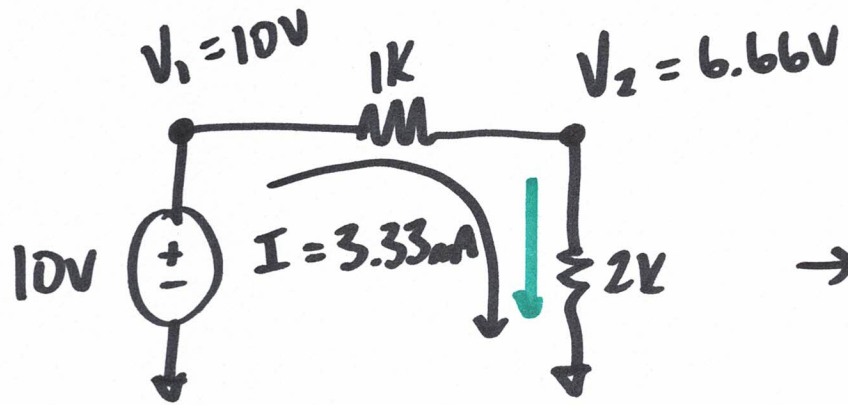


$$V = IR$$


$$V = 3.33 \mu\text{A} \cdot 2 \mu\text{a}$$

$V_2 = 6.66 \text{ V}$
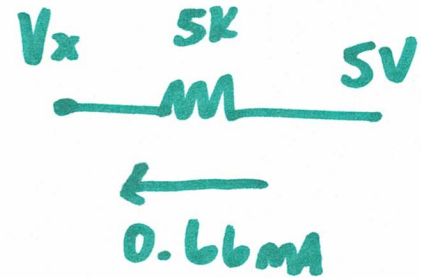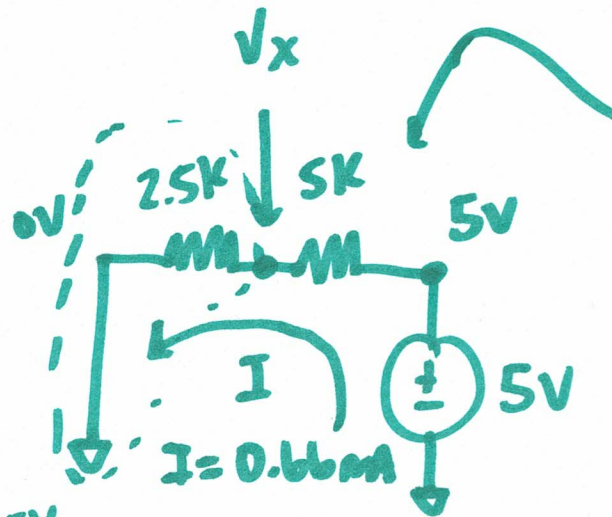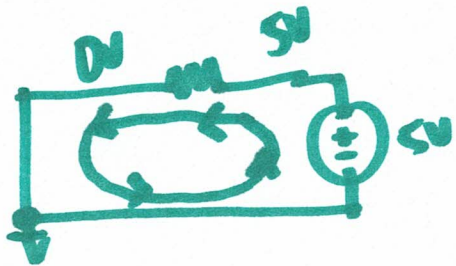
$$\frac{10\text{V} - 0\text{V}}{3\text{k}} = \boxed{3.33\text{mA}}$$



$$V = IR$$

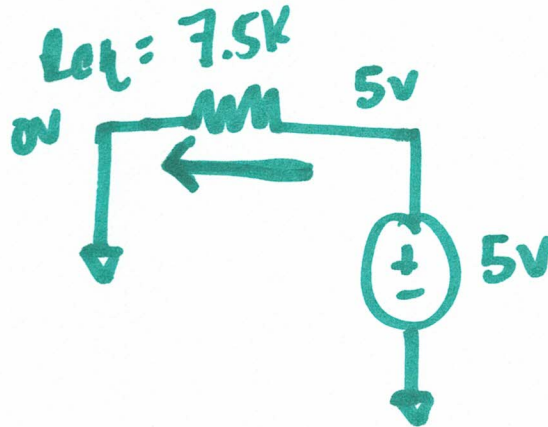

$$I = V/R$$

$$I = \frac{5V}{7.5k} = 666.66\mu A = 0.666mA$$

$$= 0.666mA$$



$$V_x = 0.66mA \cdot 2.5k$$

$$V_x =$$

$$V = 5V - V_x = 0.66\mu A \cdot 5k$$


$$5V - V_x = 3.3V$$

$$+ V_x \quad + V_x$$


$$5V - 3.3V = V_x$$

$$V_x = 1.7V$$

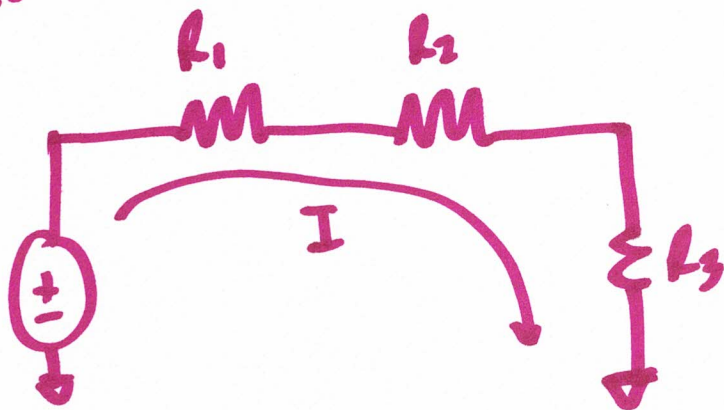
Series resistors: same current, not necessarily same voltage



$$R_{eq} = R_1 + R_2 + R_3$$

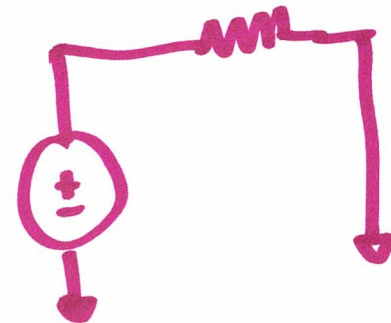

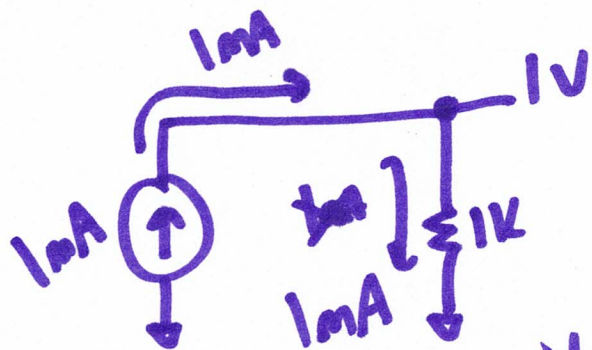
Parallel resistors: same voltage, not necessarily same current.



$$V = I \cdot R$$




$$V = 1mA \cdot 1k$$

$$V = 1V$$

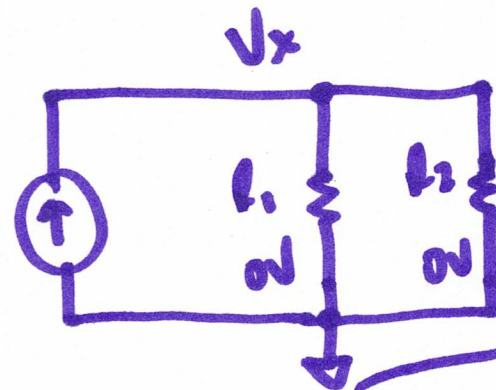


$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

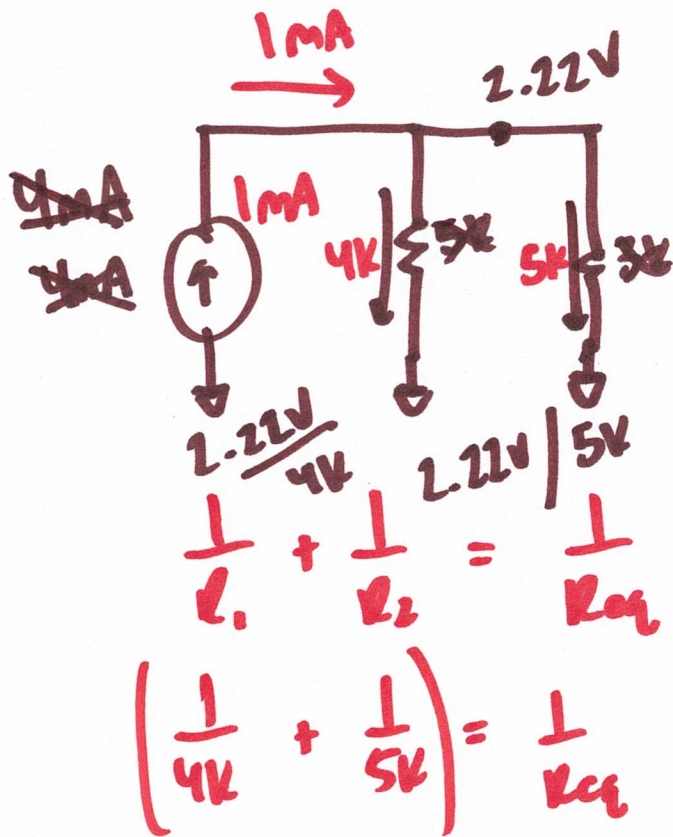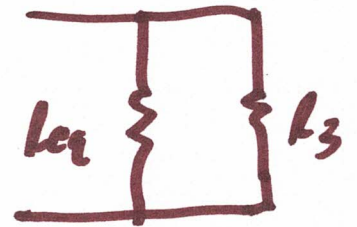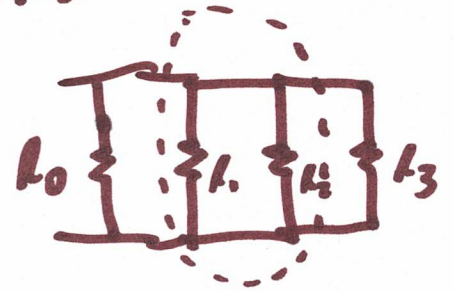parallel resistors: $R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$



$$R_{eq} = \frac{4k \cdot 5k}{4k + 5k}$$

$$R_{eq} = 2.22k$$

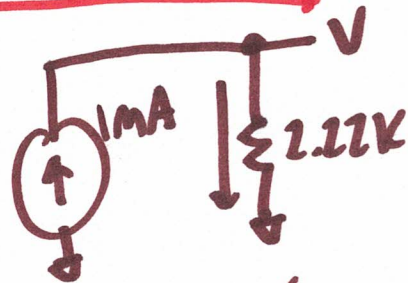


$$V = 1mA \cdot 2.22k$$

$$V = 2.22V$$



$$\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} = \frac{1}{R_{eq}}$$

KCL:

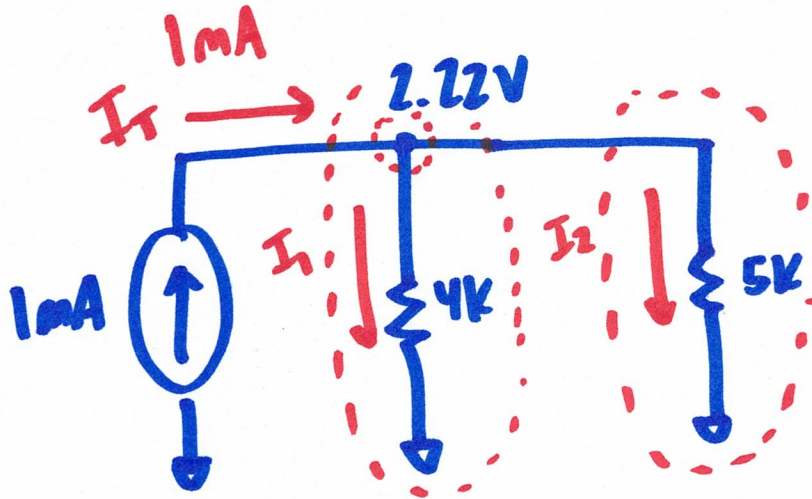



$$2.22\text{V} \text{ --- } \frac{4\text{k}}{\text{---}} \text{ --- } 0\text{V}$$

$$I_1 = V/R = \frac{2.22\text{V}}{4\text{k}} = 0.555\text{mA}$$

$$2.22\text{V} \text{ --- } \frac{5\text{k}}{\text{---}} \text{ --- } 0\text{V}$$

$$I_2 = V/R = \frac{2.22\text{V}}{5\text{k}} = 0.444\text{mA}$$

} 0.199mA
≈ 1mA

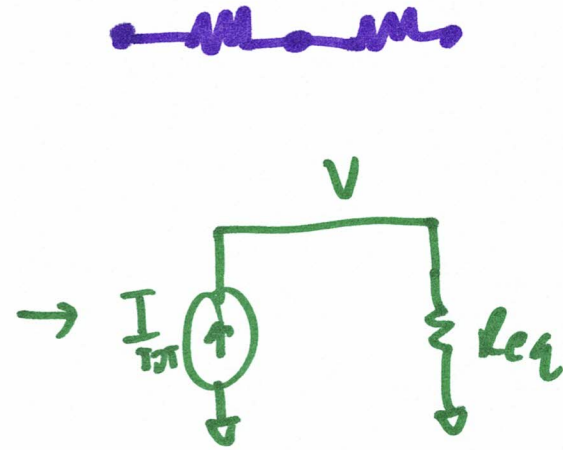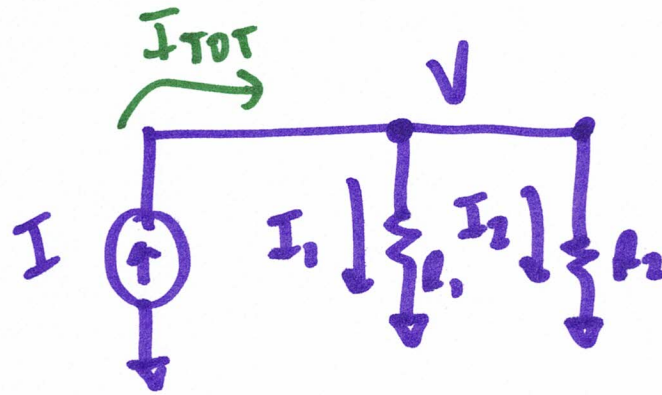

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} \frac{(R_1 \cdot R_2)}{(R_1 \cdot R_2)}$$

$$R_{eq} = \frac{R_1 \cdot R_2}{R_2 + R_1}$$

"product over sum"

$$I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

$$I_{TOT} = \frac{V}{R_{eq}}$$

$$I_{TOT} = I_1 + I_2$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\sqrt{\left(\frac{1}{R_{eq}}\right)} = \sqrt{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \dots$$