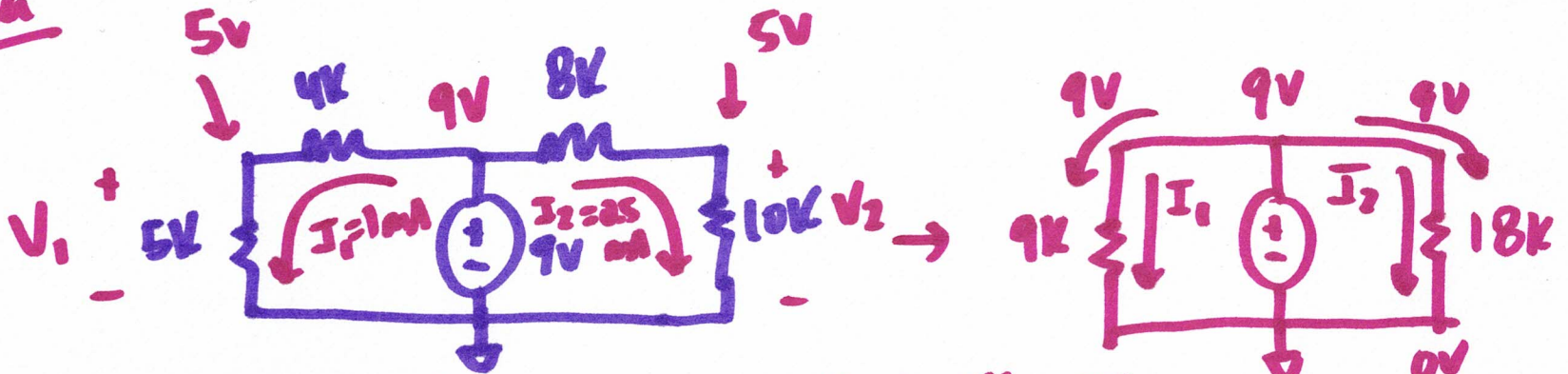


EE 220: Circuits I

HW2: 3a




$$V_1 = 1\text{mA} \cdot 5\text{k} = 5\text{V}$$


$$V_2 = 0.5\text{mA} \cdot 10\text{k} = 5\text{V}$$

$$V_2 = 5\text{V}$$


$$I_1 = \frac{9\text{V} - 0\text{V}}{9\text{k}} = 1\text{mA}$$
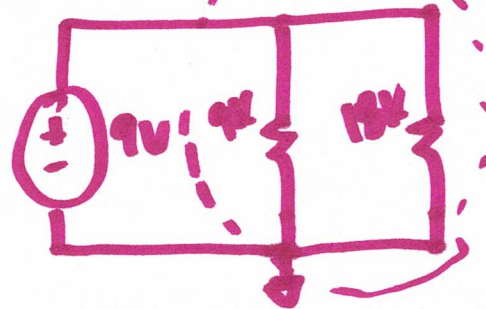
$$I_2 = \frac{9\text{V} - 0\text{V}}{18\text{k}} = 0.5\text{mA}$$



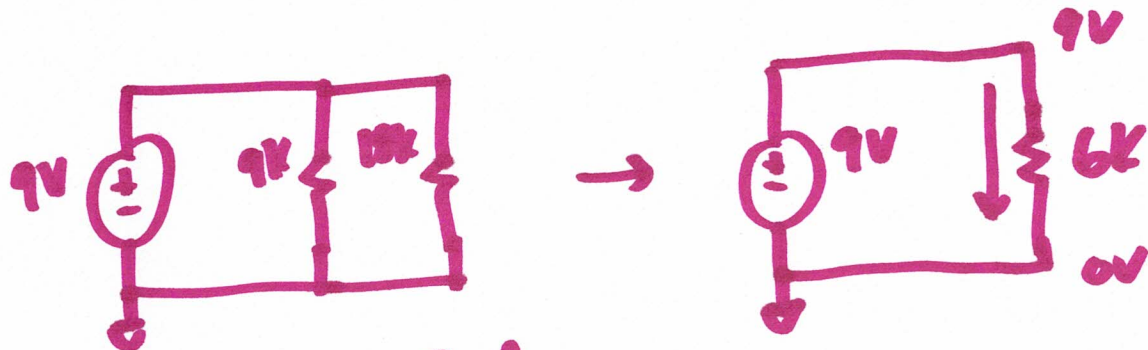


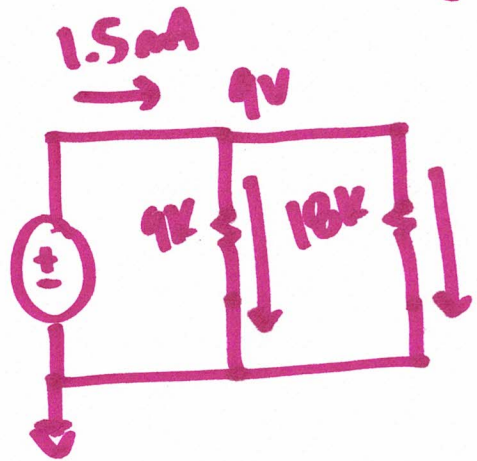$V = IR$
 $\frac{10V}{V_1} + \frac{V}{R} = \frac{9V}{V_2}$
 $\frac{V_1}{R} + \frac{V_2 - V_1}{R} = \frac{9V}{V_2}$





$\frac{9V - 0V}{6k} = 1.5mA$

$\frac{V_2 - V_1}{R} = I$





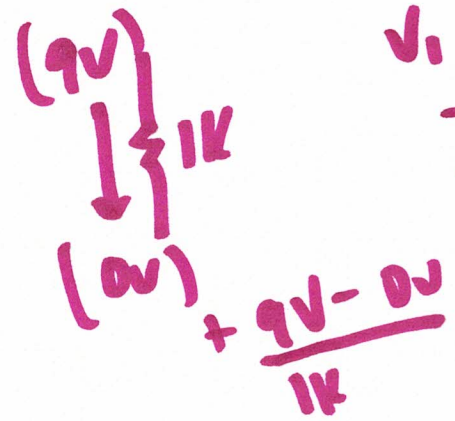


$\frac{V_1 - V_2}{R} = I$

HW2: 2b

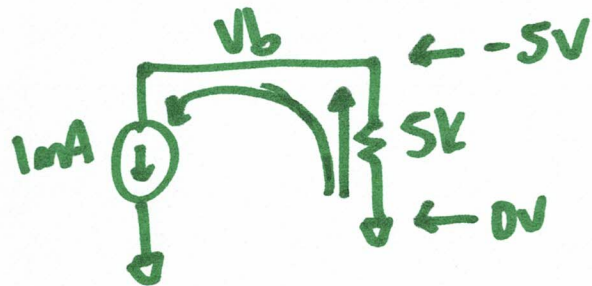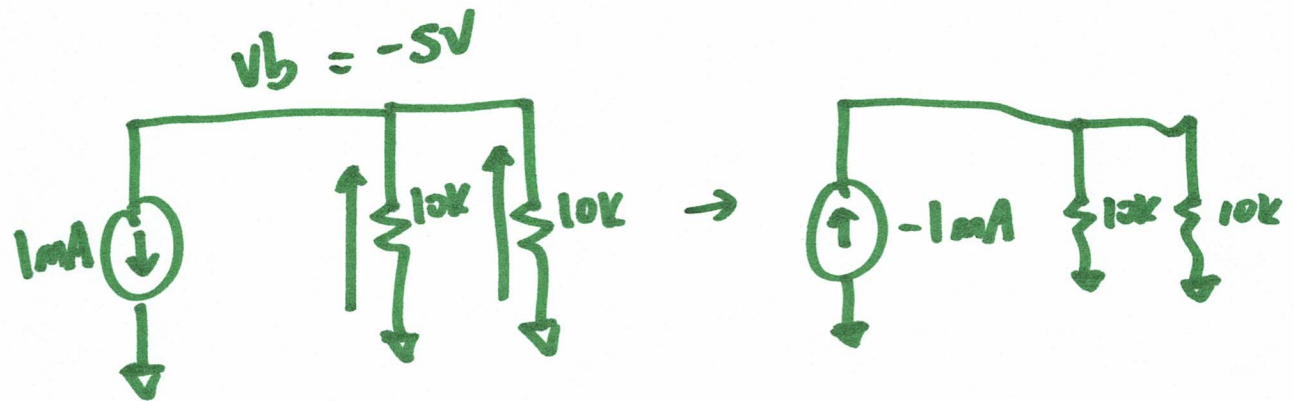
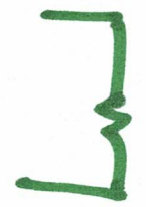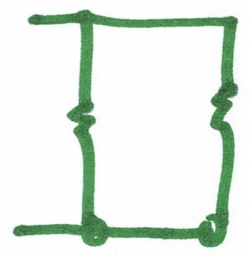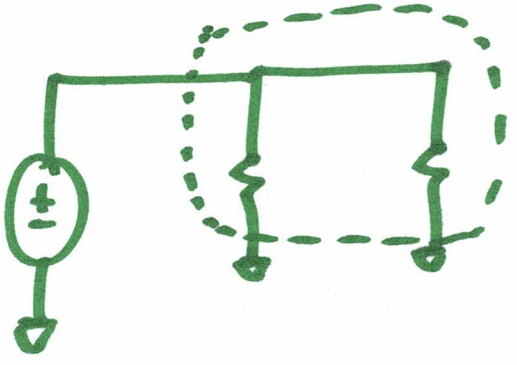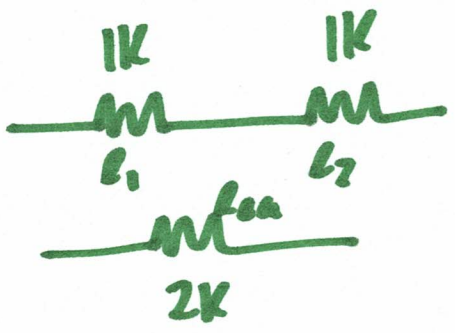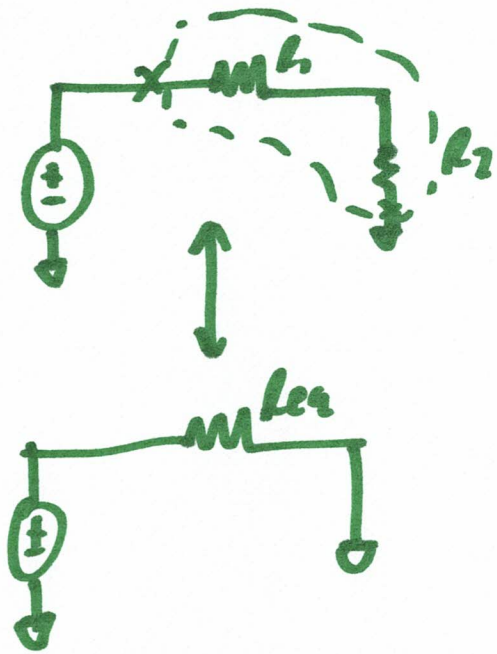
$$V = IR$$
$$V = 1mA \cdot 5k$$
$$V = 5V$$




* Sum of all currents out of a node = 0


↓
Kirchhoff's Current Law

KVL


↓
Kirchhoff's Voltage Law (KVL)

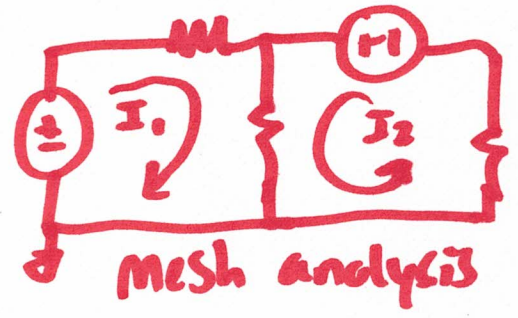

* Sum of all voltage drops in a loop = 0

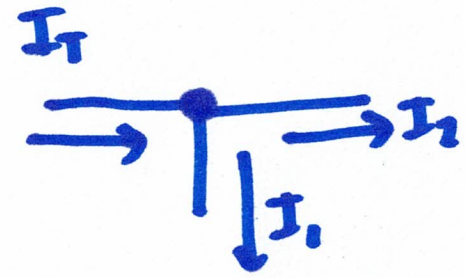


$$I_T = I_1 + I_2$$

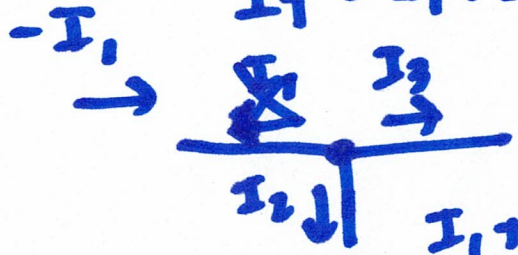

$$I_1 + I_2 + I_3 = 0$$

$$I_2 + I_3 - I_1 = 0$$

$$I_2 + I_3 = I_1$$

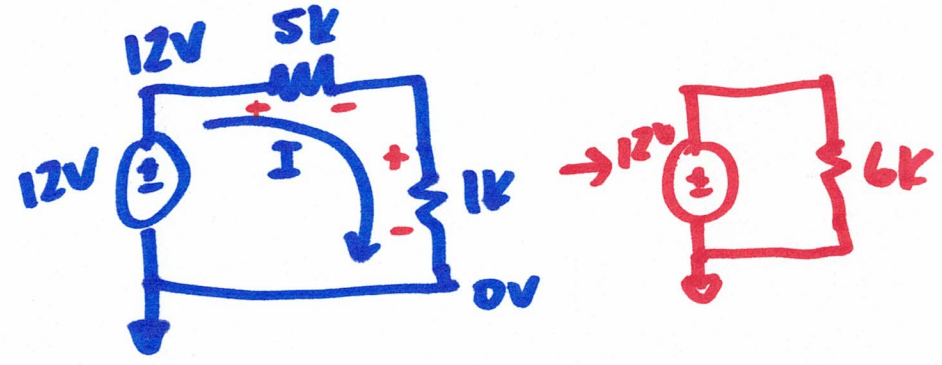


$$+12V - 5k \cdot I - 1k \cdot I = 0$$

$$12V - 6k \cdot I = 0$$

$$\frac{12V}{6k} = \frac{6k \cdot I}{6k} \rightarrow \boxed{I = 2mA}$$

HW3:1f

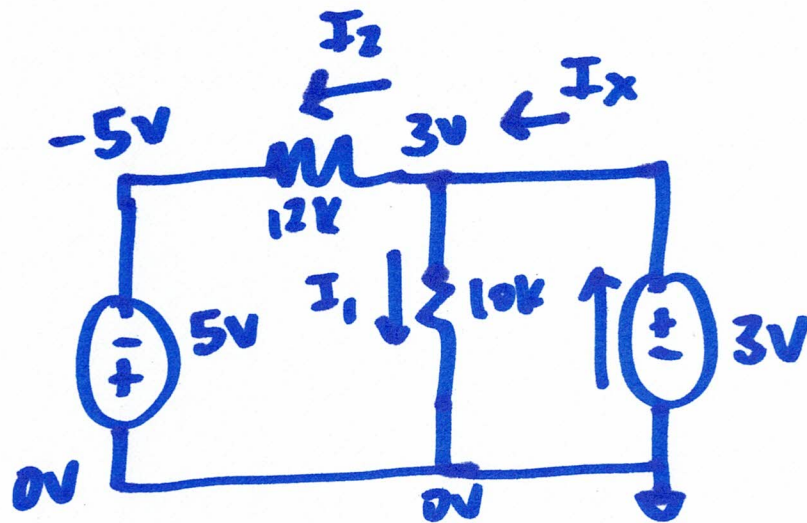


$$I_1 = \frac{3V - 0V}{10k} = 0.3mA = 300\mu A$$


$$I_2 = \frac{3V - (-5V)}{12k} = \frac{8V}{12k} = 0.666mA$$

$$I_1 + I_2 = I_x = 0.66mA + 0.3mA$$

$$\boxed{I_x = 0.96mA}$$

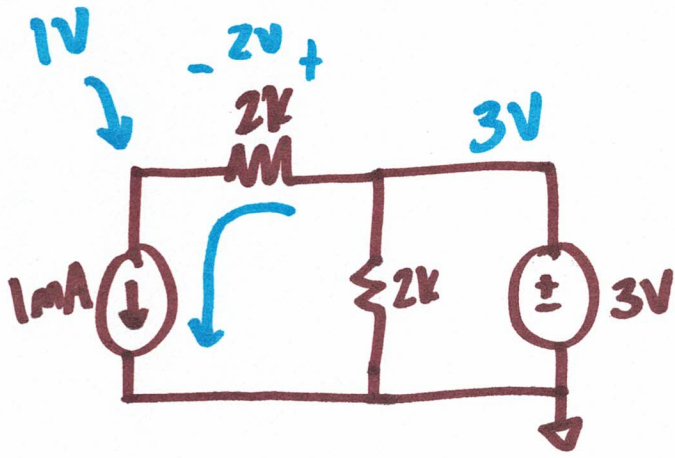


$$2k \cdot 1mA = 2V$$

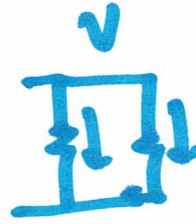

$$\frac{4.57}{4k} = I = 1.14mA$$

$$V_2 = -3.43V \quad V_1 = 4.57V$$

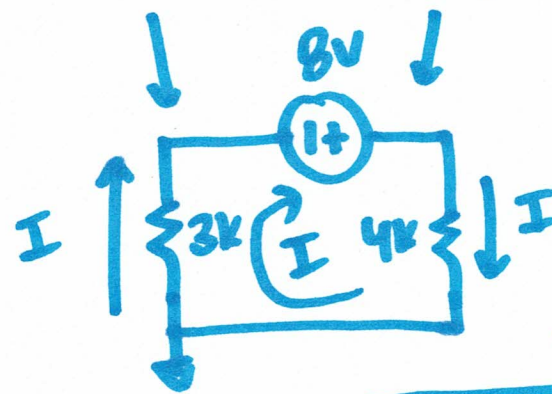

$$V_1 = -0.75V_1 + 8V + 0.75V_1$$

$$V_1 + 0.75V_1 = 8V$$

$$V_1(1 + 0.75) = 8$$

$$V_1 = \frac{8}{1.75}$$

$$V_1 = 4.57V$$

$$I = \frac{0 - V_2}{3k}$$

$$V_1 = V_2 + 8V$$

$$\frac{V_1}{4k} = I$$

$$\frac{-V_2}{3k} = \frac{V_1}{4k}$$

$$4.57V = V_2 + 8V$$

$$V_2 = -3.43V$$

$$-1 \cdot V_2 = 0.75V_1 \quad (-1)$$

$$V_2 = -0.75V_1$$