

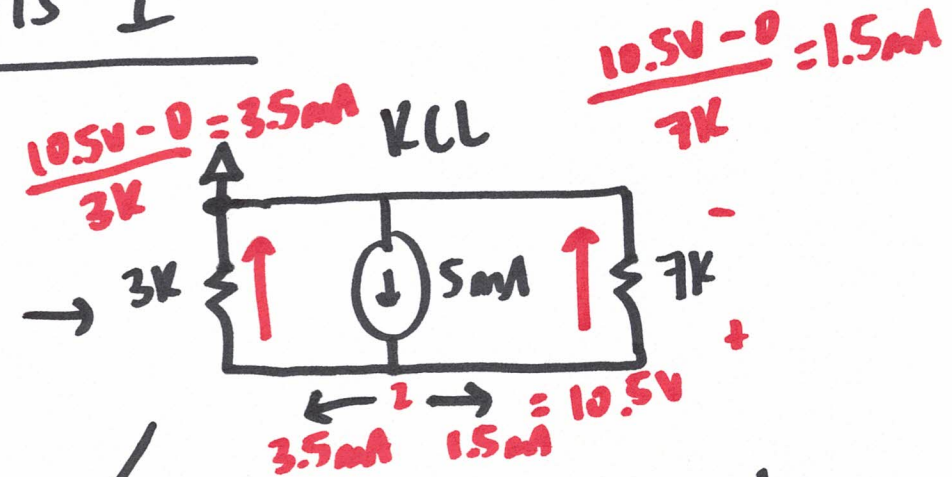


EE 220: Circuits I

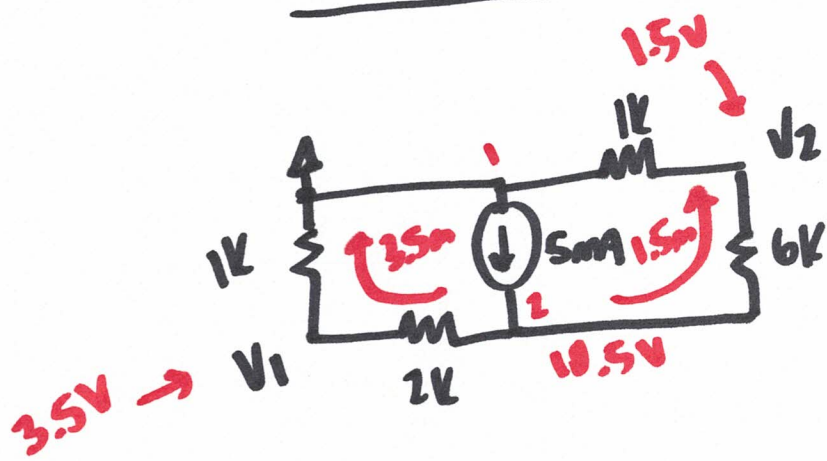


parallel: share 2 nodes
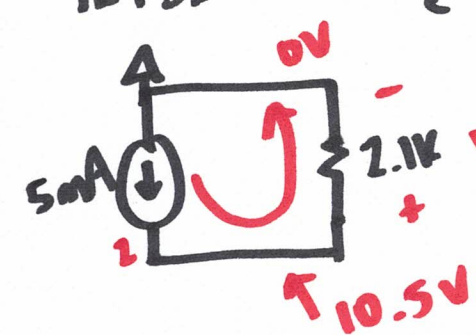
$$R_{eq} = \frac{7k \cdot 3k}{7k + 3k} = 2.1k$$



$$V = 5mA \cdot 2.1k = 10.5V$$

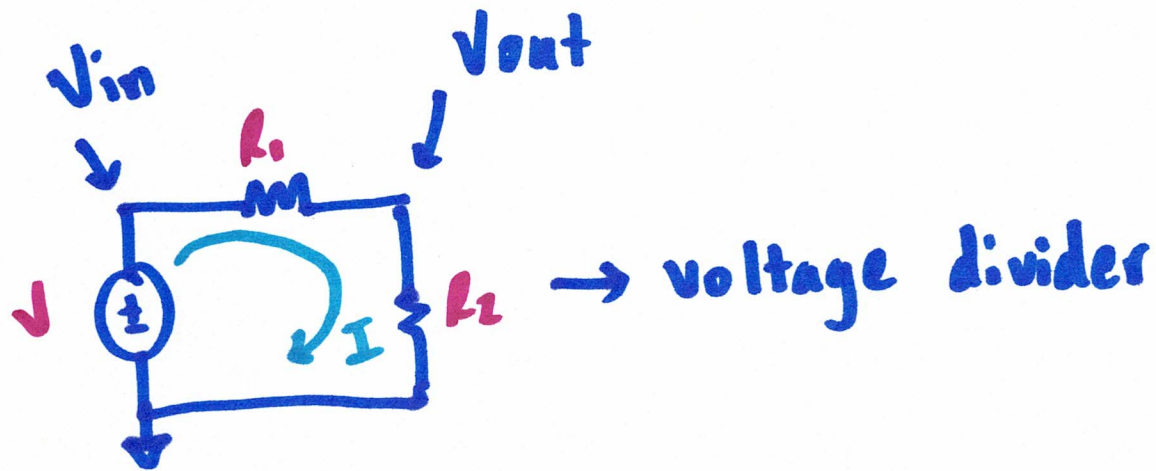

$$I = \frac{V_{in} - V_{out}}{R_1}$$

$$I = \frac{V_{out} - 0}{R_2} = \frac{V_{out}}{R_2}$$

$$\frac{V_{in} - V_{out}}{R_1} = \frac{V_{out}}{R_2}$$

$$\frac{V_{in}}{R_1} - \frac{V_{out}}{R_1} = \frac{V_{out}}{R_2}$$


$$\frac{V_{in}}{R_1} = \frac{V_{out}}{R_1} + \frac{V_{out}}{R_2} \rightarrow \frac{V_{in}}{R_1} = V_{out} \left[\frac{\frac{1}{R_1} + \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} \right]$$

$$V_{out} = \frac{(v_{in}/R_1) \cdot R_1 \cdot R_2}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \cdot R_1 \cdot R_2}$$

Voltage divider
Equation



$$V_{out} = \frac{v_{in} \cdot R_2}{R_2 + R_1}$$
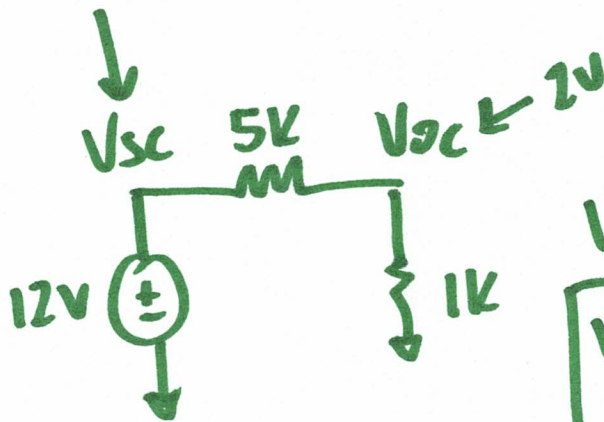
$$V_{out} = v_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$




$$V_{oc} = 12V \left(\frac{1k}{1k + 5k} \right)$$

$$V_{oc} = \frac{12}{6} = 2V$$

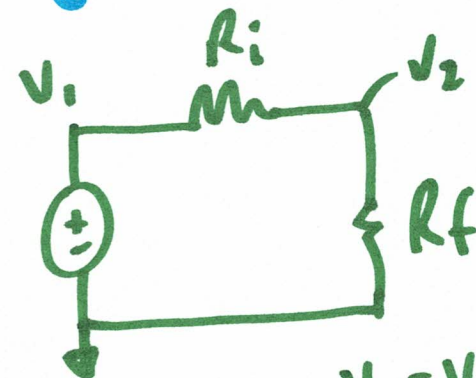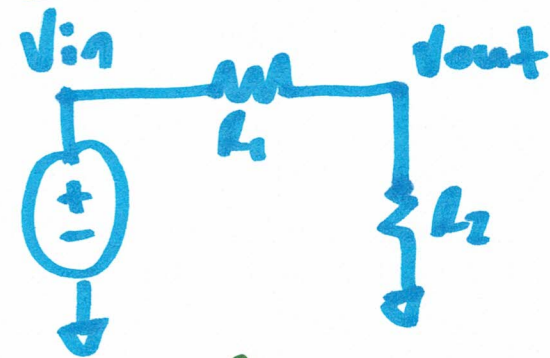


$$V_2 = V_1 \cdot \left(\frac{R_f}{R_i + R_f} \right)$$

Voltage Divider

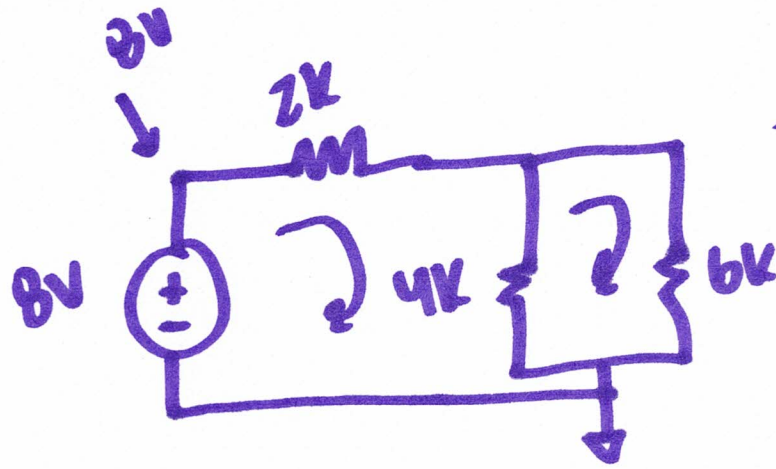

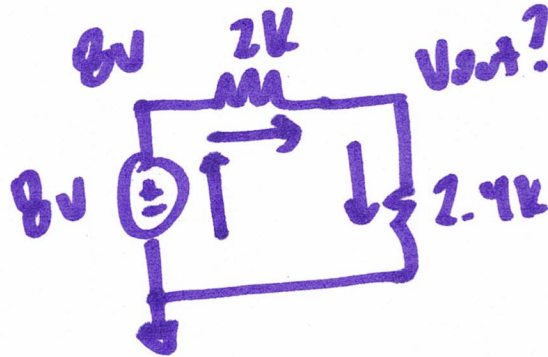
$$\rightarrow R_{eq} = \frac{4k \cdot 6k}{4k + 6k} = 2.4k$$




$$V_{out} = 8V \left(\frac{2.4k}{2k + 2.4k} \right)$$

$$V_{out} = ?$$

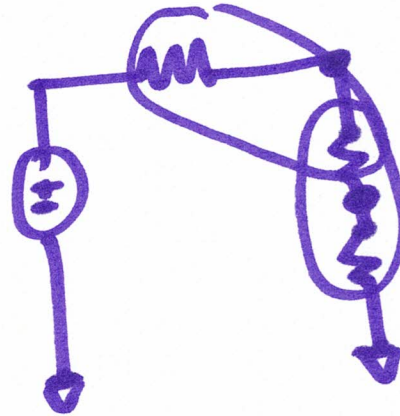

$$0 = 8V - I \cdot 2k - I \cdot 2.4k$$

Current Divider

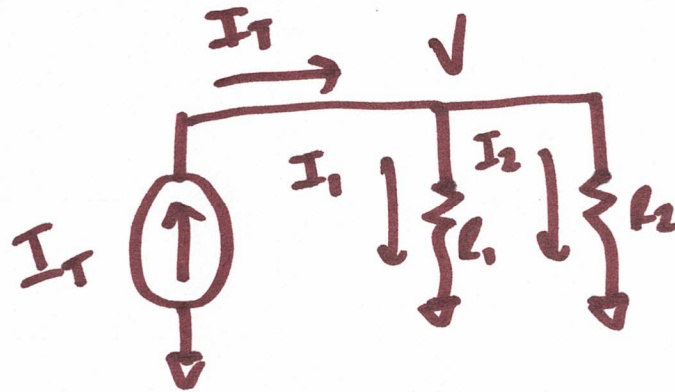

$$I_T = I_1 + I_2$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right)$$

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2}$$

$$I_T = \frac{V}{R_{eq}}$$


~~$$I_1 = \frac{I_T \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}}{R_1}$$

$$I_1 = I_T \cdot \frac{R_1 \cdot R_2}{R_1 \cdot (R_1 + R_2)}$$~~

$$I_T = \frac{V}{\left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right)} \rightarrow V = I_T \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_T = V \cdot \left(\frac{R_1 + R_2}{R_1 \cdot R_2} \right)$$

Current Divider

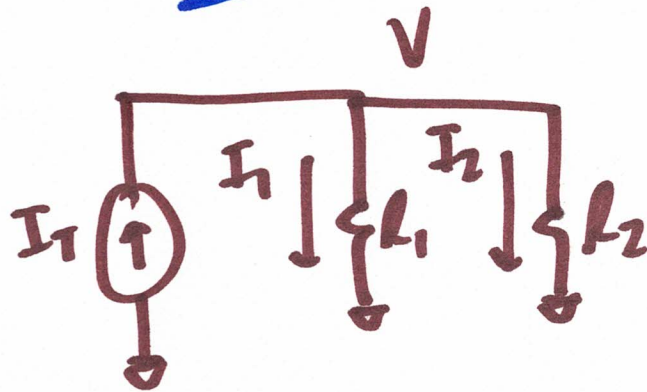

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2}$$


$$V = I_T \cdot \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right)$$

$$I_1 = \frac{I_T \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}}{R_1}$$



$$\underline{I_1} = I_T \cdot \frac{R_2}{R_1 + R_2}$$
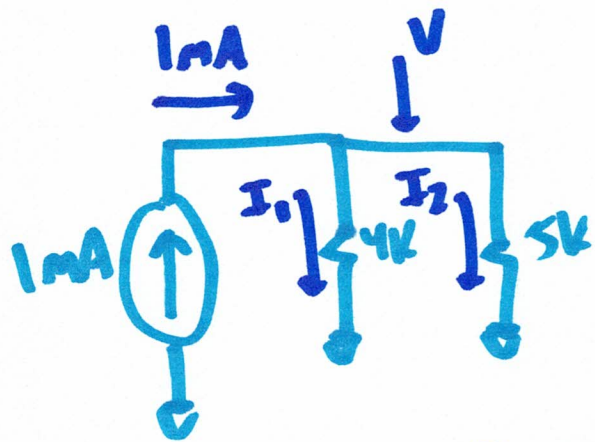
$$\underline{I_2} = I_T \cdot \frac{R_1}{R_1 + R_2}$$



$$I_1 = 1\text{mA} \cdot \left[\frac{5\text{k}}{9\text{k}} \right]$$

$$\underline{I_1 = 0.555\text{mA}}$$

$$\underline{I_2 = 1\text{mA} \left[\frac{4\text{k}}{9\text{k}} \right] = 0.444\text{mA}}$$

