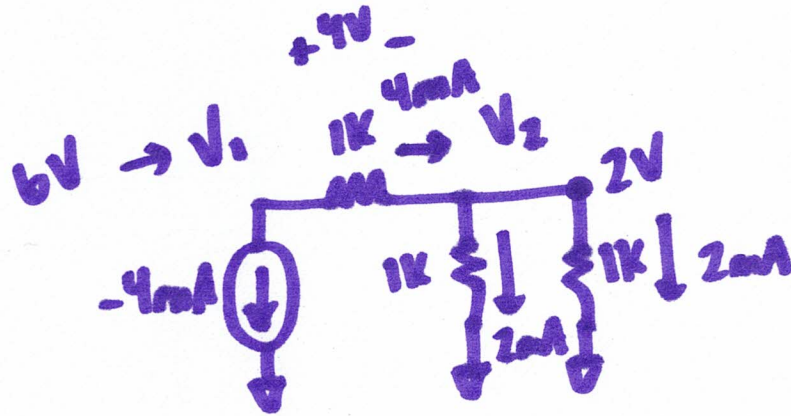



# EE 220: Circuits I

HW 4: 2C



$$\frac{1}{3k} + \frac{1}{3k} + \frac{1}{3k} = \frac{1}{R_{eq}}$$

$$R_{eq} = 1k$$

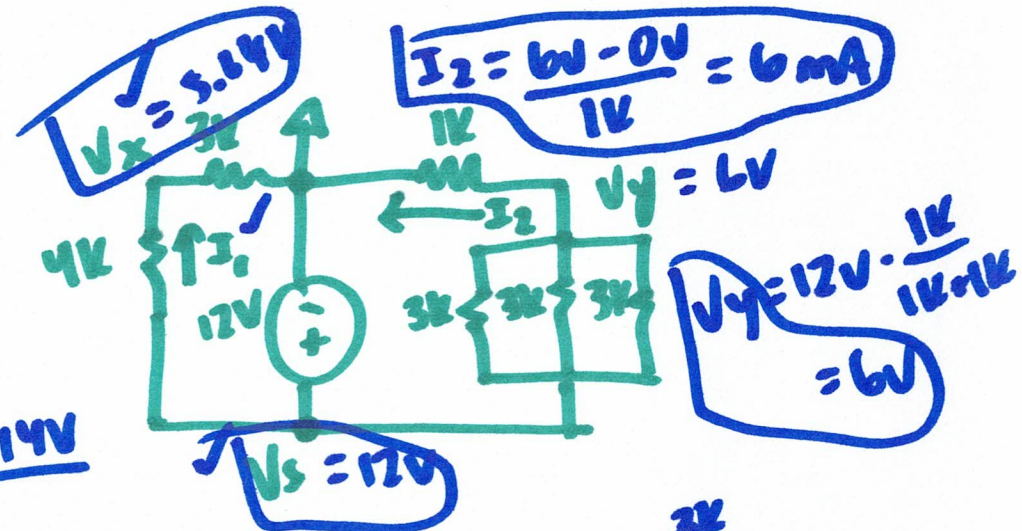




$$I_1 = \frac{12V - 5.14V}{4k}$$

$$I_1 = 1.71mA$$

$$V_x = V_s \cdot \frac{3k}{4k+3k}$$

$$V_x = 12V \cdot \frac{3}{7} = 5.14V$$

# superposition

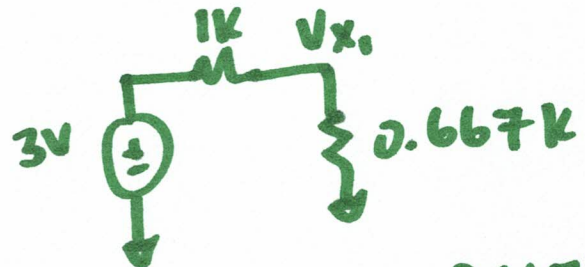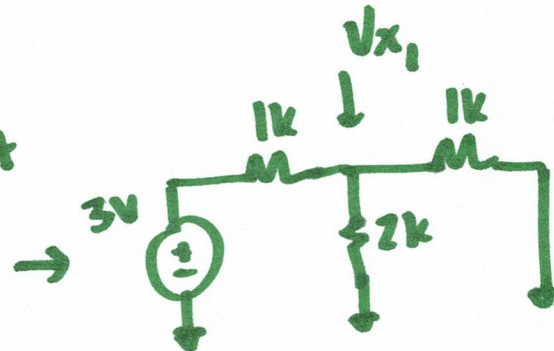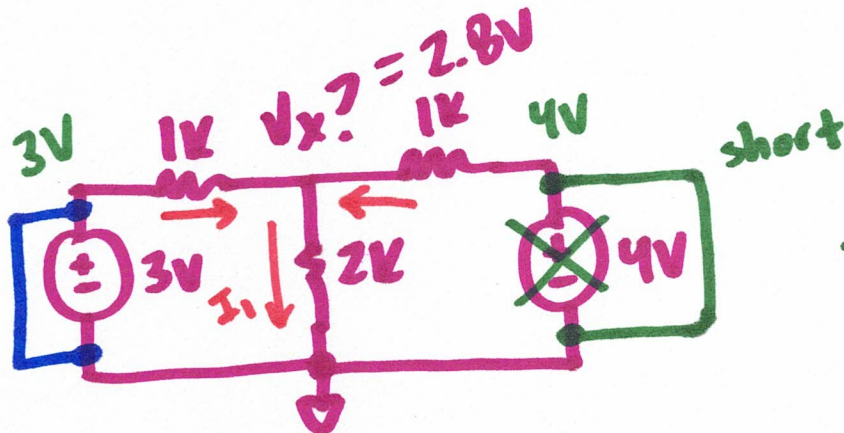

$$V_{x_1} = 3V \left( \frac{0.667k}{1k + 0.667k} \right)$$


$$V_{x_1} = 1.2V$$

$$I_1 = \frac{2.8V - 0V}{2k}$$

$$I_1 = 1.4mA$$

$$V_x = V_{x_1} + V_{x_2}$$





$$V_x = 1.2V + 1.6V = 2.8V$$

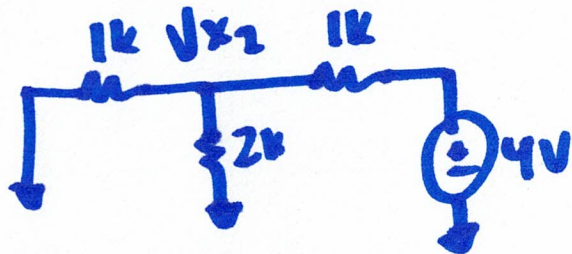

$$V_{x_2} = 4V \cdot \left( \frac{0.667k}{1k + 0.667k} \right)$$


$$V_{x_2} = 1.6V$$

(Ex2)

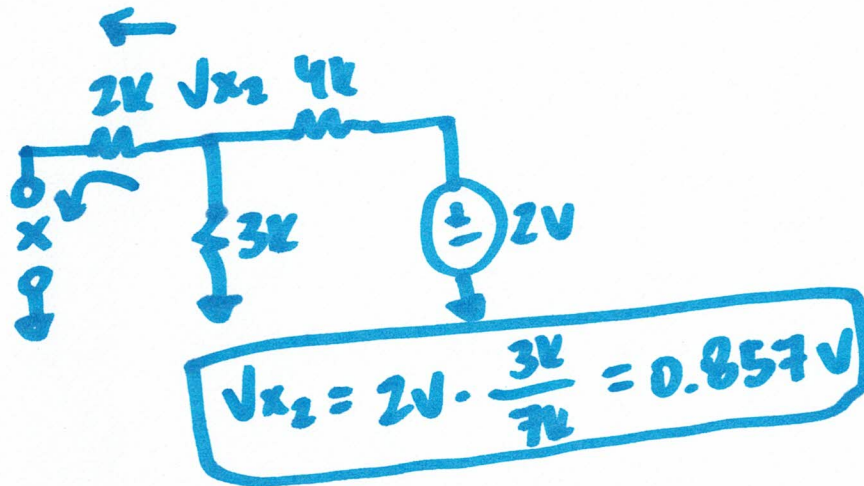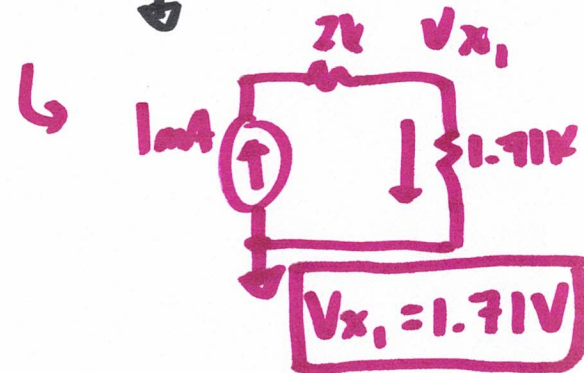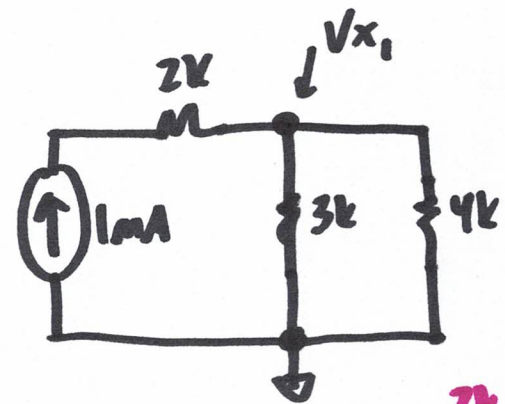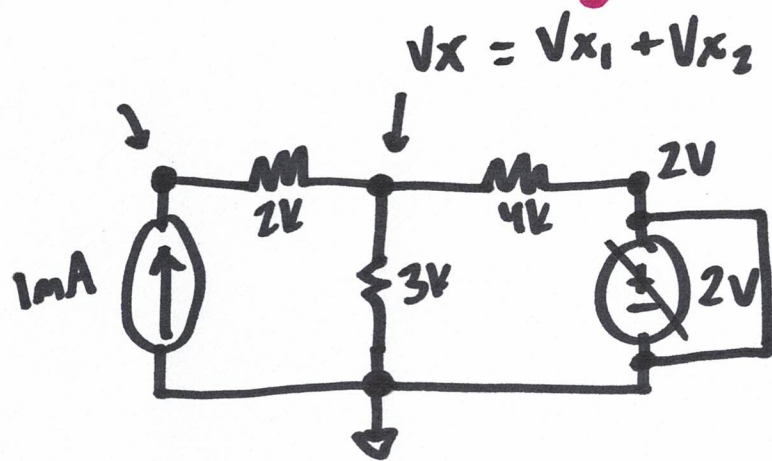


$$V_x = V_{x_1} + V_{x_2} = 1.71V + 0.857V$$

$$V_x = 2.567V$$

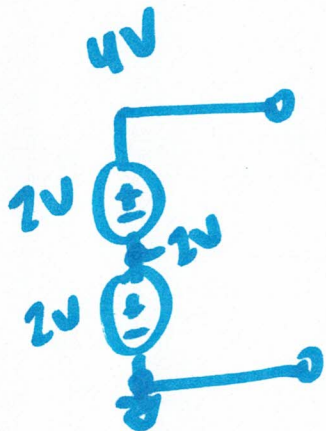

# mesh analysis → uses KVL

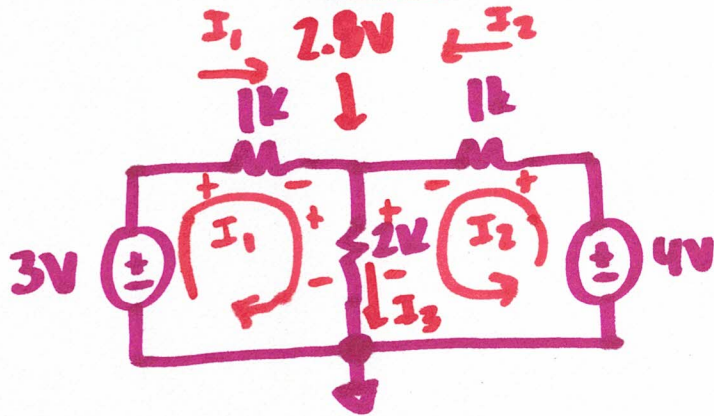

$$\textcircled{1} \quad +3V - I_1 \cdot 1k - (I_1 + I_2) \cdot 2k = 0 \rightarrow 3V - I_1 \cdot 1k - I_1 \cdot 2k - I_2 \cdot 2k = 0$$

$$\textcircled{2} \quad +4V - I_2 \cdot 1k - (I_1 + I_2) \cdot 2k = 0 \rightarrow 4V - I_2 \cdot 1k - I_1 \cdot 2k - I_2 \cdot 2k = 0$$

$$\rightarrow 3V - I_1 \cdot 3k - I_2 \cdot 2k = 0$$

$$\frac{3V - I_1 \cdot 3k}{2k} = \frac{I_2 \cdot 2k}{2k}$$

$$I_2 = 1.5mA - 1.5 \cdot I_1$$

$$I_2 = 1.5mA - 1.5(0.2mA)$$

$$I_2 = 1.2mA$$

$$\rightarrow 4V - I_2 \cdot 3k - I_1 \cdot 2k = 0$$

$$4V - [1.5mA - 1.5I_1] \cdot 3k - I_1 \cdot 2k = 0$$

$$4V - 4.5V + 4.5k \cdot I_1 - I_1 \cdot 2k = 0$$

$$-0.5V + 2.5kI_1 = 0$$

$$\frac{2.5kI_1}{2.5k} = \frac{0.5V}{2.5k}$$

$$I_1 = 0.2mA$$

$$I_3 = 1.4mA$$