

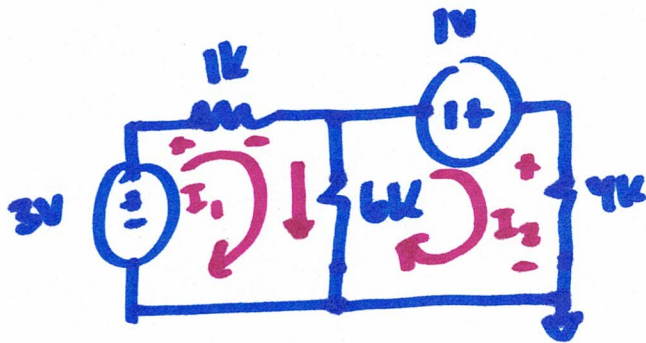


# EE 220: Circuits I

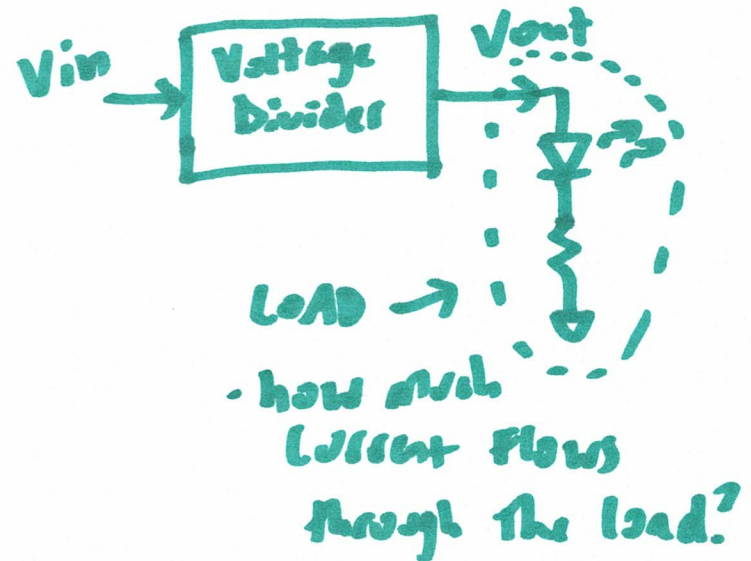


$$\textcircled{1} \quad +3V - I_1 \cdot 1k - (I_1 - I_2) \cdot 6k = 0$$
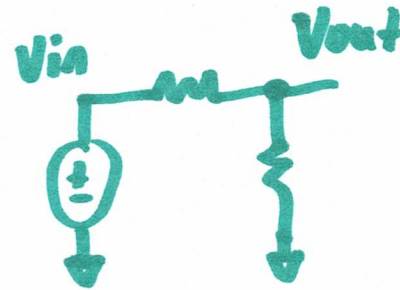
$$\textcircled{2} \quad +1V - I_2 \cdot 4k - (I_2 - I_1) \cdot 6k = 0$$




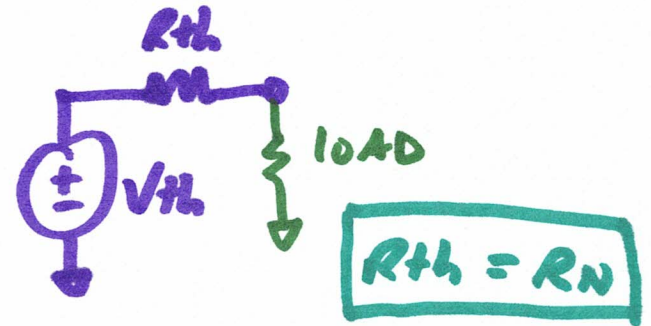
# Thevenin & Norton Equiv. CKts


• Thevenin: any linear circuit  $\rightarrow$



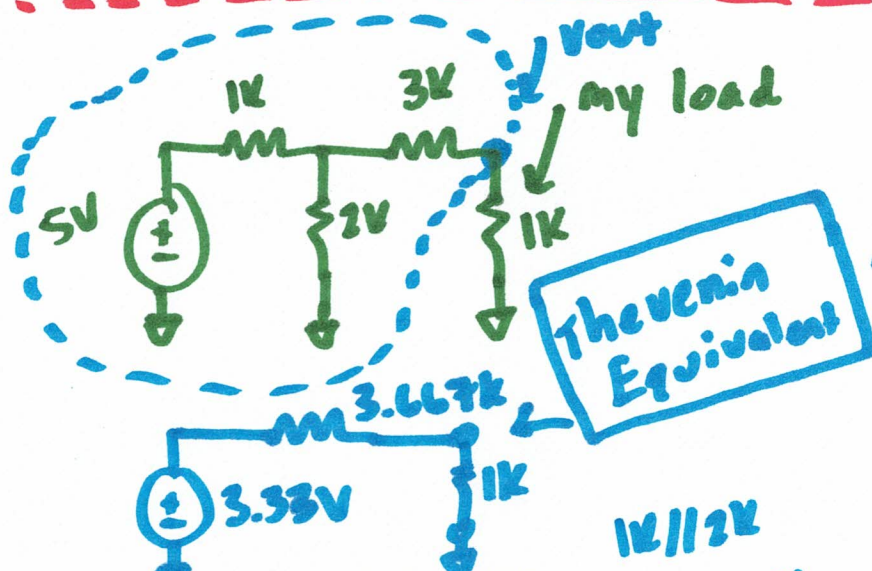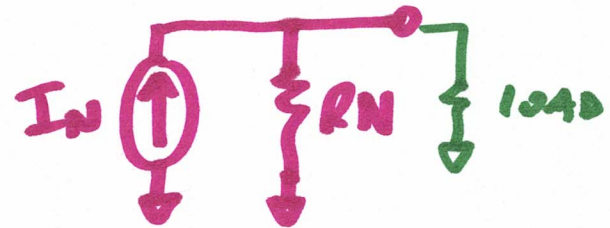
• Norton: any linear circuit  $\rightarrow$




1. Find thevenin voltage

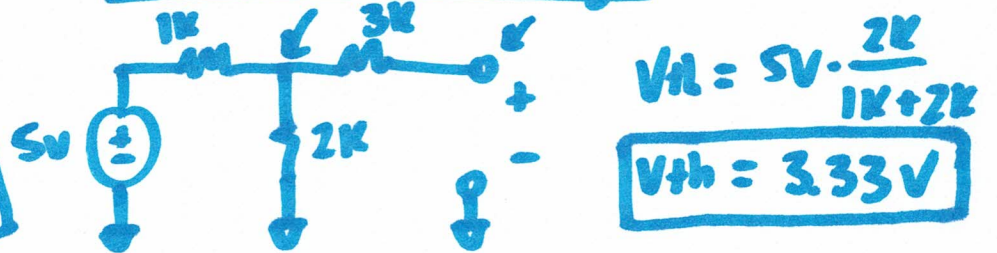


2. Find thevenin resistance

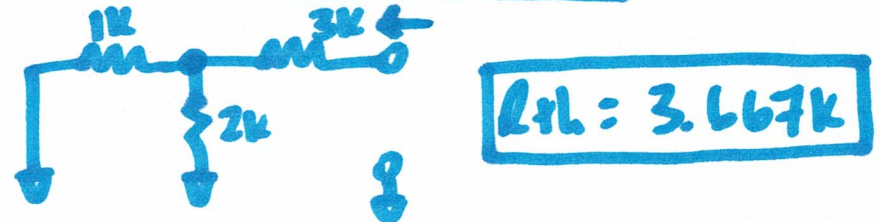

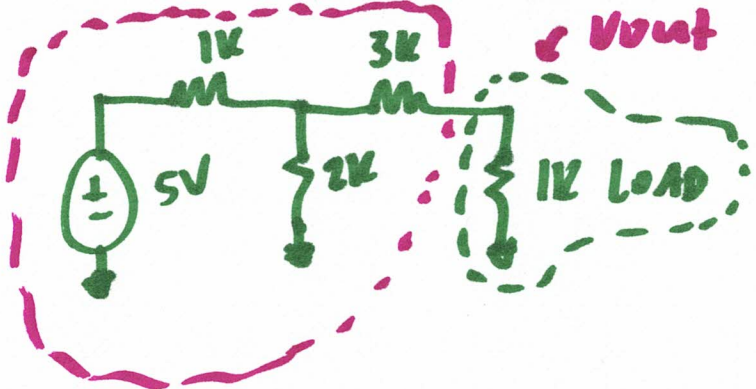
$$1k \parallel 2k = \frac{1k \cdot 2k}{1k + 2k}$$



Norton equivalent

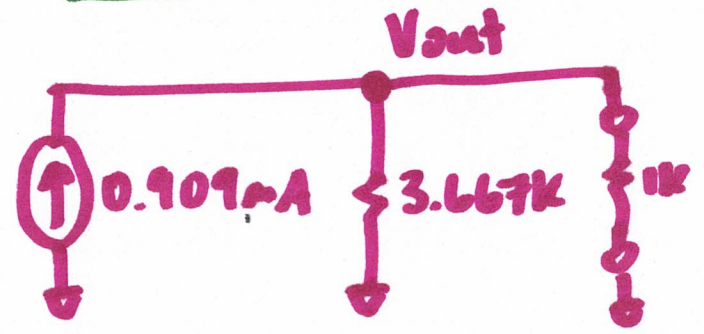

1.) Norton current

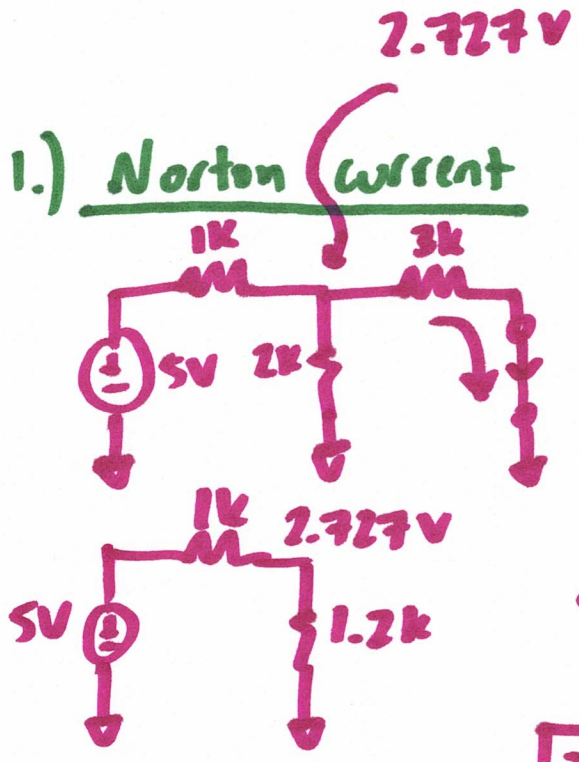





$3k // 2k = 1.2k$

$5 \cdot \frac{1.2}{2.2} = \frac{2.727V}{3k}$

$I_N = 0.909mA$

$R_N = R_N = 3.667k$



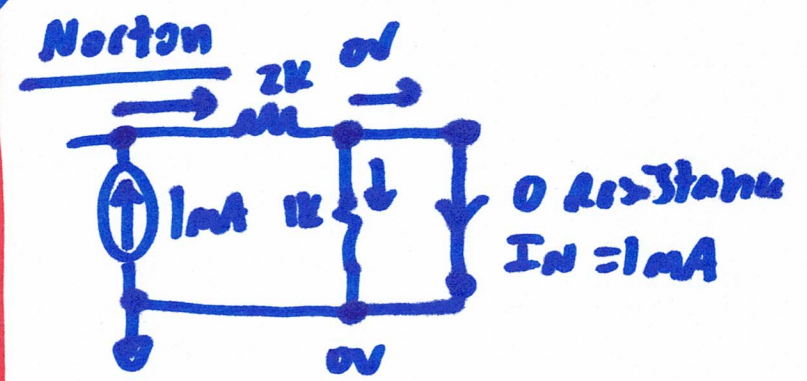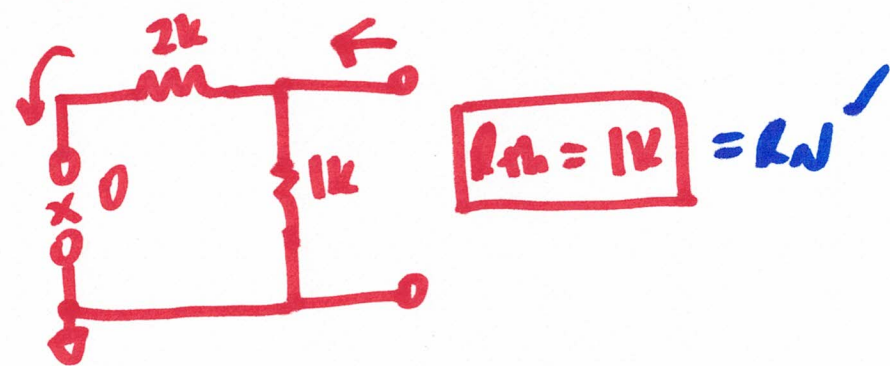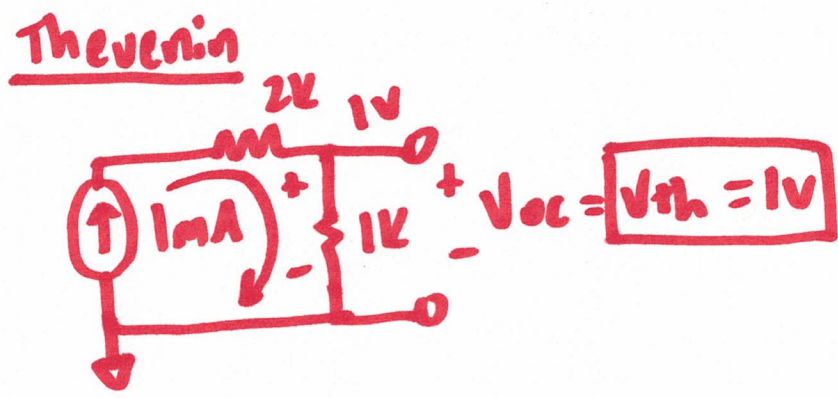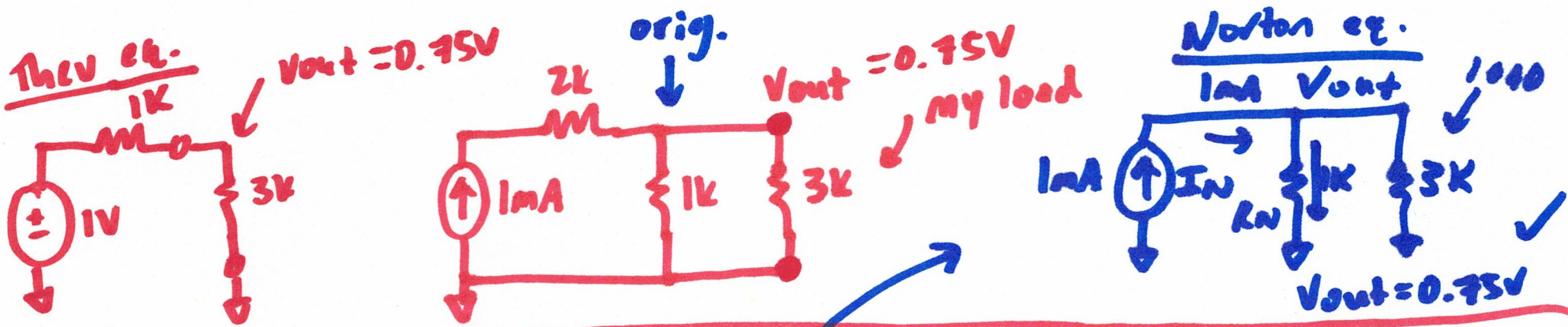

$I_T = 1mA$


$I(1k) = 1mA \cdot \frac{3k}{4k} = 0.75mA$

## When finding:


### 1. Thevenin voltage



### 2. Norton current

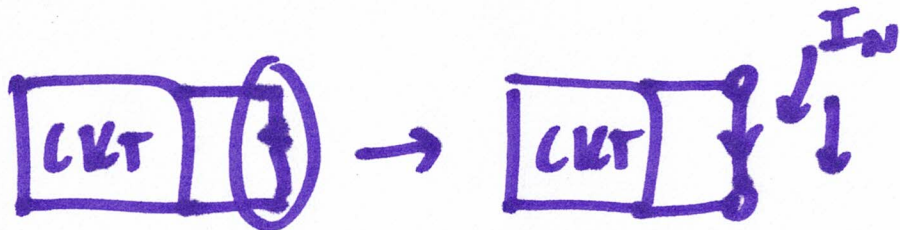

### 3. Thevenin/Norton Resistance

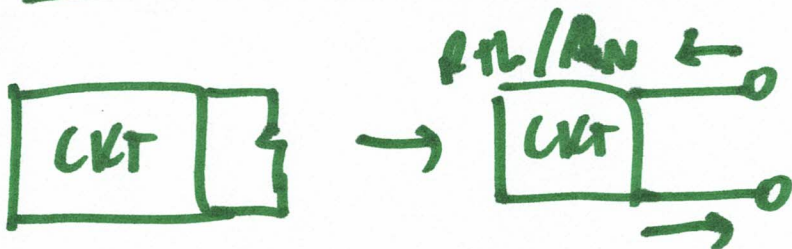

## Do:

1. Find the voltage across the load terminals with load resistor removed. (open)
2. Find the current through the load terminals with load resistor removed (short)
3. Get rid of all power sources (short across  $V_{source}$ , open  $I_{source}$ ) find resistance between the two load terminals.