

James Skelly

EE 420: Analog IC Design

Dr. R. Jacob Baker

Low Voltage, High Gain Op Amp Design

The voltage, current, and sizing parameters recorded in the table below were carefully selected with the goal of designing a low voltage (down to $V_{DD} = 2V$), high gain op-amp in mind.


MOSFET Parameters for Low Voltage, High Gain Op-Amp Design			
$V_{DD} = 2V$			
C5 Process, Scale Factor = 600 nm			
Parameter	NMOS	PMOS	Comments
Bias Current, I_D	10 μ A	10 μ A	Approximate
W/L	120/2	300/2	Selected based on I_D , V_{OV}
Actual W/L	72 μ m/1.2 μ m	180 μ m/1.2 μ m	W/L * 600 nm
$V_{DS,SAT} / V_{SD,SAT}$	50 mV	50 mV	Overdrive Voltage (V_{OV})
V_{GS} / V_{SG}	750 mV	970 mV	Gate-Source / Source-Gate Voltage
V_{THN} / V_{THP}	700 mV	920 mV	Threshold Voltage
KP_n / KP_p	133 μ A/ V^2	333 μ A/ V^2	Transconductance Parameter
t_{ox}	139 Å	139 Å	Oxide Thickness
$C'_{ox} = \epsilon_{ox}/t_{ox}$	2.5 nF/ μ m ²	2.5 nF/ μ m ²	$C_{ox} = C'_{ox}WL \cdot (\text{scale})^2$
C_{oxn} / C_{oxp}	216 nF	540 nF	Oxide Capacitance
C_{gsn} / C_{sgp}	144 nF	360 nF	$C_{gs} = (2/3)C_{ox}$
C_{gdn} / C_{dgp}	200 pF	290 pF	From C5 Model Text File
g_{mn} / g_{mp}	227 μ A/V	206 μ A/V	Transconductance
r_{on} / r_{op}	847 k Ω	671 k Ω	$I_D = 10\mu$ A
$g_{mn} r_{on} / g_{mp} r_{op}$	192.3	138.2	Open Circuit Gain
λ_n / λ_p	0.118 V^{-1}	0.149 V^{-1}	Channel Length Modulation Parameter

Summary of Op-Amp Performance				
Specification	VDD = 2V Load = 1kΩ	VDD = 2V Load = 100pF	VDD = 5V Load = 1kΩ	VDD = 5V Load = 100pF
DC Open Loop Gain	96.1 dB	106.8 dB	98.4 dB	106.2 dB
Unity Gain Frequency (f_{un})	3.65 MHz	4.98 MHz	8.16 MHz	8.45 MHz
Phase Margin	94.4°	30.1°	86.6°	24.2°
CMRR ($f = 100kHz$)	111.1 dB	97.6 dB	118.6 dB	102.1 dB
No Load				
	VDD = 2V	VDD = 3V	VDD = 4V	VDD = 5V
PSRR+ ($f = 1kHz$)	79.7 dB	76.1 dB	74.7 dB	73.3 dB
PSRR- ($f = 1kHz$)	68.2 dB	70.0 dB	71.0 dB	71.9 dB
Input CMR				
	CMR _{MIN} = 850 mV		CMR _{MAX} = VDD + 650 mV	
Output Swing (Saturation Region)				
	V _{OUT,MAX} = VDD – 50 mV		V _{OUT,MIN} = 50 mV	
Slew Rate (Max Load)				
	VDD = 2V	1.28 V/μs	VDD = 5V	1.72 V/μs
No Load				
	VDD = 2V	VDD = 3V	VDD = 4V	VDD = 5V
Power Dissipation (Average)	1.53 mW	2.92 mW	4.64 mW	6.84 mW

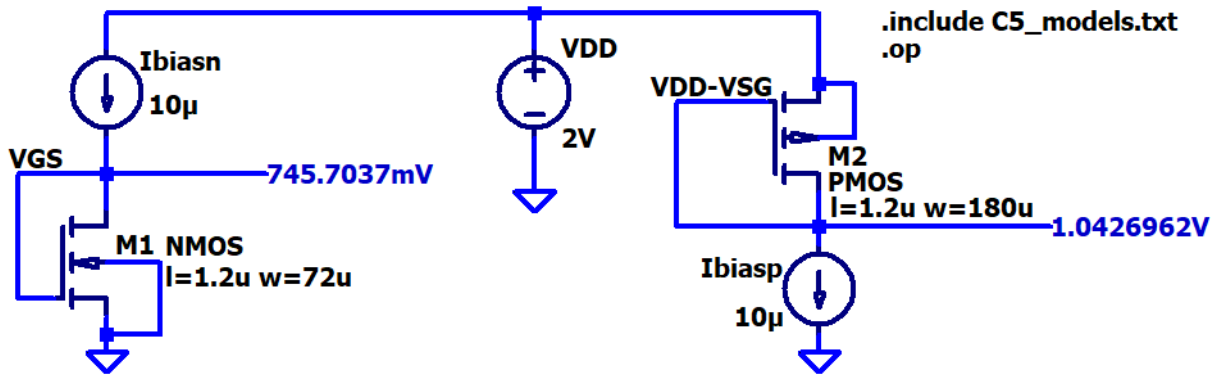**** Max Load is 100pF capacitor in parallel with 1k resistor**

Selecting Transistor Sizes


The schematic shown in the figure below was drafted to select the sizes based on desired drain current and overdrive voltage. Aiming for an overdrive voltage that is 2.5% of VDD when VDD = 2V, and when the drain current through the devices is 10μA, the sizes were chosen, as seen in the figure, to be $W_n/L_n = 120/2$ and $W_p/L_p = 300/2$, with a scale factor of 600 nm (see **MOSFET Parameters** table above). Transistors with these geometries were then used to construct current mirrors, produce reference voltages for biasing, and construct the op-amp.



Schematic Drafted to Selected MOSFET Sizes

Generating Reference Voltages for Biasing

The Beta Multiplier Reference

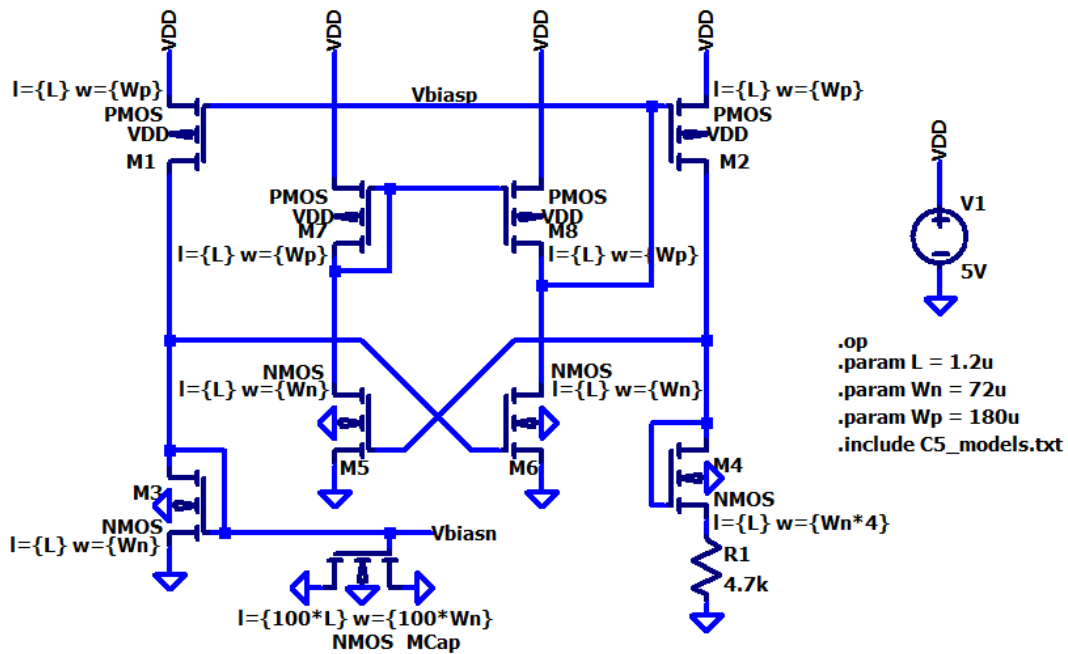


Beta Multiplier Reference Circuit (Startup Circuit Omitted)

The beta multiplier reference was designed with a differential amplifier in order to hold the drain voltages of M3 and M4 at the same potential, and therefore, to achieve better matching. The transistor sizes used in the BMR were also used throughout the rest of the biasing circuit.

A startup circuit was also included, but was omitted from the figure above to save space.


A MOSFET capacitor is connected to the bias voltage Vbiasn to improve stability. Keeping Vbiasn stable is very important here because it is the basis for the entire biasing circuit. The biasing circuit consists of current mirrors that source and sink constant currents, and therefore produce constant voltages. The reference voltages used to bias the op-amp were generated by the circuit seen below. Note the longer L PMOS device M1, which was sized to select Vhigh (VSD,SAT), and the longer L NMOS device MWS1, which was sized to select Vlow (VDS,SAT). Notice that the PMOS bodies are tied to their sources to eliminate body effect.

Biasing Circuit

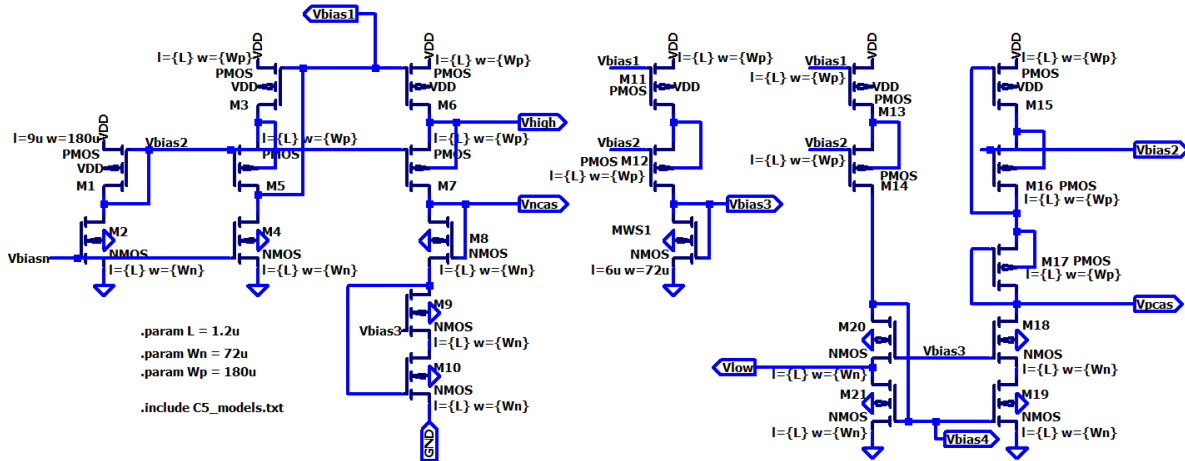


Biasing Circuit (Beta Multiplier used to generate Vbiasn, not pictured here)

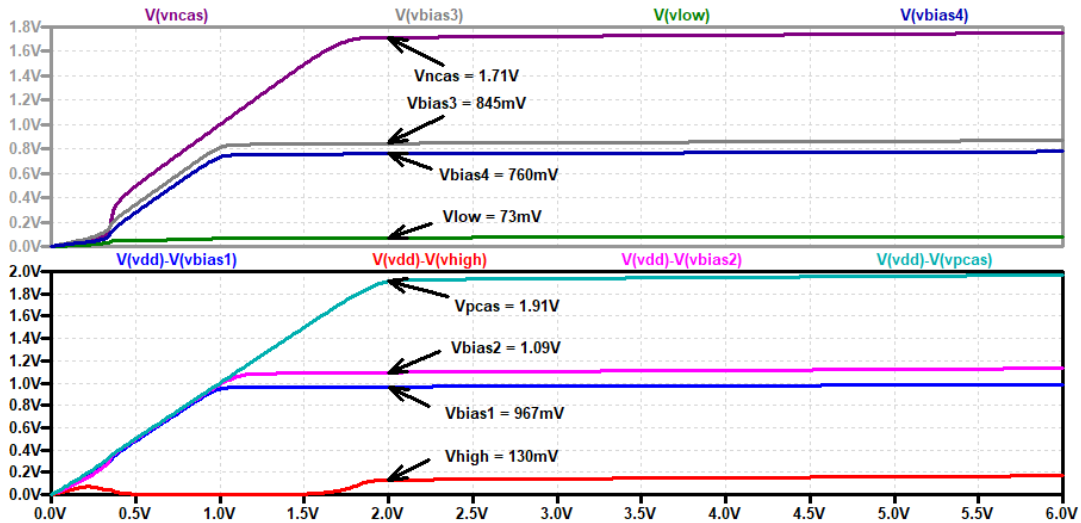We can observe from the plot below that as VDD changes, the bias voltages remain reasonably constant from VDD = 2V to VDD = 6V. This will allow for consistent performance of our op-amp even with large variations in power supply voltage. VDD is subtracted out of the PMOS-generated reference voltages because they are dependent upon VDD.



Sweeping VDD from 0V to 6V, Plotting Reference Voltages

Designing the Op-Amp

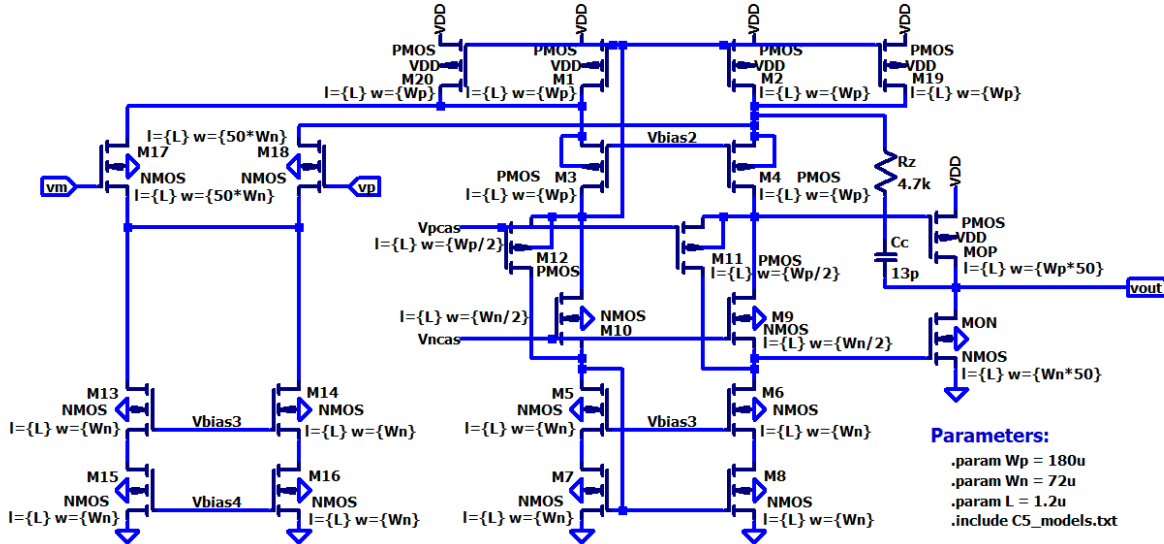


Folded-Cascode Op-Amp with Class AB Output Buffer, NMOS Differential Amplifier Input Stage

Design Tradeoffs	
Category	Description of Tradeoff
MOSFET W/L Sizing	<ul style="list-style-type: none"> The NMOS were chosen to have $W/L = 120/2$. The PMOS were chosen to have $W/L = 300/2$. Pros: $L = 2$ limits current, enhances gain. Lower power consumption. Cons: Larger layout size, slower step response/slew rate.
Overdrive Voltage	<ul style="list-style-type: none"> V_{ov} for NMOS and PMOS devices was selected to be 50mV. Pros: Operation down to $VDD = 2V$, limited channel length modulation. Cons: Operating close to border of saturation and triode.
Op-Amp Topology	<ul style="list-style-type: none"> Folded-Cascode topology w/ class AB output buffer was used. Pros: Floating current sources for reduction of input-referred offset voltage, cascode structure for higher output resistance. Cons: Larger layout size than other two-stage op-amp topologies, more current drawn in output stage.
Output Buffer	<ul style="list-style-type: none"> Wide W output buffer capable of driving necessary loads. Pros: Very smooth step response, reasonably fast slew rate, very small difference in performance based on load. Cons: Large layout size, giant increase in power consumption.

Calculating Input Common-Mode Range (CMR)

It is important to calculate the input common-mode range (CMR) of the op-amp in order to assure that the MOSFETs that make up the diff-amp (input stage) will operate in the saturation region. If the input signal exceeds the maximum common-mode voltage ($V_{CM,MAX}$), the transistors will move into the triode region, and behave like resistors. If the input signal falls below the minimum common mode voltage ($V_{CM,MIN}$), the transistors will turn off.

CMR_{MIN}

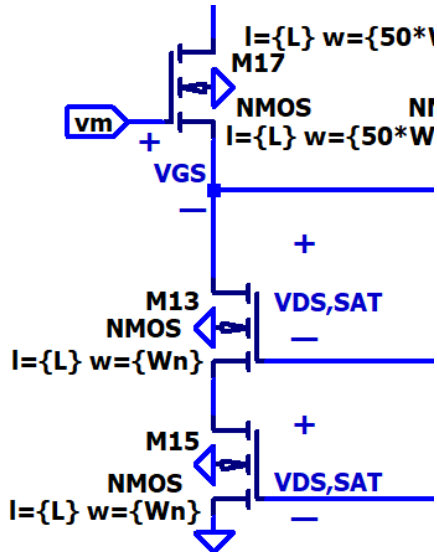


In order to calculate the minimum common-mode voltage of the diff-amp, we need to consider the minimum possible voltage across NMOS devices M13 and M15 (left). In order for the devices to operate in the saturation region, their drain-to-source voltages must be **at least** $V_{DS,SAT}$. In order for device M17 to be on, the gate-to-source voltage must be greater than the threshold voltage. Therefore, we can write the equation for $V_{CM,MIN}$ as

$$V_{CM,MIN} = (2 * V_{DS,SAT}) + V_{GS}$$

Substituting values from the table of parameters,

$$V_{CM,MIN} = (2 * 50mV) + 750mV = 850mV$$

CMR_{MAX}

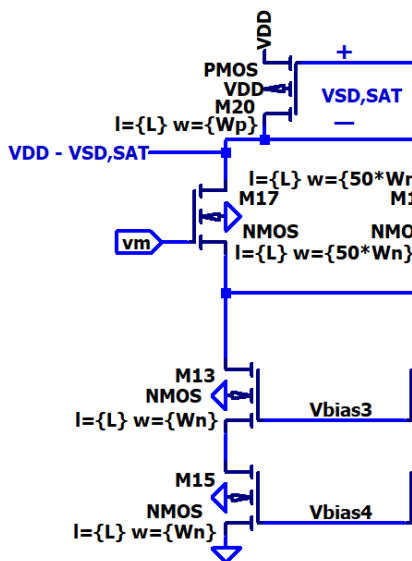

In order for M17 to stay in saturation,

$$V_{DS} \geq V_{GS} - V_{THN}$$

We can cancel out the source voltage V_s and rewrite as

$$V_D \geq V_G - V_{THN}$$

Since a $V_{SD,SAT}$ is dropped across M20 (left), the drain voltage of M17 can be written (as shown) as

$$V_D = V_{DD} - V_{SD,SAT}$$


$$V_{DD} - V_{SD,SAT} \geq V_G - V_{THN}$$

$$V_{DD} - V_{SD,SAT} + V_{THN} \geq V_G$$


$$V_G = V_{CM,MAX} = V_{DD} + 650mV$$

Op-Amp Simulation Results


Frequency Response

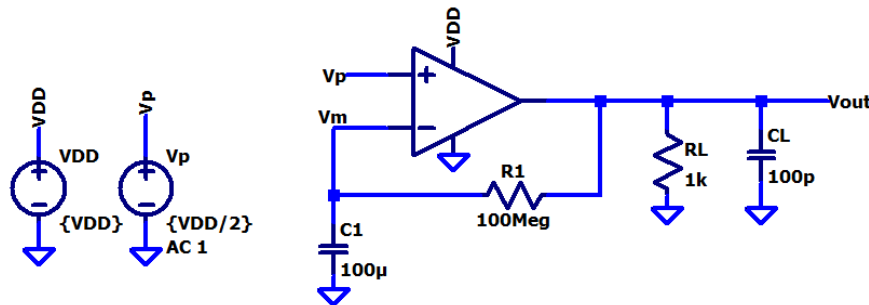

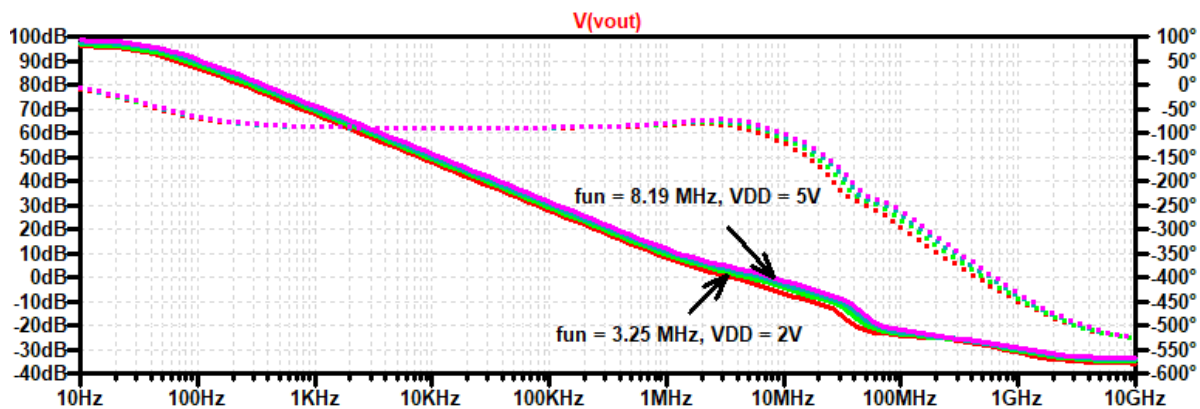
Shown above is the schematic used to generate the frequency response simulations below. A symbol of the op-amp was generated in LTspice in order to create more concise schematics for testing. The frequency response simulations below include results when the op-amp is driving a purely resistive load (1k), a purely capacitive load (100pF), and both resistive and capacitive.



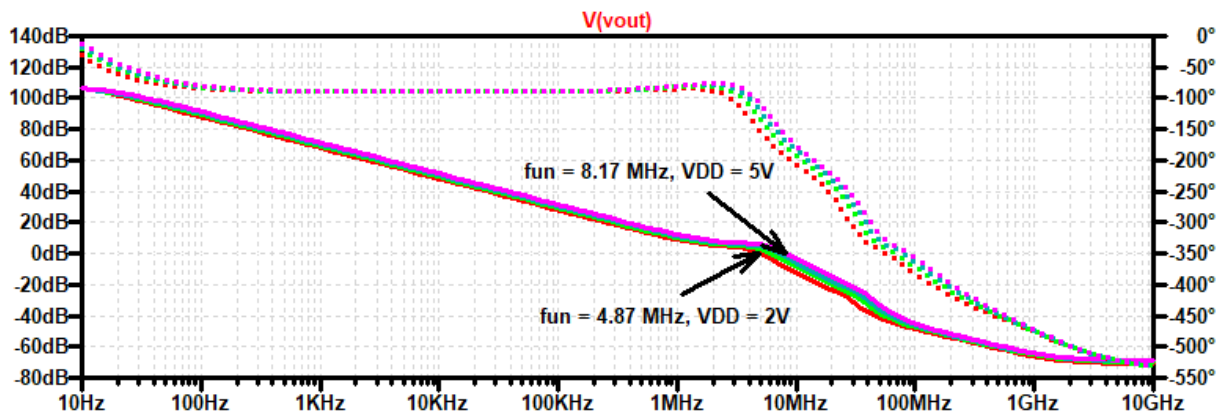AC Analysis for Op-Amp Driving Purely Resistive 1k Load. VDD Parameter Step from 2V to 5V in 1V Increments




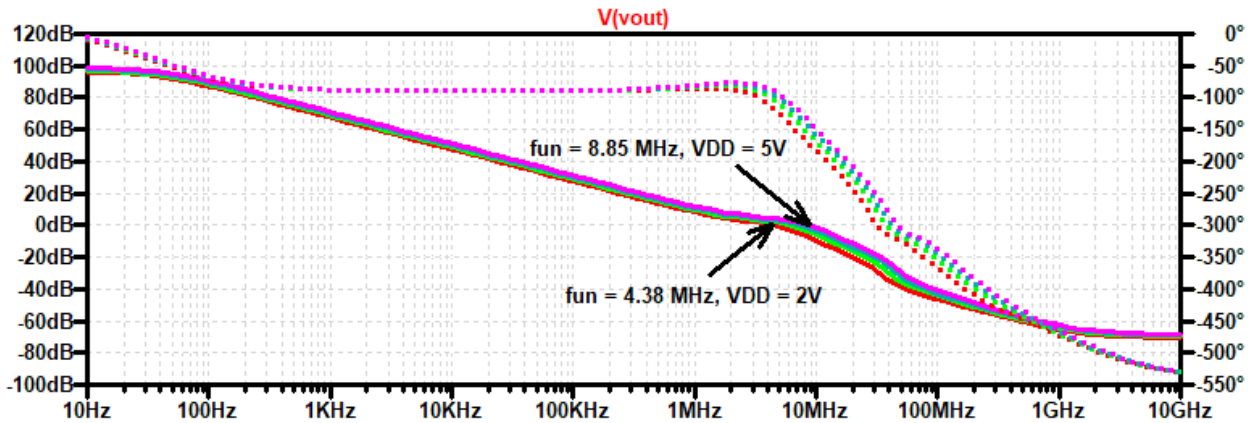AC Analysis for Op-Amp Driving Purely Capacitive 100pF Load. VDD Parameter Step from 2V to 5V in 1V Increments



Op-Amp Driving 1k Resistive Load & 100pF Capacitive Load. VDD Parameter Step from 2V to 5V in 1V Increments

Common-Mode Rejection Ratio (CMRR)

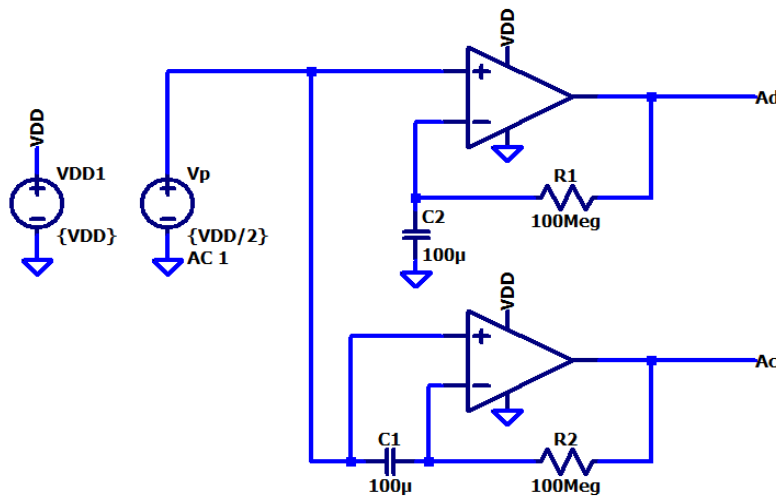


Schematic Used to Test CMRR of Op-Amp


The Common-Mode Rejection Ratio (CMRR) indicates how well the op-amp can filter out or “reject” noise that is applied to both input terminals. Observe the equation for CMRR below.

$$CMRR = 20 * \log \left| \frac{A_d}{A_c} \right| \quad (\text{eq. 22.27, CMOS Book})$$

In the above equation, A_d is the differential mode gain of the diff-amp, and A_c is the common-mode gain of the diff-amp. Since CMRR and common-mode gain are inversely proportional (logarithmically), killing the common-mode gain improves the CMRR. The input stage of the op-amp above consists of a differential amplifier in which each input terminal contains wide W NMOS devices ($m=50$). This increases the transconductance (g_m) of the input terminals, thereby decreasing the common-mode gain, and improving the CMRR. Simulation results for the CMRR are seen below.

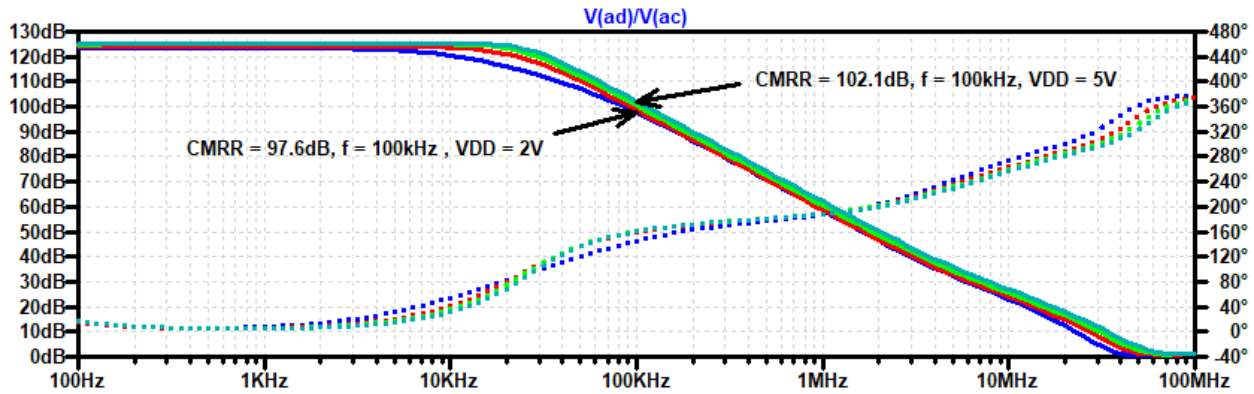


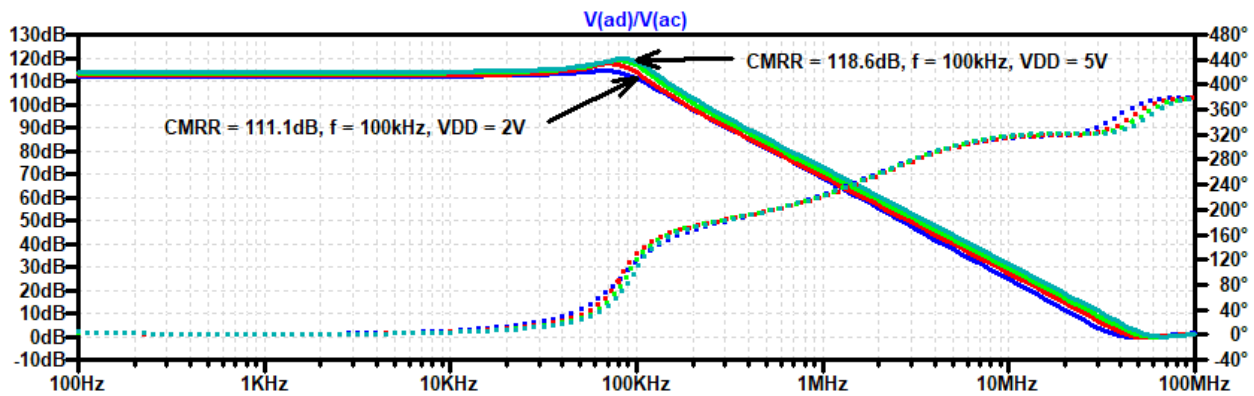CMRR Simulation for Op-Amp Driving 100pF Capacitive Load. VDD Parameter Step from 2V to 5V in 1V Increments



CMRR Simulation for Op-Amp Driving 1k Resistive Load. VDD Parameter Step from 2V to 5V in 1V Increments


Power Supply Rejection Ratio (PSRR)

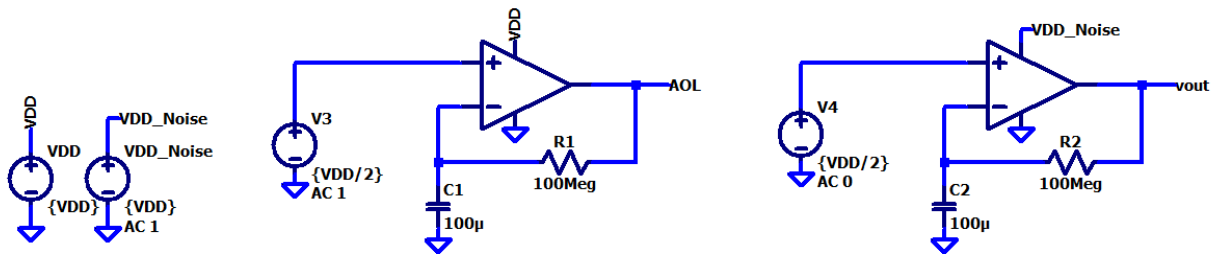

Schematic used to test positive PSRR of Op-Amp


The Power Supply Rejection Ratio (PSRR) defines how well an op-amp can reject noise on the VDD or ground power buses. The larger the PSRR, the better the op-amp rejects noise on these power buses. In the design of this op-amp, a compensation capacitor was connected from the output back to the PMOS devices in the folded-cascode in order to filter out noise and improve the positive PSRR. Simulation results for the positive and negative PSRR are seen below.

PSRR+

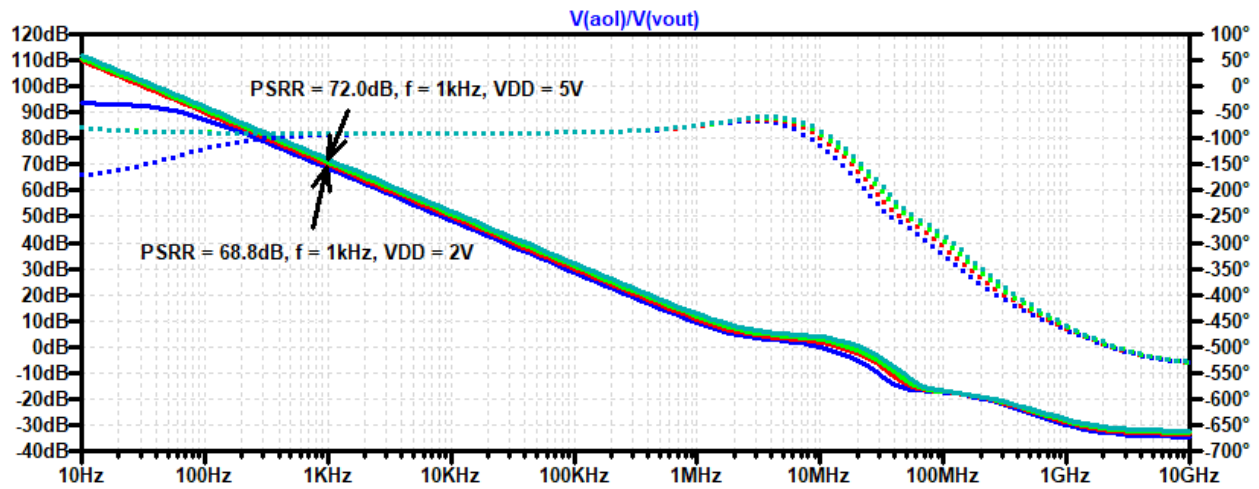


PSRR+ Simulation for Op-Amp with no load. VDD Parameter Step from 2V to 5V in 1V Increments

PSRR-

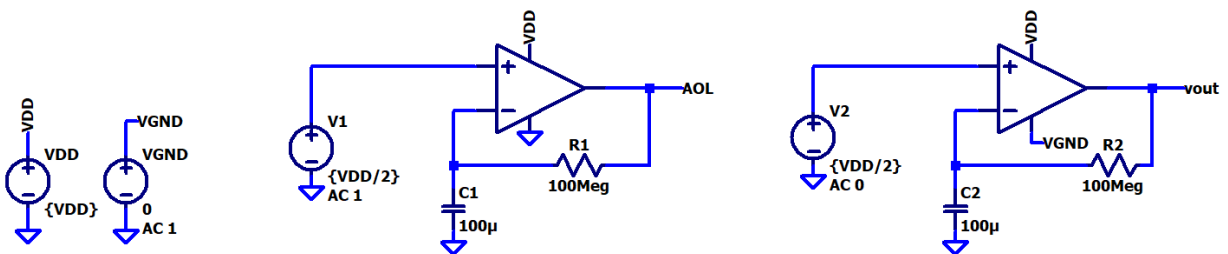


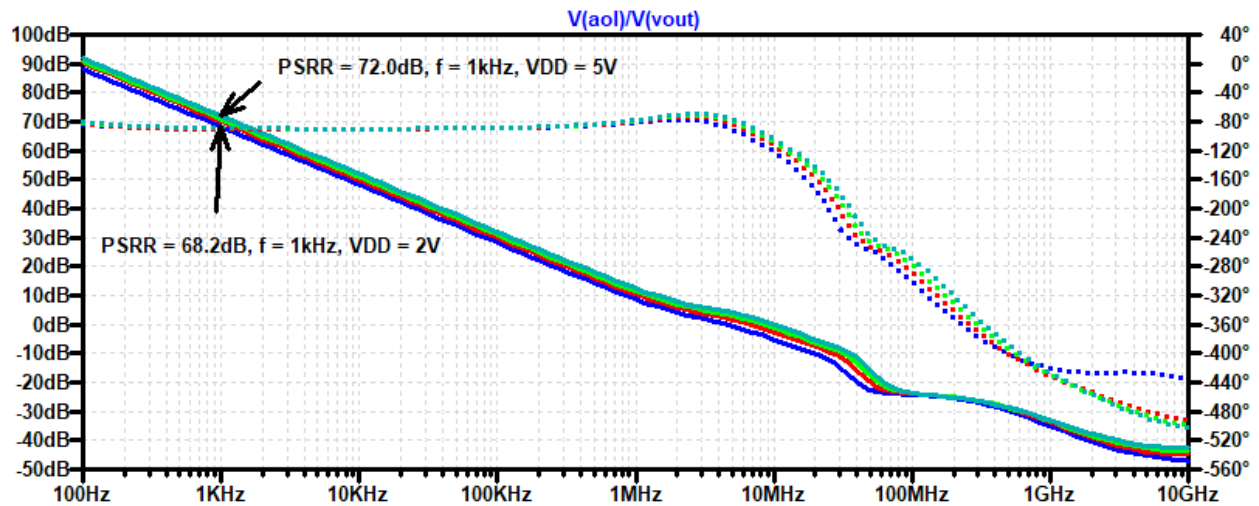Schematic used to test negative PSRR of Op-Amp




PSRR- Simulation for Op-Amp with no load. VDD Parameter Step from 2V to 5V in 1V Increments

Step Response (VDD = 5V)

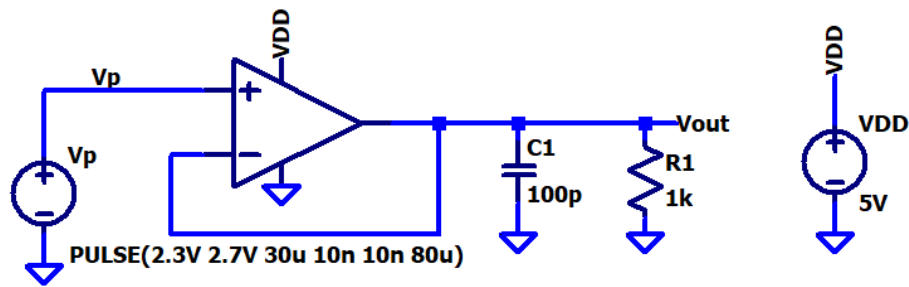


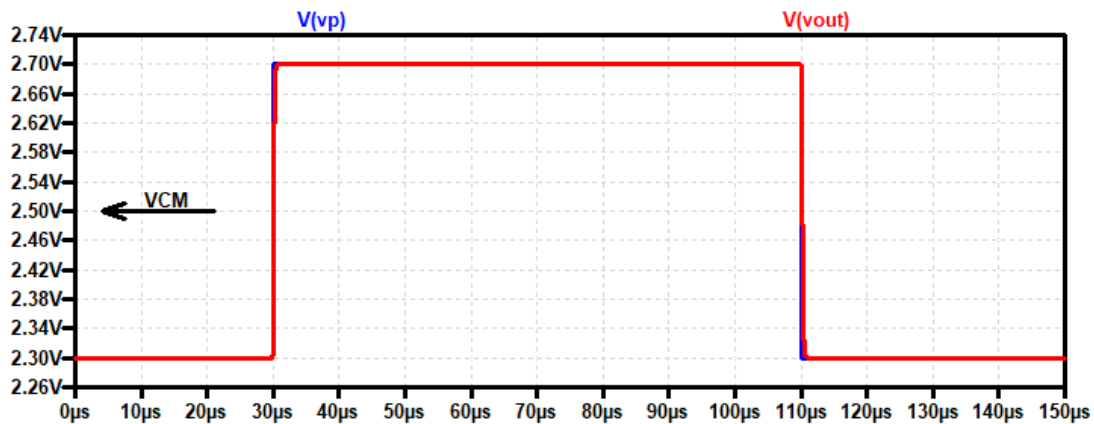Unity follower configuration to test step response, rise time, fall time



Step Response of Op-Amp with VDD = 5V, Driving maximum load

Correcting the step response of the op-amp required important design decisions and consideration of tradeoffs. The class AB amplifier used to drive the output signal is a good example. Designing the output stage with wide W ($m = 50$) drastically increases the power consumption of the op-amp. However, while having smaller W devices on the output stage may conserve power, the step response becomes slow and unstable. Observe the rising edge of the output signal below.

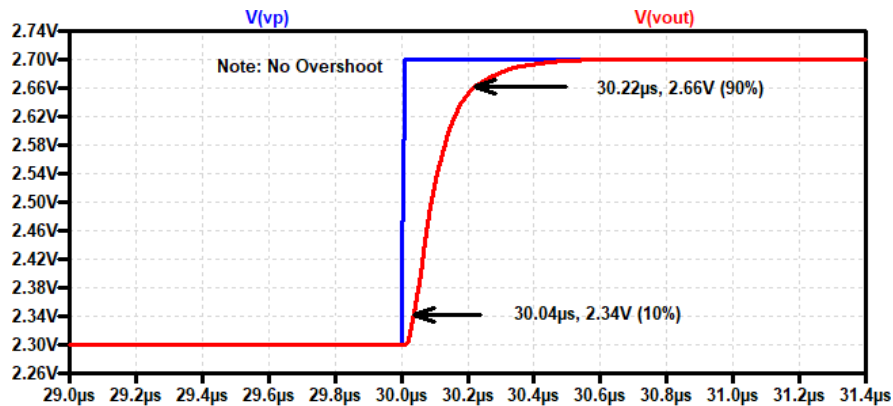


Zoomed-In View of Step Response to measure rise time

The rise time of the output signal can be calculated by

$$t_{rise} = t(90\%) - t(10\%) = 30.22\mu s - 30.04\mu s$$
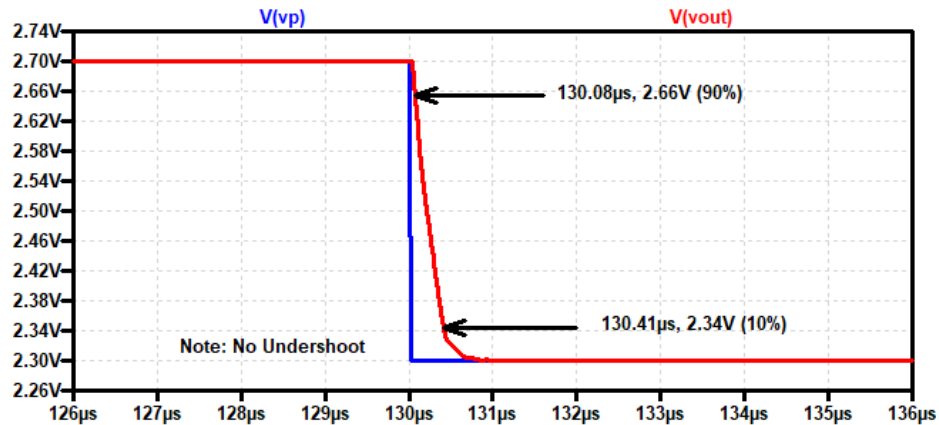
$$t_{rise} = 0.18\mu s = 180 \text{ ns}$$




Zoomed-In View of Step Response to measure fall time.

The fall time of the output signal can be calculated by

$$t_{fall} = t(10\%) - t(90\%) = 130.41\mu s - 130.08\mu s$$


$$t_{fall} = 0.33\mu s = 330 \text{ ns}$$

Step Response (VDD = 2V)

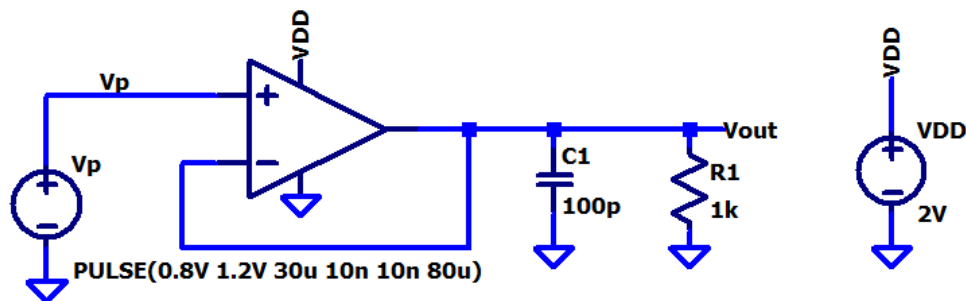


Unity follower configuration to test step response, rise time, fall time.

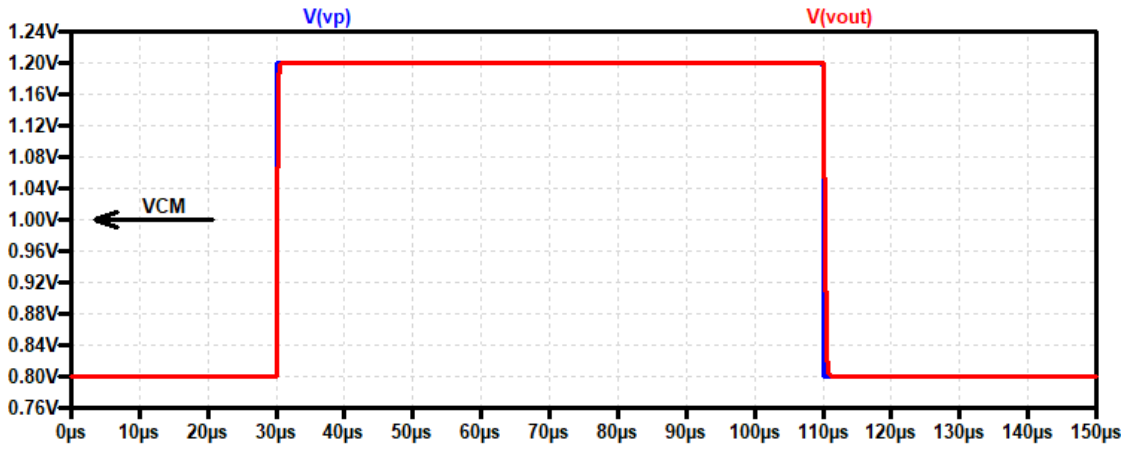The same configuration was used to test the step response of the op-amp when the power supply voltage is 2V. Simulation results are seen below.




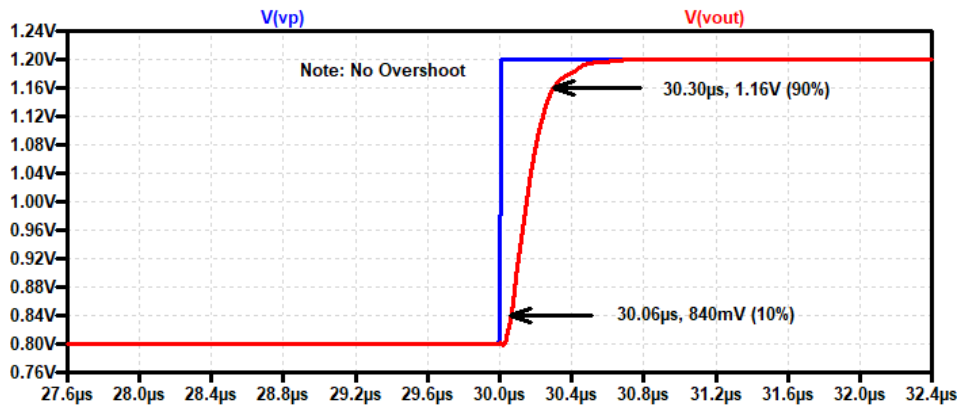Step Response of Op-Amp with VDD = 2V, driving max load



Zoomed-In View of Step Response to measure rise time.

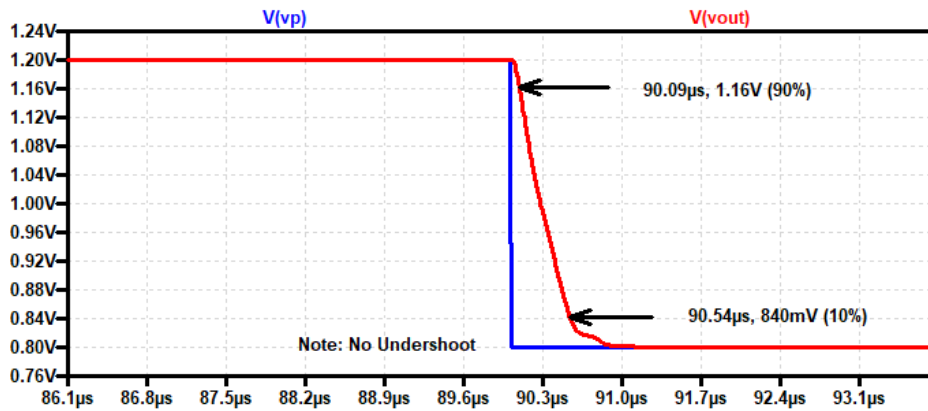
$$t_{rise} = 30.30\mu s - 30.06\mu s = 0.24\mu s = 240\text{ ns}$$



Zoomed-In View of Step Response to measure fall time.


$$t_{fall} = 90.54\mu s - 90.09\mu s = 0.45\mu s = 450\text{ ns}$$

Slew Rate

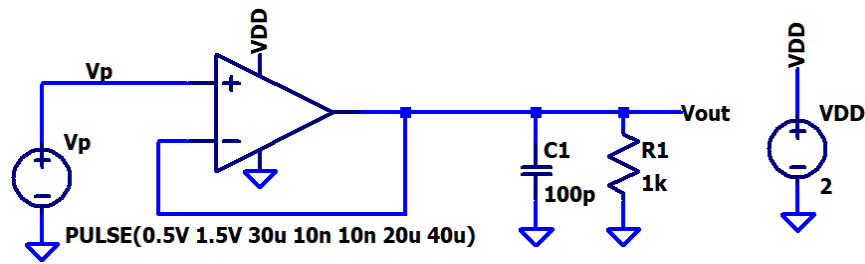

Unity Follower Configuration, IV change in input/output used to measure experimental slew rate while driving max load.

The slew rate of the op-amp defines how fast the output is capable of changing. In this design, the goal was to achieve a slew rate greater than or equal to 1 volt per microsecond. In other words, we want the output to be able to transition up or down 1V in one microsecond or less. Having a wide W output stage (our class AB amplifier is wide) improves slew rate because the wide W PMOS can source more current and the wide W NMOS can sink more current. Since the rate of change of voltage across a capacitor (dV/dt) is directly proportional to the current through the capacitor, increasing the amount of current that can flow through the capacitor naturally improves the rate of change of voltage across that capacitor. Since we are trying to drive a capacitive load, the rate of change of voltage across the load is equal to the slew rate. The slew rate in this design was limited by the output stage to lower the total power consumption. Observe the results of the simulation below.

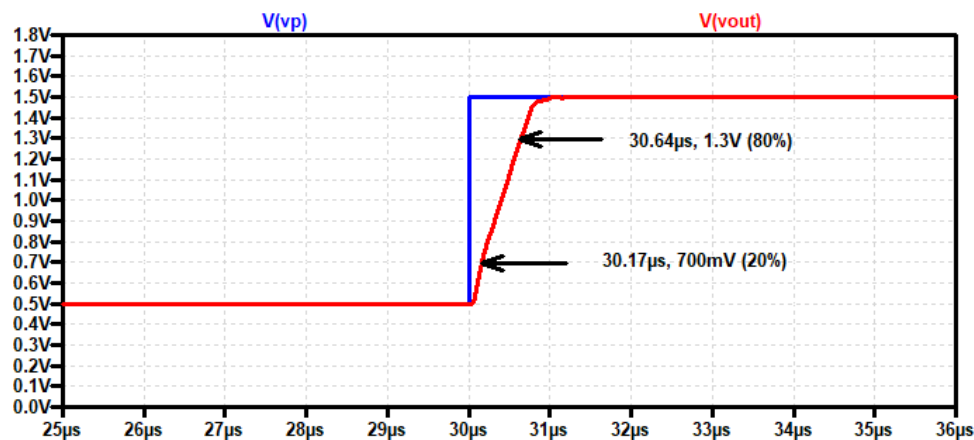


Measuring the slew rate of the op-amp. Slope of the output signal rising edge is measured from 20% to 80% of the signal.

$$\text{Slew Rate} = \frac{dV_{out}}{dt} = \frac{\Delta V_{out}}{\Delta t} = \frac{1.3V - 0.7V}{30.64\mu s - 30.17\mu s}$$

$$\text{Slew Rate} = 1.28 V/\mu s$$

Inverting Op-Amp Topology (VDD = 5V)

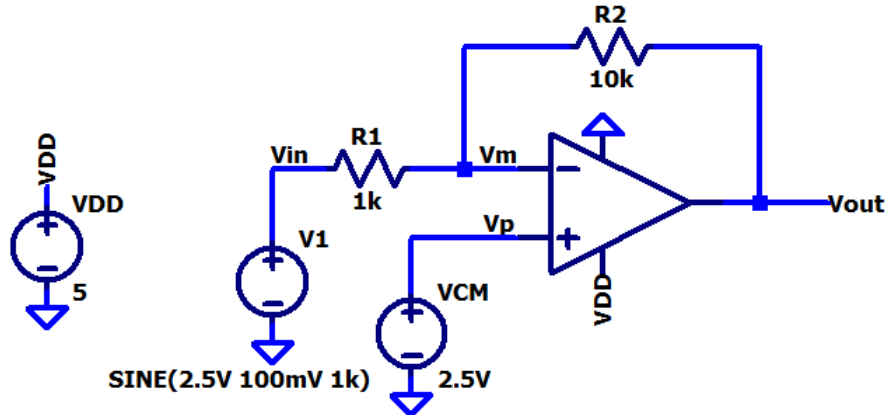


Schematic used to test operation of op-amp in the inverting topology with a gain of -10, VDD = 5V.

For the inverting op-amp topology, we know that the gain is equal to -1 multiplied by the ratio of R2 divided by R1, or

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

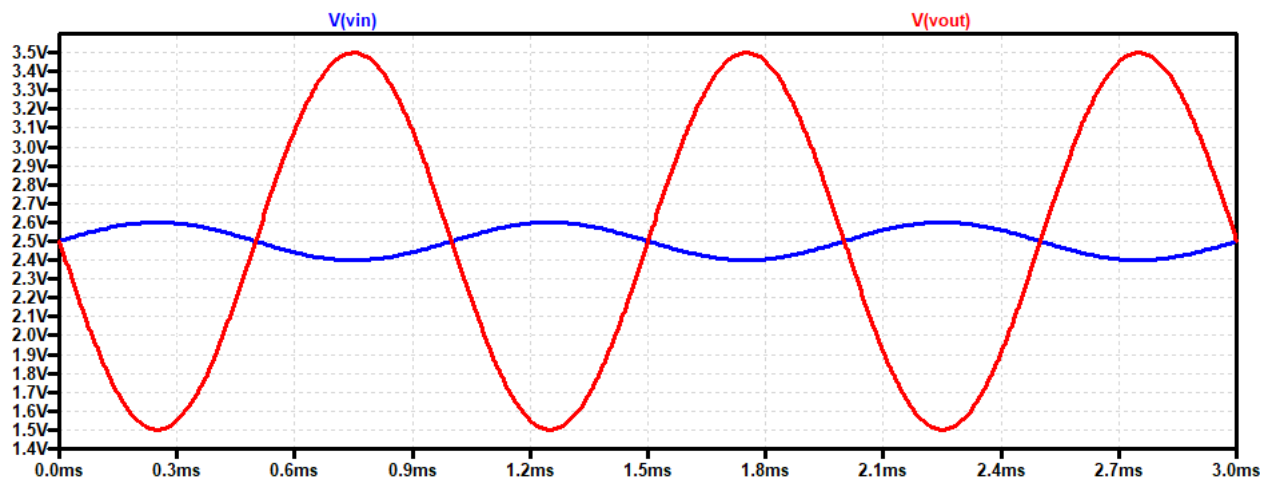
Since R2 is ten times larger than R1 in the circuit above, the gain is -10. With a gain of -10 and an input signal of 100mV oscillating around the common-mode voltage (2.5V), we expect an output signal of 1V oscillating around the common-mode voltage, with a phase shift of 180°.



Transient analysis of inverting op-amp with gain of -10, frequency of 1kHz.

The simulation results shown above confirm that the op-amp is working properly in the non-inverting configuration with a gain of -10 for VDD = 5V.

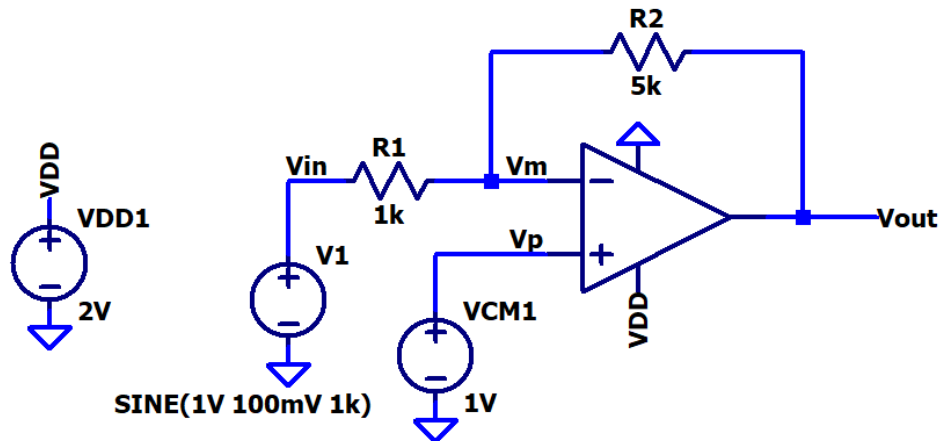
Inverting Op-Amp Topology ($V_{DD} = 2V$)



Schematic used to test operation of op-amp in the inverting topology with a gain of -5, $V_{DD} = 2V$.

Here, we test to make sure that the op-amp can operate down to $V_{DD} = 2V$. To avoid clipping, the gain has been changed in this configuration to better suit $V_{DD} = 2V$.

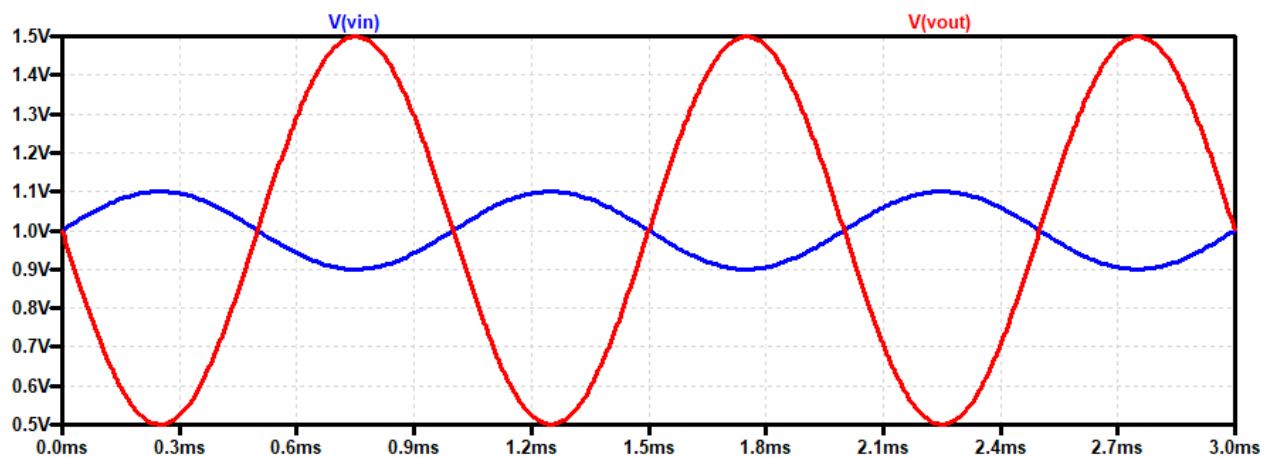Since R_2 is five times larger than R_1 in the circuit above, the gain is -5. With a gain of -5 and an input signal of 100mV oscillating around the common-mode voltage (1V), we expect an output signal of 500mV oscillating around the common-mode voltage, with a phase shift of 180° .



Transient analysis of inverting op-amp with gain of -5, frequency of 1kHz.

The simulation results shown above confirm that the op-amp is working properly in the non-inverting configuration with a gain of -5 for $V_{DD} = 2V$.


Power Dissipation (No Load)

The power dissipated by the op-amp can be estimated by summing the currents in each branch (in the biasing circuit as well as the op-amp) and multiplying the sum by the power supply voltage (VDD).


In the biasing circuit, there are 10 total branches, each with $10\mu\text{A}$ of current flowing. In the op-amp, there are 7 total branches, 6 of which have $10\mu\text{A}$ of current flowing, and 1 which has $500\mu\text{A}$ of current flowing (output stage, W is 50 times larger). This means we can approximate the power dissipated by the op-amp as

$$P = IV = [(16 * 10\mu\text{A}) + * 500\mu\text{A}] * VDD$$

$$P = 660\mu\text{A} * VDD$$

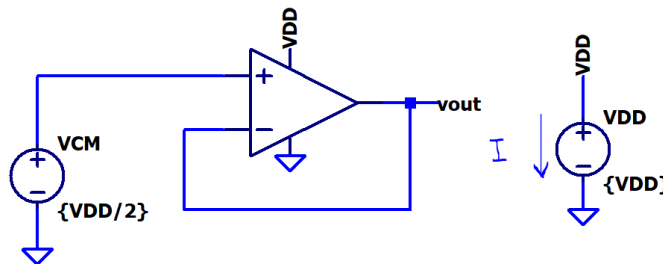

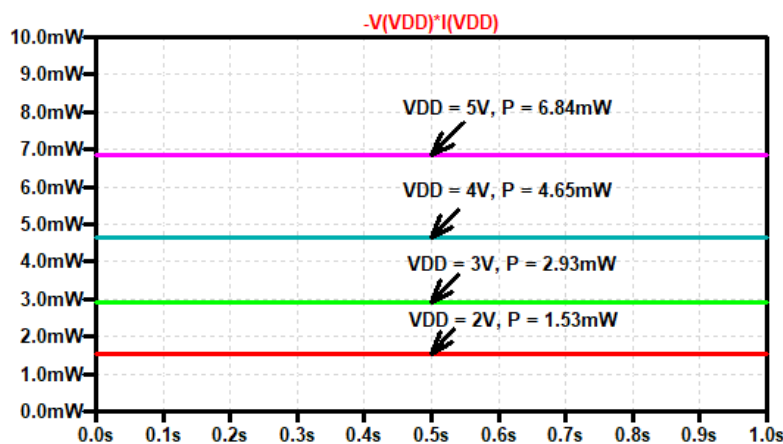Schematic drafted to measure current drawn from power supply at different power supply voltages.




Transient simulation showing power consumed by op-amp at different power supply voltages.

For all values of VDD, the op-amp consumes less than 7mW of power.

Operation as Temperature Changes

Adding a temperature coefficient of $TC_R = 0.002$ to the resistor in the BMR and the zero-nulling resistor in the op-amp, we can observe the operation of the op-amp at temperatures above and below nominal operating temperature.


Frequency Response

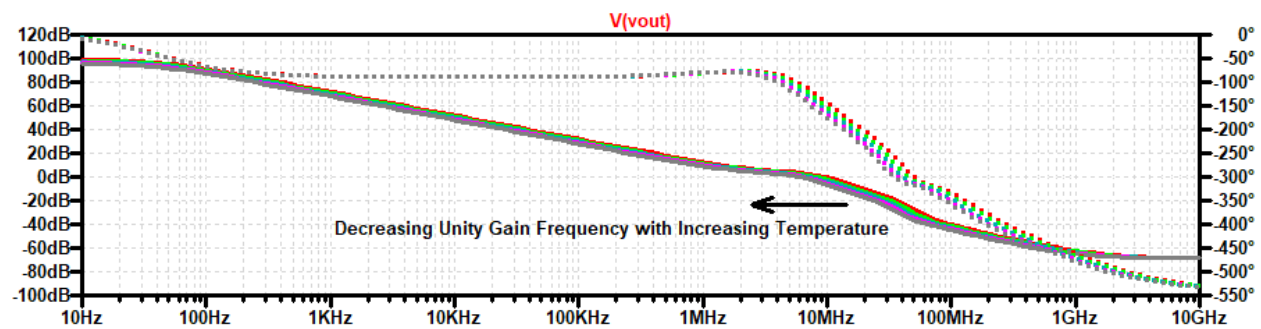

Frequency response for op-amp driving resistive and capacitive load, temperature stepping from 0°C to 200°C. VDD = 5V

Since the temperature coefficient of the resistor is positive, its resistance will increase with increasing temperature. As the resistance of the resistor in the beta multiplier reference increases, the reference current, and as a result also the reference voltages, of the BMR decrease. This will cause a chain reaction, as the bias voltages generated by the biasing circuit will then be inaccurate, matching will be poor, and the op-amp will begin to perform poorly. For example, in the frequency response above, as the temperature increases, the unity gain frequency of the op-amp decreases considerably. Consider also the step response shown below. As temperature rises, the step response slowly becomes unstable, and the output rings with some slight overshoot. Even at temperatures lower than room temperature shown below, the op-amp's step response looks less like a first order response than it does at room temperature or slightly above.

Step Response

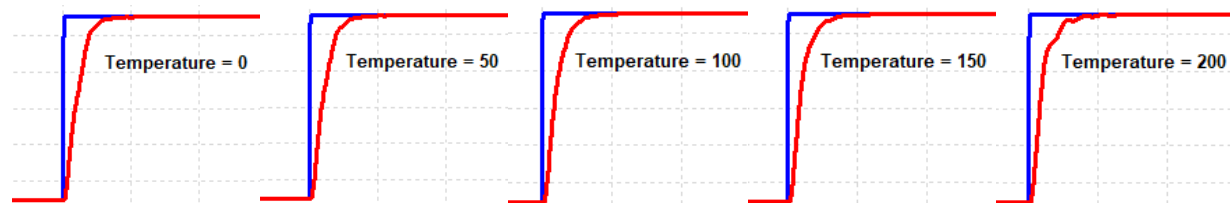

Step response for op-amp driving max load. Ringing becomes obvious at 200°C.

Summary

The op-amp design described in this report meets all of the project specifications. The DC open-loop gain (A_{OLDC}) of the op-amp is 96.1 dB at the lowest power supply voltage ($V_{DD} = 2V$) driving the minimum load (1k resistive) and 106.2 dB at the highest power supply voltage ($V_{DD} = 5V$) driving the maximum load (100pF capacitive). The unity gain frequency, or gain-bandwidth product (GBW), is 3.65 MHz at the lowest power supply voltage driving the minimum load, and 8.45 MHz at the highest power supply voltage driving the maximum load.

The common-mode voltage (input CMR) of the op-amp can range from 850 mV (CMR_{MIN}) up to voltages 650 mV above the power supply voltage (CMR_{MAX}). For operation in the saturation region, the output can swing within 50 mV of the power supply rails (down to 50 mV, up to $V_{DD} - 50$ mV). The op-amp output can go all the way up to V_{DD} and all the way down to ground, but the output stage transistors will be operating in the triode region.

With no load, the op-amp dissipates 6.84 mW of power at the maximum power supply voltage of 5V, and dissipates 1.53 mW at the minimum power supply voltage of 2V. Dividing out the power supply voltage, this translates to 1.37 mA of current drawn at $V_{DD} = 5V$, and 765 μA of current drawn at $V_{DD} = 2V$.

Key design decisions, coupled with considerable tradeoffs, were made regarding input stage MOSFET widths, output stage MOSFET widths, compensation capacitor size, and bias current.

- **Input Stage MOSFET Widths:** Using a large multiplier ($m=50$) on the input terminals of the op-amp allows for a better common-mode rejection ratio. However, it greatly increases the layout size of the differential amplifier. It was decided that the CMRR improvement was more important in this case than minimizing layout size.
- **Output Stage MOSFET Widths:** Using a large multiplier ($m=50$) on the transistors that make up the output buffer allows for better slew rate, faster rise time and fall time of output signals, and more capability for driving larger loads. However, much like the input stage, these wider W devices take up much more layout space, and also source/sink much more current, which causes the op-amp to consume much more power. The op-amp power consumption could be greatly reduced by using a smaller multiplier in the output stage, but this would cause the slew rate to decrease, and the step response to overshoot.
- **Compensation Capacitor Size:** Using a 13pF compensation capacitor allowed for the maximum power supply rejection ratio, and the cleanest step response. However, a 13pF capacitor is large for an on-chip capacitor, and would take up a significant amount of layout space. The PSRR could also be improved by increasing the width of the output stage MOSFETs, but as was discussed previously, increasing these widths greatly increases the power consumption of the op-amp. For this design, it was decided that the larger compensation capacitor was a worthwhile tradeoff to reduce power consumption and maintain a clean step response.

- **Bias Current:** The bias current in this design was selected to be $10\mu\text{A}$. Lower current translates to higher gain, and using $10\mu\text{A}$ makes calculations much simpler. However, using a drain current as low as $10\mu\text{A}$ requires the output stage to be larger in order to achieve a reasonably fast slew rate, and ultimately results in more power consumption as a result. It was decided that using a large enough output stage to meet the slew rate requirement would be necessary regardless of drain current, since the drain current is much smaller than the current that is sourced/sunk in the output buffer.

Future Work and Improvement

Although the op-amp meets the specifications for this project, there are certainly areas where the design can be improved. The key areas where the op-amp can be improved are input CMR, gain bandwidth product (unity gain frequency), phase margin for capacitive loads, power consumption, slew rate, and operation with changing temperature.

- **Input CMR and Gain Bandwidth Product:** In this design, the input stage of the op-amp consists of an NMOS differential amplifier, with a CMR that can extend up to 650 mV above VDD and down to 850 mV. However, this CMR can be greatly improved by adding a PMOS differential amplifier stage to the input. This stage would require more hardware (two more PMOS devices to source current, two more PMOS devices as part of the differential pair, and two more NMOS devices to sink current), and would increase the power consumption of the circuit slightly, along with increasing the layout size. However, by adding the PMOS diff-amp, the common-mode range would extend above VDD still, and also below ground. When the input common-mode voltage is high and moves toward VDD, this would shut off the PMOS diff-amp input transistors, but the NMOS diff-amp inputs would still be on. When the input common-mode voltage is low and moves toward ground, this would shut off the NMOS diff-amp input transistors, but the PMOS diff-amp inputs would still be on. Further, when both the NMOS and PMOS diff-amps are on, the input stage transconductance would be the sum of the transconductances of each, and would move the unity gain frequency out. The addition of the PMOS diff-amp to the input stage would certainly improve the performance of the op-amp.
- **Phase Margin for Capacitive Loads:** The op-amp's phase margin for resistive loads and for no loads is close to optimal (90°). However, for capacitive loads, the phase margin is much lower, and far from optimal. If this chip were to be fabricated, it is likely that the op-amp would not be stable for capacitive loads, and certainly would not be able to drive the capacitance of the oscilloscope for testing. In simulation, all is well with the step response, but many conditions in simulation, even of a realistic design in a small process,

are ideal. For quality performance, the design would need to be improved to have a higher phase margin for capacitive loads.

- **Power Consumption:** The power consumed by the op-amp in this design can be improved only slightly by using a smaller bias current. The power consumption can greatly be improved by making the output stage smaller, but this will lead to other issues, such as slew rate becoming slower, and step response ringing.
- **Slew Rate:** The design meets the specification for slew rate, but only by a couple hundred millivolts for $V_{DD} = 2V$. If minimizing power consumption is not essential, the output stage could be designed to source and sink much larger amounts of current, which would make it capable of driving large loads. The slew rate, as a result, would improve substantially. In this design, the output stage was designed for optimal slew rate along with optimal power consumption in mind. Future designs that do not require low power constraints to be met could drive large loads with no problem at the cost of power, and larger layout size.
- **Operation with Changes in Temperature:** From the simulation results, we can see that at high temperatures, the op-amp performance is less desirable. In future designs, a bandgap voltage reference could be used to bias the op-amp MOSFETs to improve performance at temperatures higher and lower than room temperature. The bandgap voltage reference is capable of outputting voltages that change very little with large changes in temperature and large changes in power supply voltage. Using a bandgap reference for biasing would eliminate the ringing in the step response at high temperatures, and would also improve the unity gain frequency at high temperatures.