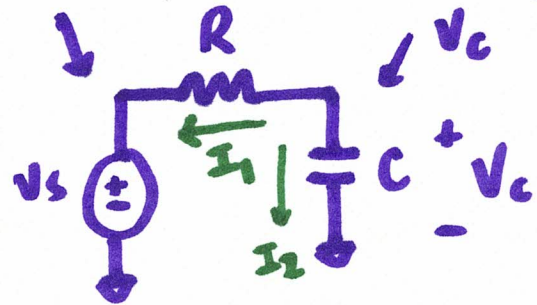


"FIFE" EQUATION DERIVATION

$$V_s = V_{cf}$$



$$\begin{aligned} -I_1 &= I_2 \\ +I_1 &= I_2 + I_2 \\ \underline{0} &= I_2 + I_1 \end{aligned}$$

$$\left. \begin{aligned} I_1 &= \frac{V_c - V_s}{R} \\ I_2 &= C \cdot \frac{dV_c}{dt} \end{aligned} \right\} \frac{V_c - V_s}{R} + \underbrace{C \frac{dV_c}{dt}}_{I_2} = 0$$

$$\left(\frac{-1}{C}\right) \frac{V_c - V_s}{R} = -C \frac{dV_c}{dt} \left(\frac{-1}{C}\right)$$

$$-1 \left(\frac{V_c - V_s}{RC}\right) = \frac{dV_c}{dt}$$

$$-\frac{1}{RC} = \frac{dV_c}{dt} \cdot \left(\frac{1}{V_c - V_s}\right)$$

$$\int_0^t -\frac{1}{RC} \cdot dt = \int_{V_{ci}}^{V_c} \left(\frac{1}{V_c - V_s}\right) dV_c$$

$$-\frac{1}{RC} \cdot (t - 0) = -\frac{t}{RC} = \ln|V_c - V_s| \Big|_{V_{ci}}^{V_c}$$

$$-\frac{t}{RC} = \ln|V_c - V_s| - \ln|V_{ci} - V_s|$$

$$e^{-\frac{t}{RC}} = e^{\ln \left| \frac{V_c - V_s}{V_{ci} - V_s} \right|}$$

$$e^{-t/RC} = \frac{V_c - V_s}{V_{ci} - V_s}$$

$$V_s + (V_{ci} - V_s) e^{-t/RC} = V_c \quad \tau = R \cdot C$$

$$\boxed{V_c(t) = V_{cf} + (V_{ci} - V_{cf}) e^{-t/\tau}}$$