

**Final Exam – Wednesday, May 11**  
**EE220 – Circuits I**  
**Spring 2022**


**Name:** \_\_\_\_\_

To get full credit:


- Show your work.
- Put a box around each of your answers.
- Make sure to **follow all instructions**.
- **Good Luck!**

<b>Problem</b>	<b>Points Earned</b>	<b>Points Possible</b>
<b>1</b>		<b>10</b>
<b>2</b>		<b>5</b>
<b>3</b>		<b>10</b>
<b>4</b>		<b>15</b>
<b>5</b>		<b>15</b>
<b>6</b>		<b>10</b>
<b>7</b>		<b>10</b>
<b>8</b>		<b>10</b>
<b>9</b>		<b>5</b>
<b>10</b>		<b>10</b>
<b>Total:</b>		<b>100</b>

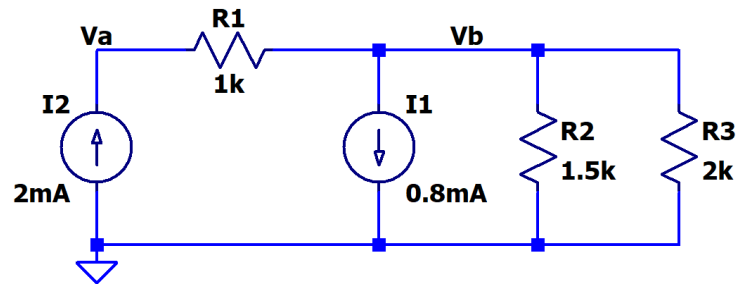
1. Determine the voltages (**V<sub>a</sub>**, **V<sub>b</sub>**) labeled in the circuit below, as well as the currents flowing through R1, R2, and R3. (10 points)



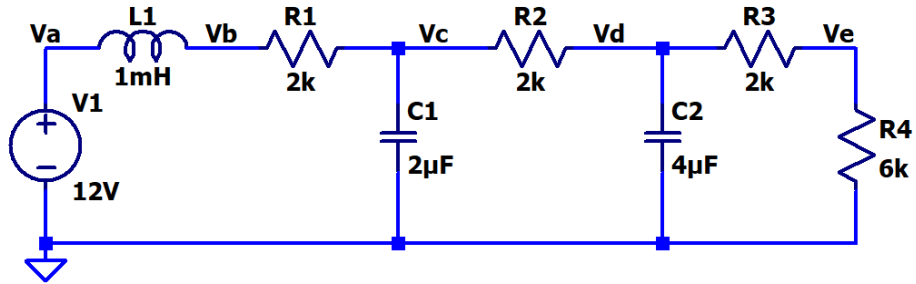
2. Determine the voltages ( $V_a$ ,  $V_b$ ,  $V_c$ ,  $V_d$ ,  $V_e$ ) labeled in the circuit below, as well as the currents flowing through  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ . Note that  $V_1$  is a DC voltage source. Assume the circuit has been sitting here in steady state for a long time. Assume also that the capacitors and the inductor are ideal. (5 points)



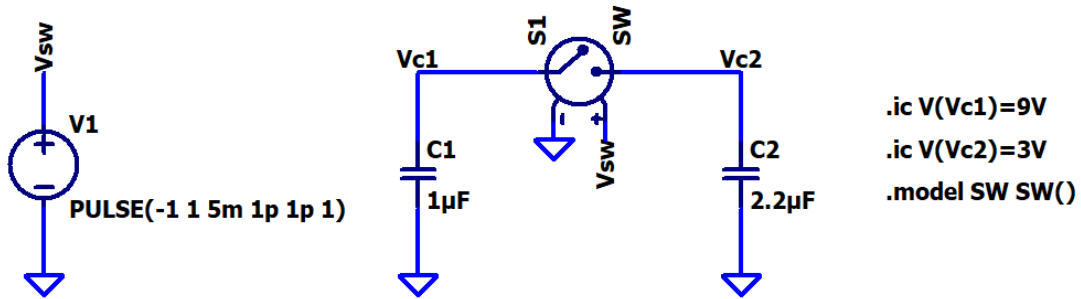
3. The capacitors shown in the circuit below are initially charged to the voltages specified by the given initial conditions. The switch is initially open. How much charge is initially stored on C1? How much charge is initially stored on C2? At time  $t=5\text{ms}$ , the switch in the circuit closes, and charge sharing occurs. What are the values of the labeled voltages (**Vc1** and **Vc2**) some time after the switch closes? Assume that both the switch and the capacitors are ideal. (10 points)




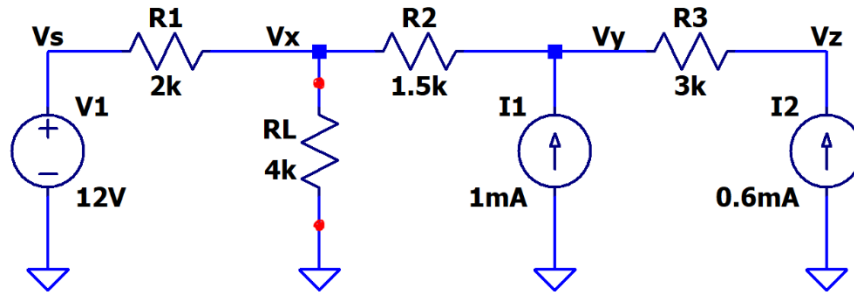
4. Determine  $V_x$  labeled in the circuit below using any method you choose. Then, find the Thevenin and Norton equivalent circuits **when the load resistor ( $R_L$ ) is removed**. Verify that your equivalent circuits are correct by connecting the load resistor across the terminals of your equivalent circuits and comparing the output voltage to your original calculation of  $V_x$ . (15 points)



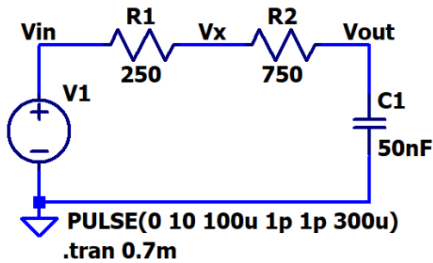
5. Given the RC circuit and the input waveform  $V_{in}(t)$  (plotted below in blue), sketch the waveforms for  $V_x(t)$  and  $V_{out}(t)$ , one on each of the given plots. **Be sure to specify which waveform you are plotting, and on which plot you are plotting it, below. If it is not clear to me which one you are attempting to plot, you will lose points.** Fill in the table with voltage values for  $V_x(t)$  and  $V_{out}(t)$  at the specified times. (15 points)




<i>Time (t)</i>	<i><math>V_x(t)</math></i>	<i><math>V_{out}(t)</math></i>
25 $\mu$ s		
125 $\mu$ s		
210 $\mu$ s		
420 $\mu$ s		
490 $\mu$ s		

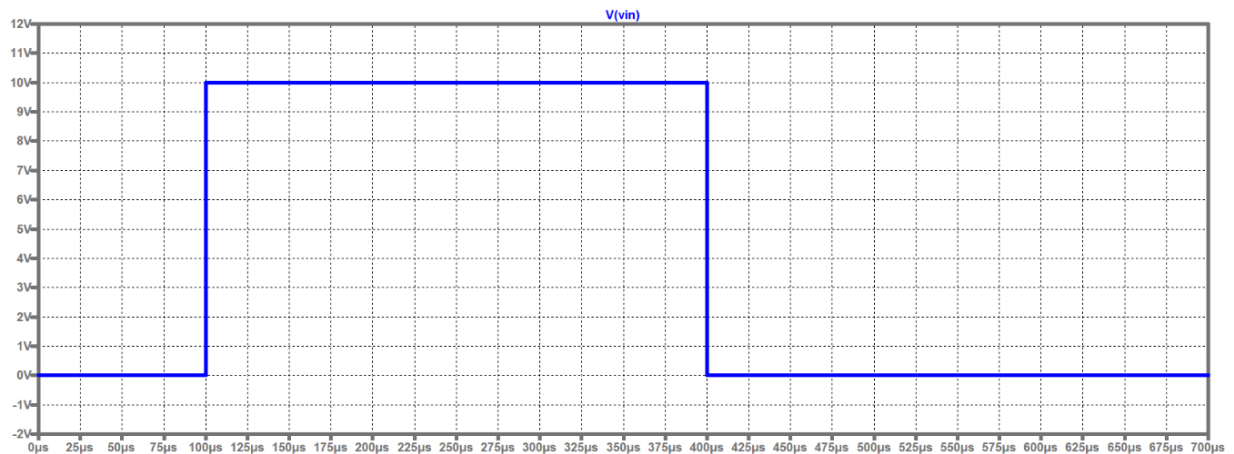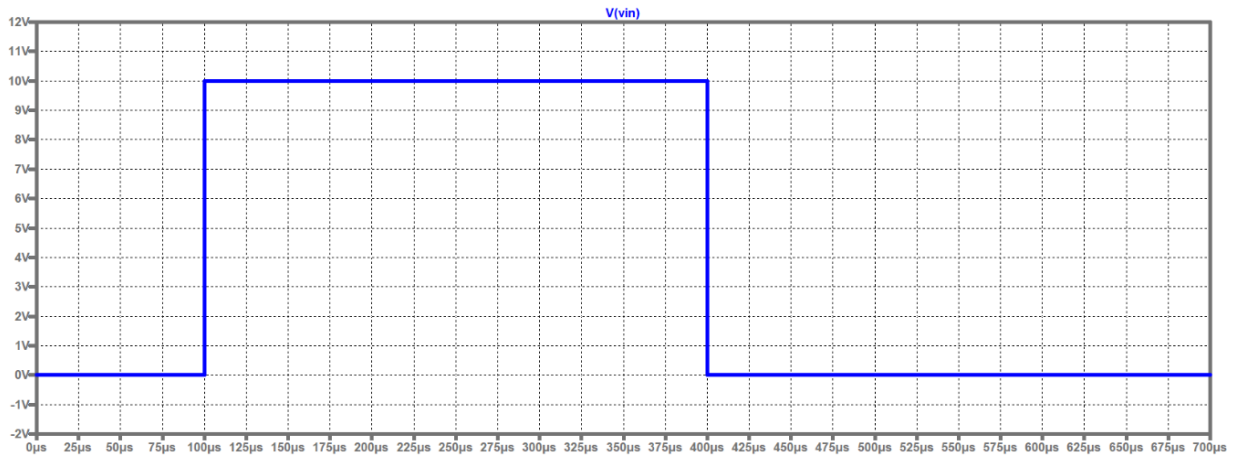

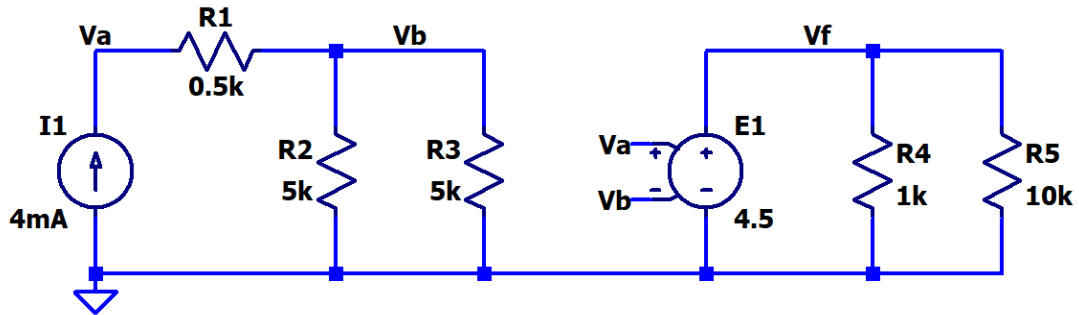6. Determine each of the voltages labeled in the circuit below ( $V_a$ ,  $V_b$ ,  $V_f$ ). Do R3 and R5 dissipate the same amount of power? Show your power calculations to support your answer. (10 points)




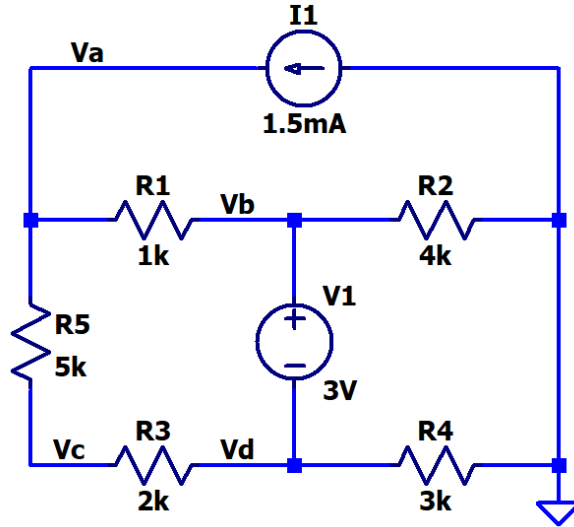7. Determine each of the voltages labeled in the circuit below ( $V_a$ ,  $V_b$ ,  $V_c$ ,  $V_d$ ) using mesh analysis. Do  $R_2$  and  $R_3$  dissipate the same amount of power? Show your power calculations to support your answer. (10 points)






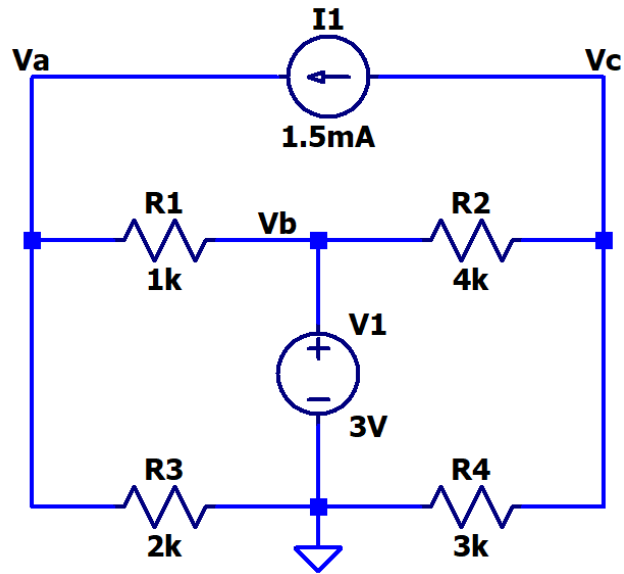8. Determine the voltages  $V_a$ ,  $V_b$ , and  $V_c$  labeled in the circuit below using superposition. (10 points)



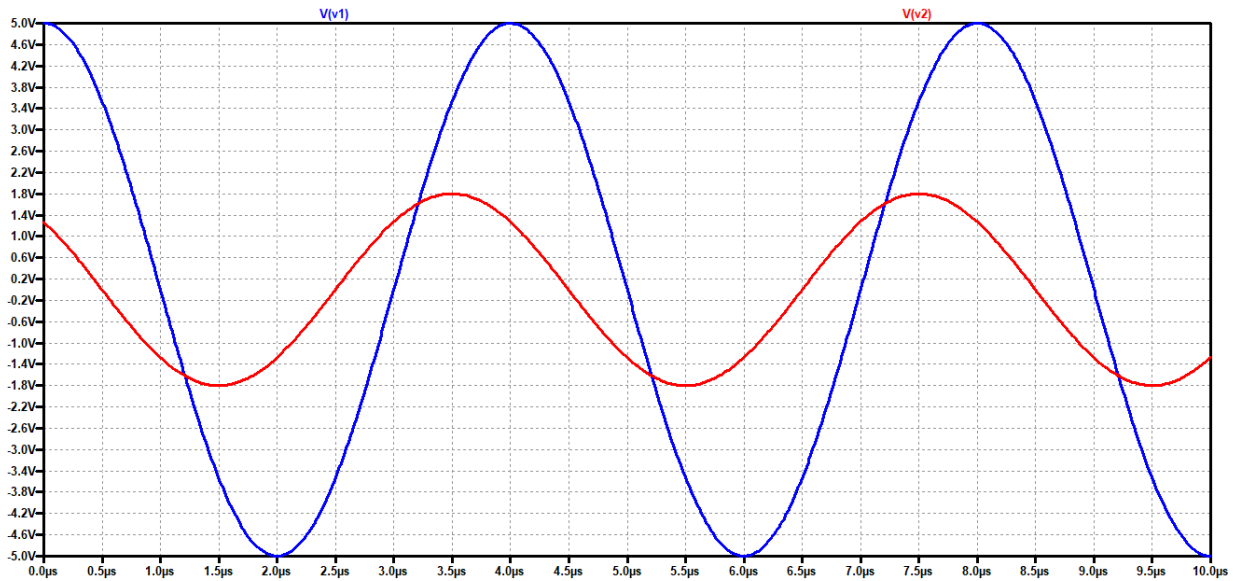9. Two sinusoidal waveforms are plotted below. Both waveforms have the same frequency, but their amplitudes are different, and they are not in phase. **Determine the equations for  $V_1$  and  $V_2$  as a function of time,  $t$ .** Write your equations in terms of a cosine function, where  $V_1$  has a phase of  $0^\circ$ . Which signal is leading? Which is lagging? **Be sure to include the actual values for amplitude (V), frequency (Hz) and phase shift (degrees) in your equations.** If you leave these as variables, you will not get the points. (5 points)



10. Determine the phasor representation of  $V_{in}$ ,  $V_{out}$ , and  $I$  in the circuit given below. Note that  $V_{in}$  is a cosine wave with a phase shift of  $0^\circ$  (synonymous with a sine wave with a phase shift of  $90^\circ$ ). You do not need to draw or sketch any of the waveforms. I only want the phasor form of the input voltage, output voltage, and current. (10 points)

