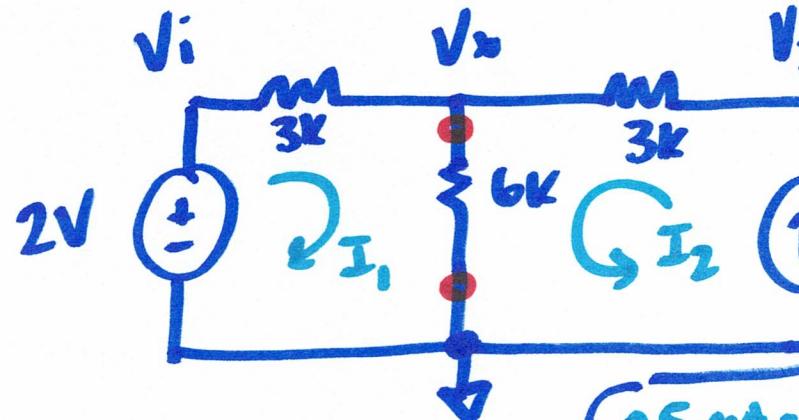


# EE 220: Circuits I [Exam Review 1]

- Thevenin & Norton examples ✓
- mesh analysis / superposition ✓
- AC steady state analysis (phasor problems)
- Dependent sources ✓
- charge sharing ✓
- caps (DC open) & inductors (DC short) ✓
- AC signals (sinusoids)
- power dissipation ✓

QB



$$I_1: 2V - I_1 \cdot 3k - (I_1 + 0.5\text{mA}) \cdot 6k = 0$$

$$I_2 = 0.5\text{mA}$$

$$2V - I_1 \cdot 9k - 3V = 0$$

$$-IV = +I_1 \cdot 9k$$

$$I_1 = \frac{IV}{9k} = 0.111\text{mA}$$

$$0.5\text{mA} - 0.111\text{mA} = 0.389\text{mA}$$


$$V_x = (I_1 + I_2) \cdot 6k = 0.389\text{mA} \cdot 6k$$

~~$\therefore V_x = 3\text{V}$~~

~~$\therefore V_x = 3\text{V}$~~

✓ wrong!!  
use spec!!


$$V_x = 2.33\text{V}$$

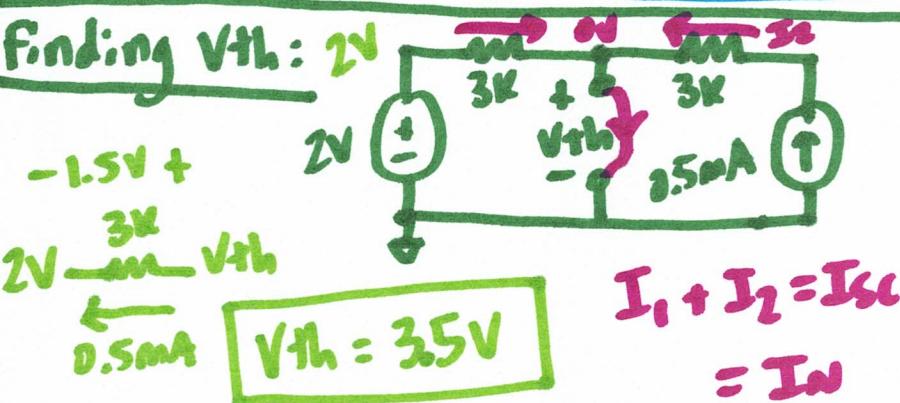

$$I_1 + I_2 = I_{SC}$$

$$= I_N$$

Finding R<sub>th</sub>:

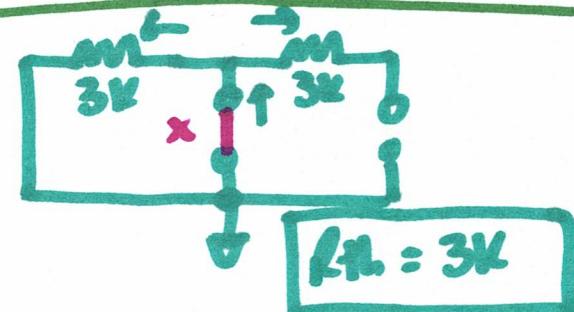


Finding I<sub>N</sub>:

$$I_N = \frac{V_{th}}{R_{th}} = \frac{3.5V}{3k} = 1.166\text{mA} = I_N$$

MT-P3

$$V_{C1} + V_{C2} = V_C$$

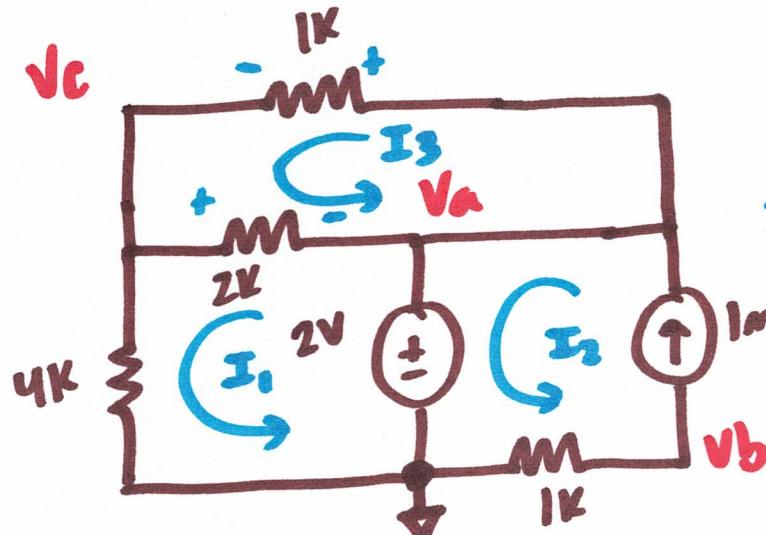

$$I_2 = 1\text{mA}$$

$$I_3: -I_3 \cdot 1\text{k} - (I_3 - I_1) \cdot 2\text{k} = 0$$





$$I_1: 2\text{V} - (I_1 - I_3) \cdot 2\text{k} - I_1 \cdot 4\text{k} = 0$$

⋮


$$I_1 = \text{something} \cdot I_3$$

Superposition
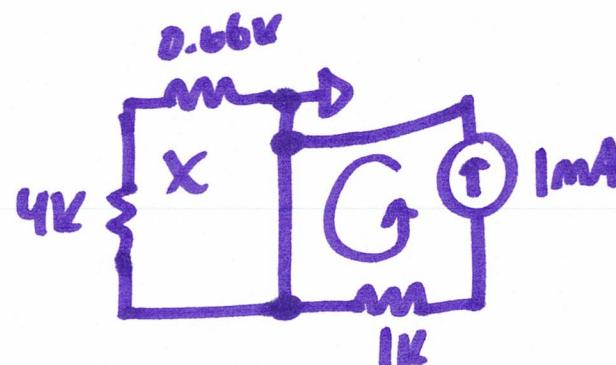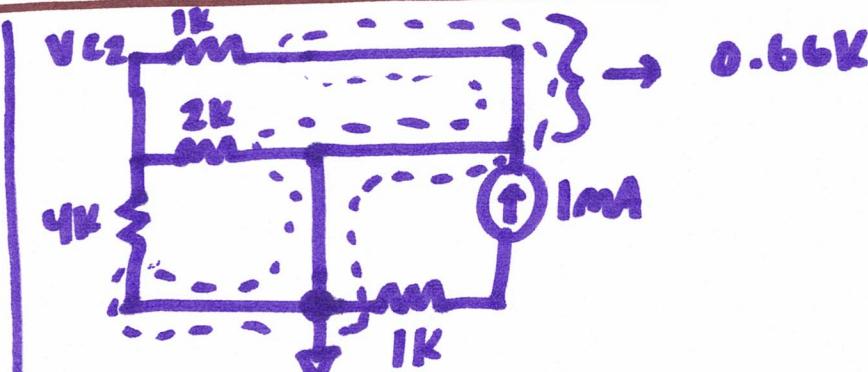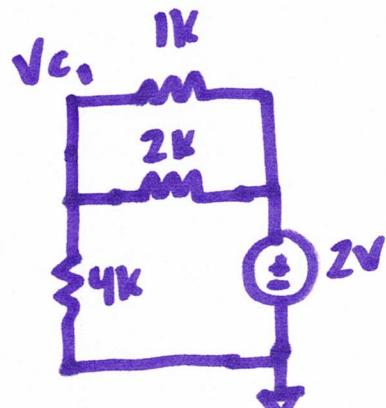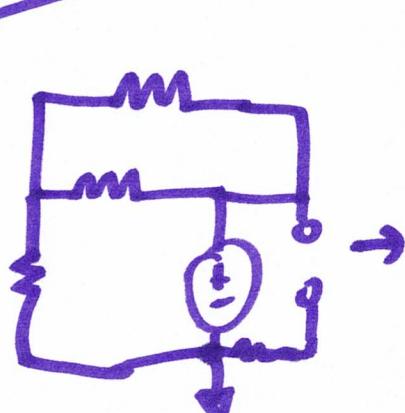
$$2\text{V} \left( \frac{4\text{k}}{0.66\text{k} + 4\text{k}} \right) = V_{C1}$$




## Balmer F17 MT P.2

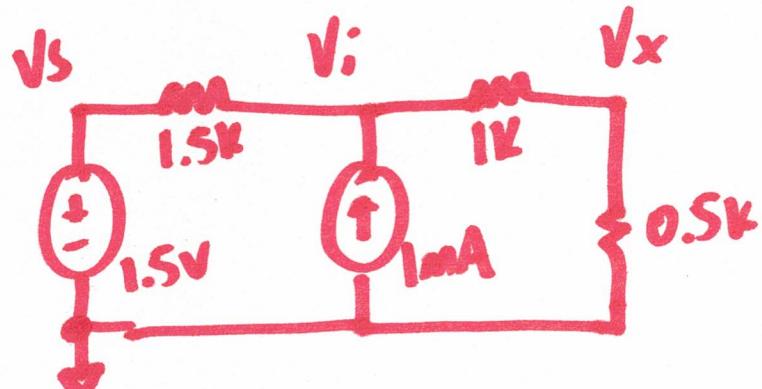


$$V_x = V_{x_1} + V_{x_2}$$
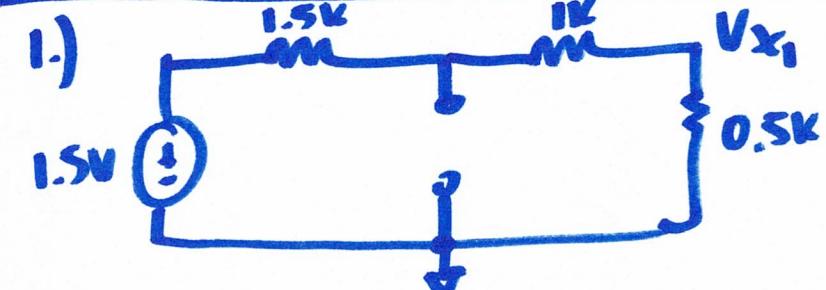
$$V_x = \underline{0.25} + \underline{0.25} = 0.5V$$



$$V_{x_1} = 1.5V \left( \frac{0.5k}{2.5k + 0.5k} \right) = 1.5V \left( \frac{1}{6} \right)$$

$$V_{x_1} = 0.25V$$

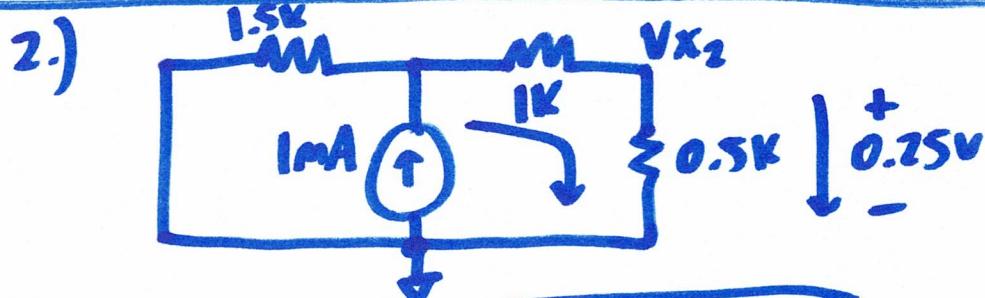

$$V_{x_2} = 0.25V$$

$$V_x = 0.25 + 0.25 = 0.5V$$

## Dependent Sources


CCVS → current controlled voltage source

CCCS → current controlled current source

VCVS → voltage controlled voltage source


VCCS → voltage controlled current source

## Baker F17 MT, P5

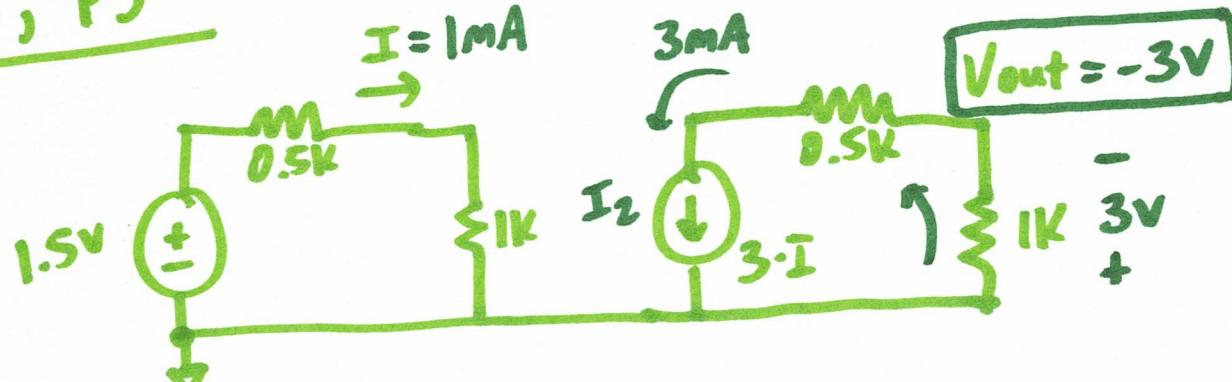


$$I = \frac{1.5V}{1.5K} = 1mA$$

## Baker F16 MT, P5

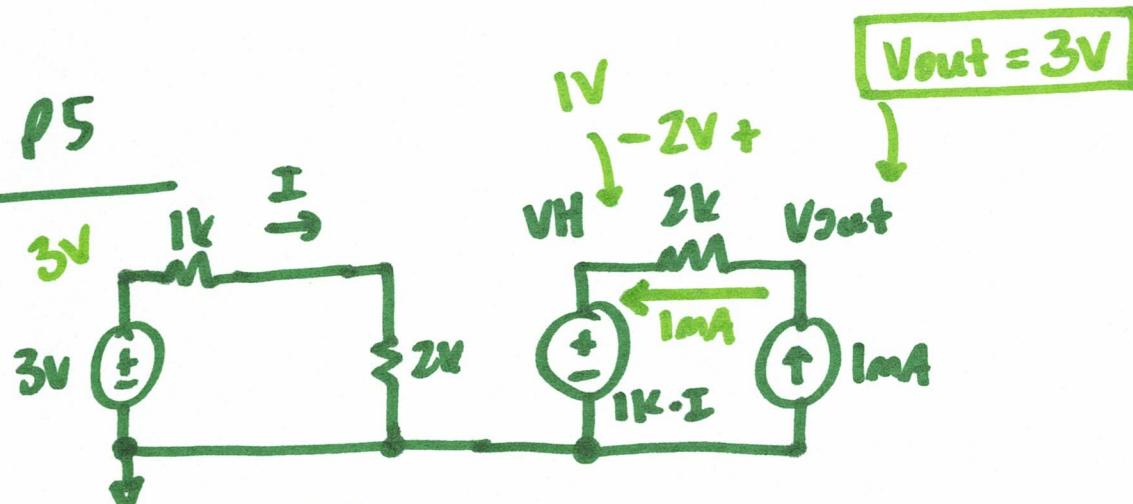

$$I = \frac{3V}{3K} = 1mA$$

## Yellow Charge Sharing

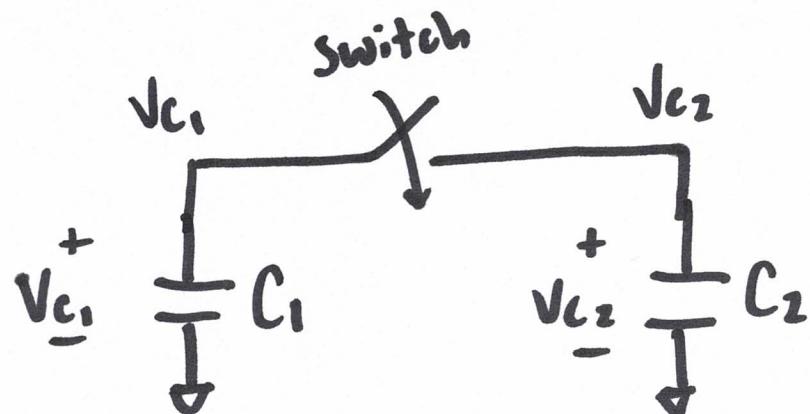

$$Q_i = C_i \cdot V_{C_i}$$

$$C \cdot V = Q$$

$$V = \frac{Q}{C}$$

$$Q_{TOT} = Q_1 + Q_2$$

$$C_{new} = C_1 + C_2$$

$$V_{new} = \frac{Q_{TOT}}{C_1 + C_2}$$

$$Q_2 = C_2 \cdot V_{C_2}$$

$$3V$$

$$2\mu F$$

$$IV$$

$$1\mu F$$

$$Q_{TOT} = 7\mu C$$

$$C_F = 3\mu F$$


$$Q_1 = 3V \cdot 2\mu F = 6\mu C$$

$$Q_2 = IV \cdot 1\mu F = 1\mu C$$


$$C_F \cdot V_F = Q_{TOT} \rightarrow V_F = \frac{Q_{TOT}}{C_F} = \frac{7\mu C}{3\mu F}$$

$$V_F = 2.33V$$


## power dissipation

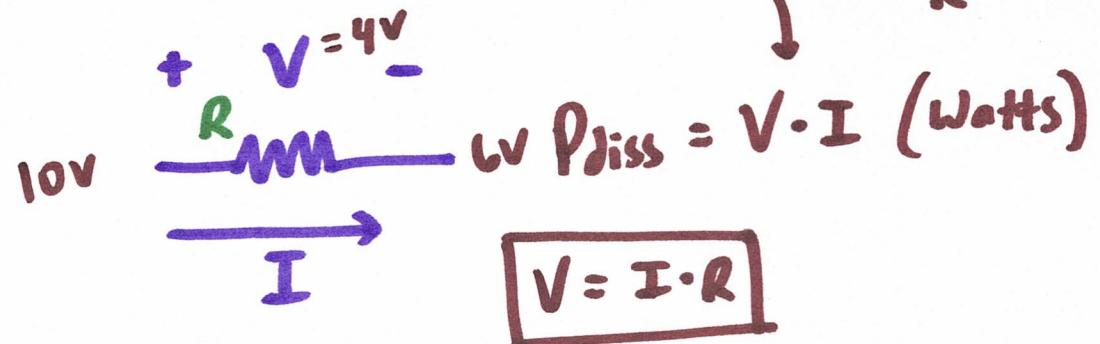

MT P.6

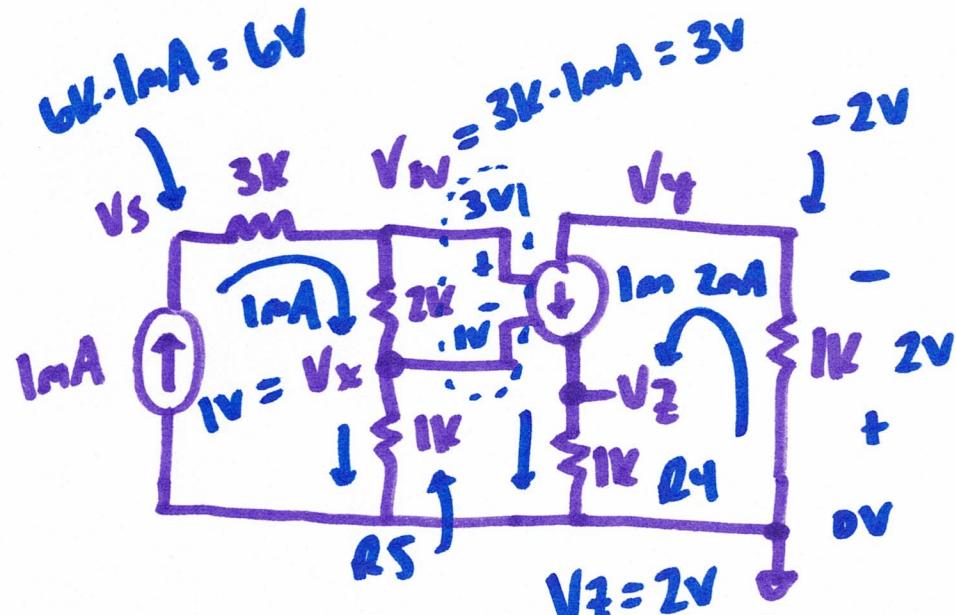

$$P(R_S) = 1V \cdot 1mA = 1mW$$

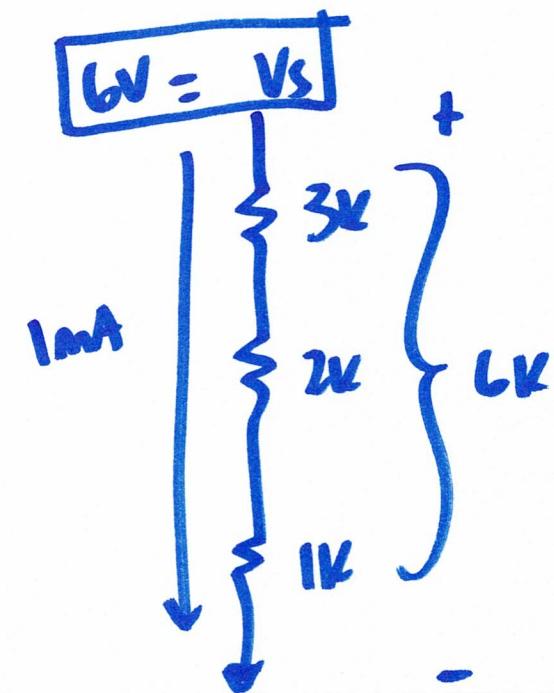

$$V(R_4) = V_z = 2V$$

$$I(R_4) = 2mA$$

$$\left. \begin{aligned} & 2V \cdot 2mA = 4mW \\ & \end{aligned} \right\}$$

# LC oscillations caps & inductors in DC


$$\omega = \frac{1}{\sqrt{LC}}$$

$$\frac{1}{2\pi f L} = C$$




$\text{+H}$  in DC = open



$\text{mm}$  in DC = short

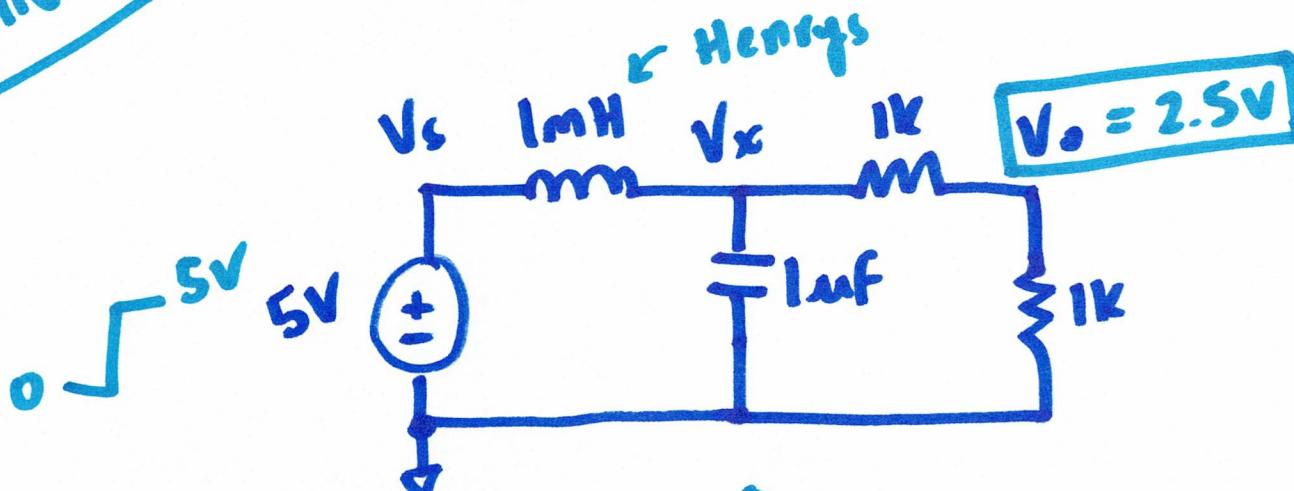


$$V_L = L \cdot \frac{dI}{dt}$$

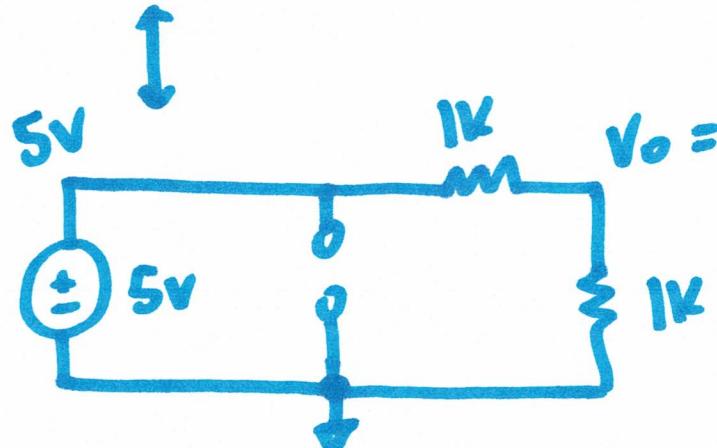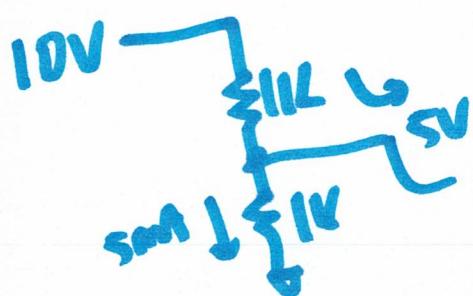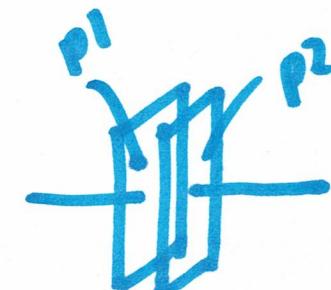

$$I_c = C \cdot \frac{dv}{dt}$$

$$Z = x + jy$$

## AC Steady State

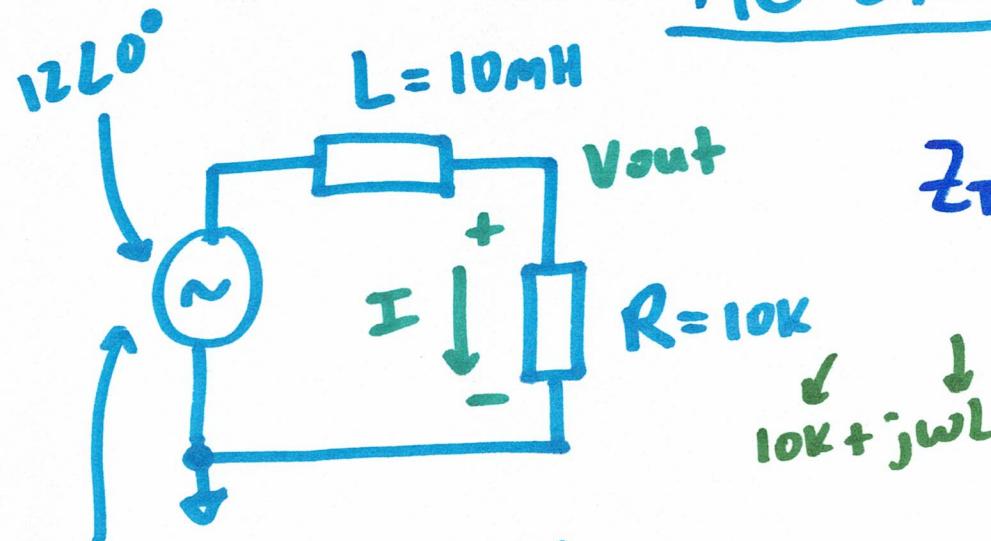

$$Z_T = Z_R + Z_L$$

$$10\text{k} + j\omega L$$

$$j\omega L = 10\text{mH} \cdot 2\pi \cdot 200\text{kHz} \cdot j$$

$$Z_L = 10\text{mH} \cdot 2\pi \cdot 200\text{kHz} \cdot j$$

$$Z_L = j12.57\text{k}$$

$$Z_R = 10\text{k} L 0^\circ$$

$$|Z_R| = \sqrt{x^2 + 0} = x$$

$$\phi = \tan^{-1}\left(\frac{0}{x}\right) = 0^\circ$$

$$|Z_L| = \sqrt{0 + y^2} = y$$

$$\phi = \tan^{-1}\left(\frac{y}{0}\right) = 90^\circ$$

$$Z_R = R L 0^\circ$$

$$Z_L = \omega L L 90^\circ$$

$$Z_C = \frac{1}{\omega C} L - 90^\circ$$

$$I = \frac{12 L 0^\circ}{16.06\text{k} L 51.5^\circ}$$

$$Z_T = 10\text{k} + j12.57\text{k}$$

$$|Z_T| = 16.06\text{k}$$

$$\phi_{Z_T} = \tan^{-1}\left(\frac{12.57\text{k}}{10\text{k}}\right) = 51.5^\circ$$

$$Z_T = 16.06 L 51.5^\circ \text{kA}$$

$$= 0.75\text{m} L - 51.5^\circ \text{A} = I$$

# op-amp

