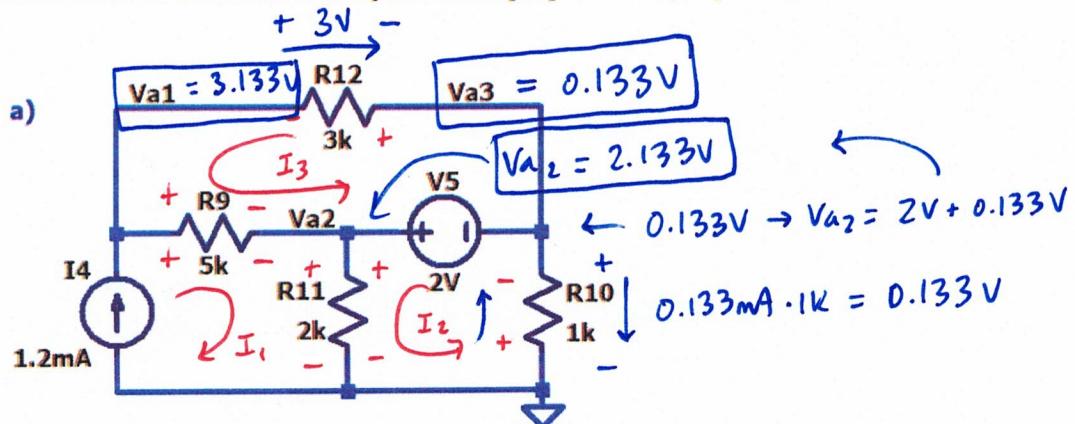


HW8: Problem 2 Solutions

2A. MESH

2. Determine the voltages and currents in the circuits given below using **both mesh analysis and superposition**. Verify your work using LTspice. No need to verify twice, but there should be hand calculations for both mesh analysis and superposition. (10 points)



$$\textcircled{1} \quad I_1 = 1.2 \text{ mA}$$

$$\textcircled{2} \quad +2V - (I_1 + I_2) \cdot 2k - I_2 \cdot 1k = 0$$

$$2V - (1.2 \text{ mA} + I_2) \cdot 2k - I_2 \cdot 1k = 0$$

$$2V - 2.4V - I_2 \cdot 3k = 0$$

$$\frac{-0.4V}{3k} = \frac{I_2 \cdot 3k}{3k} \rightarrow \boxed{I_2 = -0.133 \text{ mA}}$$

$$\textcircled{3} \quad -I_3 \cdot 3k - (I_1 + I_3) \cdot 5k - 2V = 0$$

$$-I_3 \cdot 3k - (1.2 \text{ mA} + I_3) \cdot 5k - 2V = 0$$

$$-I_3 \cdot 3k - 6V - I_3 \cdot 5k - 2V = 0$$

$$\frac{-I_3 \cdot 8k}{-8k} = \frac{8V}{-8k}$$

$$\boxed{I_3 = -1 \text{ mA}}$$


$$V_{a2} = (I_1 + I_2) \cdot 2k$$

$$V_{a2} = (1.2 \text{ mA} + (-0.133 \text{ mA})) \cdot 2k$$

$$\boxed{V_{a2} = 2.133V}$$


2A. SUPERPOSITION
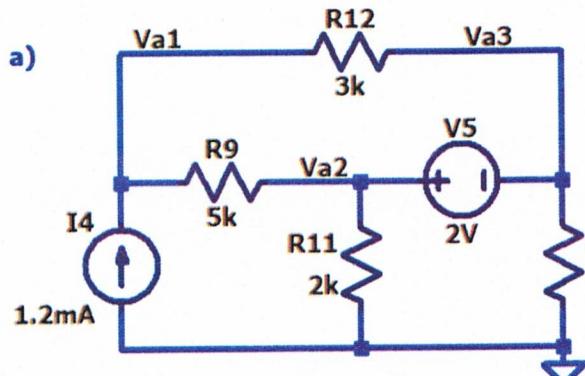
$$\begin{aligned} V_{a1} &= 3.133V \\ V_{a2} &= 2.133V \\ V_{a3} &= 0.133V \end{aligned}$$




$$\begin{aligned} V_{a1} &= V_{a1,1} + V_{a1,2} & \checkmark \\ V_{a1} &= 3.05V + 0.08V = 3.13V & \boxed{} \\ V_{a2} &= V_{a2,1} + V_{a2,2} & \checkmark \\ V_{a2} &= 0.8V + 1.33V = 2.13V & \boxed{} \\ V_{a3} &= V_{a3,1} + V_{a3,2} & \checkmark \\ V_{a3} &= 0.8V + (-0.667V) = 0.133V & \boxed{} \end{aligned}$$

PART 1: No Voltage Source

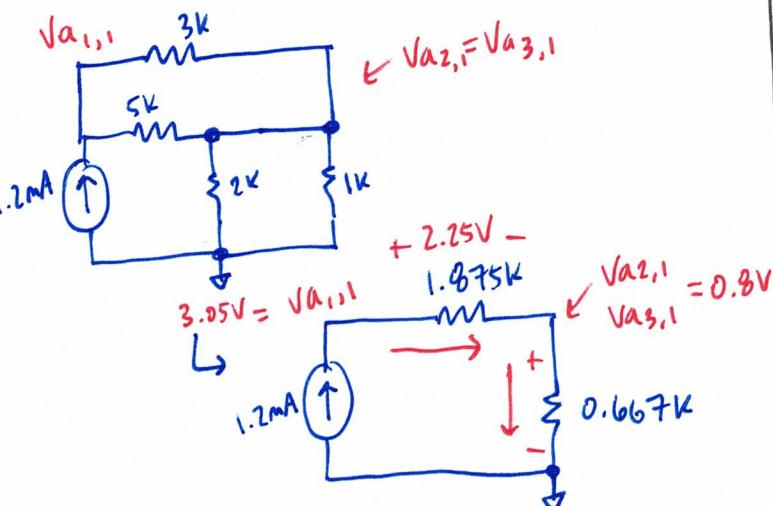

$$\begin{aligned} V_{a1,1} &= 3.05V \\ V_{a2,1} &= 0.8V \\ V_{a3,1} &= 0.8V \end{aligned}$$

PART 2: No Current Source

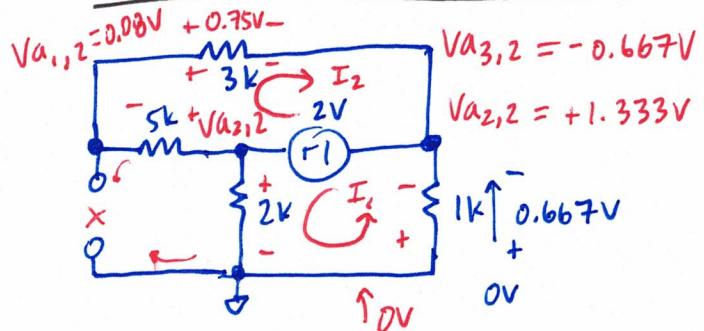

$$① +2V - I_1 \cdot 2k - I_1 \cdot 1k = 0$$

$$\frac{2V}{3k} = \frac{I_1 \cdot 3k}{3k} \rightarrow I_1 = 0.667mA$$


$$② +2V - I_2 \cdot 5k - I_2 \cdot 3k = 0$$

$$\frac{2V}{8k} = \frac{I_2 \cdot 8k}{8k} \rightarrow I_2 = 0.25mA$$

$$\begin{aligned} V_{a1,2} &= 0.08V \\ V_{a2,2} &= 1.33V \\ V_{a3,2} &= -0.667V \end{aligned}$$

ZB. MESH
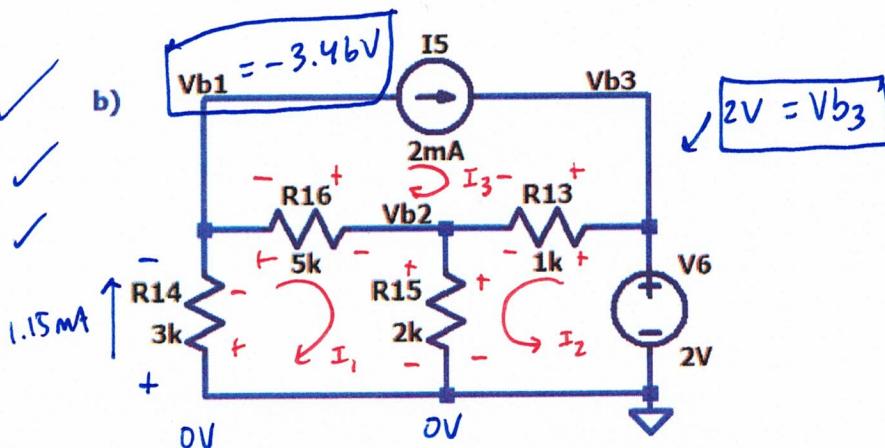
$$\begin{aligned} V_{b_1} &= -3.46 \text{ V} \\ V_{b_2} &= 0.77 \text{ V} \\ V_{b_3} &= 2 \text{ V} \end{aligned}$$



$$① \quad I_3 = 2 \text{ mA}$$

$$\begin{aligned} I_1 &= -1.5(-0.77 \text{ mA}) \\ I_1 &= 1.15 \text{ mA} \end{aligned}$$

$$\begin{aligned} ② \quad +2V - (I_2 + I_3) \cdot 1k - (I_1 + I_2) \cdot 2k &= 0 \\ +2V - (I_2 + 2 \text{ mA}) \cdot 1k - I_1 \cdot 2k - I_2 \cdot 2k &= 0 \\ 2V - I_2 \cdot 1k - 2V - I_1 \cdot 2k - I_2 \cdot 2k &= 0 \\ -I_2 \cdot 1k - I_2 \cdot 2k - I_1 \cdot 2k &= 0 \\ -\frac{I_2 \cdot 3k}{2k} = \frac{I_1 \cdot 2k}{2k} &\rightarrow I_1 = -1.5 \cdot I_2 \quad ② \end{aligned}$$

$$\begin{aligned} ③ \quad -I_1 \cdot 3k - (I_1 - I_3) \cdot 5k - (I_1 + I_2) \cdot 2k &= 0 \\ -I_1 \cdot 3k - (I_1 - 2 \text{ mA}) \cdot 5k - (I_1 + I_2) \cdot 2k &= 0 \\ -I_1 \cdot 3k - I_1 \cdot 5k + 10V - I_1 \cdot 2k - I_2 \cdot 2k &= 0 \\ -I_1 \cdot 10k - I_2 \cdot 2k + 10V &= 0 \quad ③ \\ -(-1.5 \cdot I_2 \cdot 10k) - I_2 \cdot 2k + 10V &= 0 \end{aligned}$$

$$\begin{aligned} 15k \cdot I_2 - 2kI_2 + 10V &= 0 \\ \frac{13k \cdot I_2}{13k} = \frac{-10V}{13k} &\rightarrow I_2 = -0.77 \text{ mA} \end{aligned}$$


$$V_{b_2} = (I_1 + I_2) \cdot 2k$$

$$V_{b_2} = (1.15 \text{ mA} - 0.77 \text{ mA}) \cdot 2k$$

$$V_{b_2} = 0.77 \text{ V}$$



2B. SUPERPOSITION
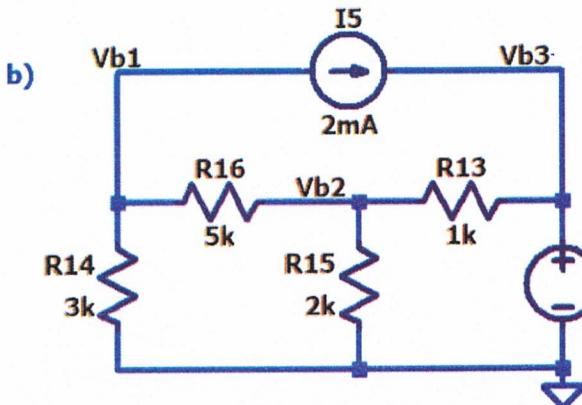
$$\begin{aligned} V_{b_1} &= -3.46V \\ V_{b_2} &= 0.77V \\ V_{b_3} &= 2V \end{aligned}$$



$$\begin{aligned} V_{b_1} &= V_{b_{1,1}} + V_{b_{1,2}} \\ V_{b_1} &= 0.46V + (-3.13)V = -3.47V \\ V_{b_2} &= V_{b_{2,1}} + V_{b_{2,2}} \\ V_{b_2} &= 1.23V + (-0.46V) = 0.77V \\ V_{b_3} &= V_{b_{3,1}} + V_{b_{3,2}} \\ V_{b_3} &= 2V + 0V = 2V \end{aligned}$$

PART 1. NO CURRENT SOURCE

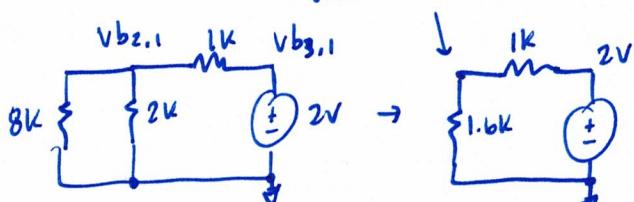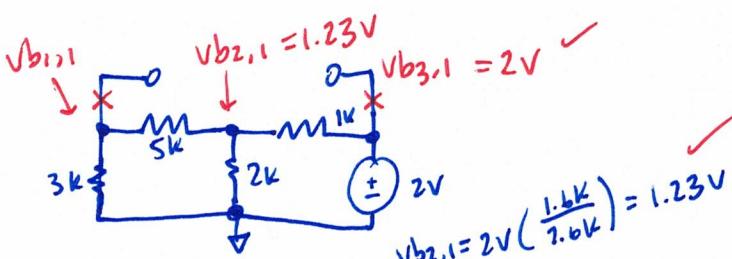



$$V_{b_{1,1}} = 1.23V \left(\frac{3k}{9k} \right) = 0.46V$$

$$V_{b_{1,1}} = 0.46V$$

$$V_{b_{2,1}} = 1.23V$$

$$V_{b_{3,1}} = 2V$$

PART 2. NO VOLTAGE SOURCE

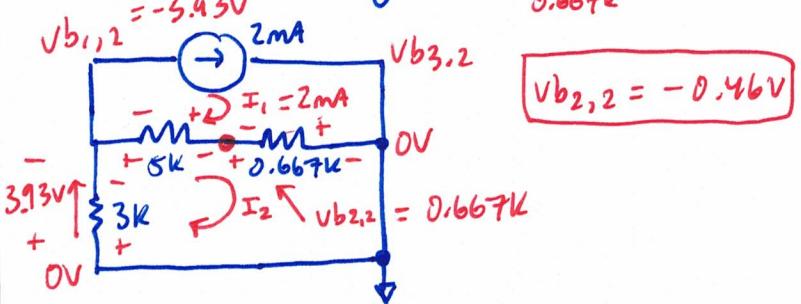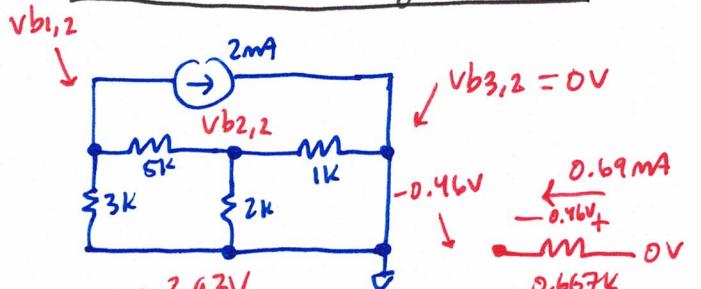

$$\rightarrow -I_2 \cdot 3k - (I_2 - 2mA) \cdot 5k - (I_2 - 2mA) \cdot 0.667k = 0$$

$$-I_2 \cdot 3k - (I_2 - 2mA) \cdot 5.667k = 0$$

$$-I_2 \cdot 3k - I_2 \cdot 5.667k + 11.33V = 0$$

$$-I_2 \cdot \frac{8.667k}{-8.667k} = -11.33V = 1.31mA = I_2$$

~~Vb2,2~~

$$V_{b_{1,2}} = -3.43V$$

$$V_{b_{2,2}} = -0.46V$$

$$V_{b_{3,2}} = 0V$$