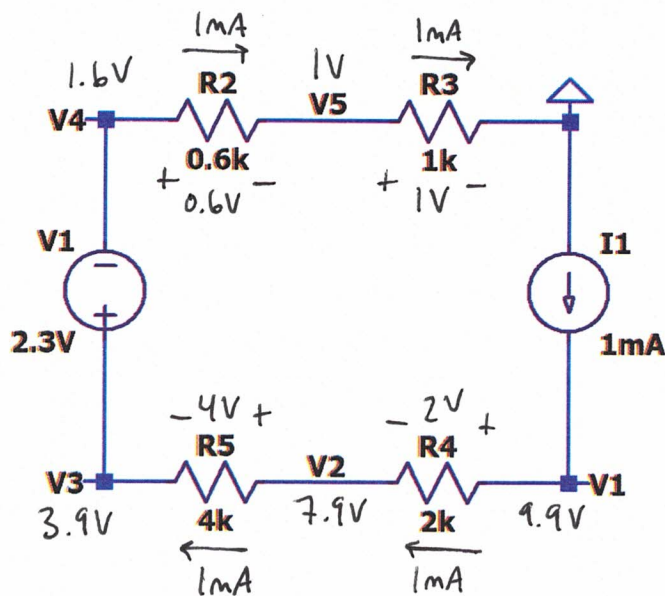


Midterm Exam – Wednesday, March 9  
 EE220 – Circuits I  
 Spring 2022

To get full credit:

- Show your work.
- Put a box around each of your answers.
- Make sure to **follow all instructions**.

1. Determine the voltages ( $V_1, V_2, V_3, V_4, V_5$ ) labeled in the circuit below. (15 points)




(2 mins)


$V_1 = 9.9V$	$V_4 = 1.6V$
$V_2 = 7.9V$	$V_5 = 1V$
$V_3 = 3.9V$	

2. Determine  $V_x$  in the following circuit using superposition. Then, determine the current flowing through  $R_1$ . (15 points)



(7 mins)

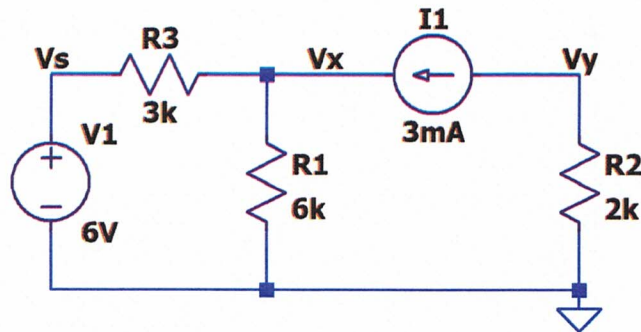

$$V_x = V_{x_1} + V_{x_2}$$

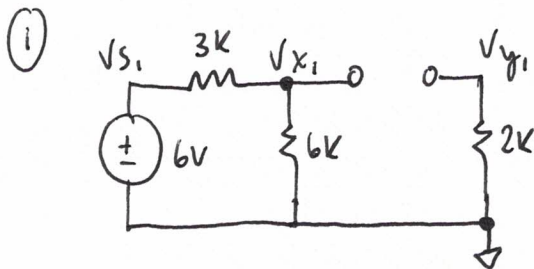
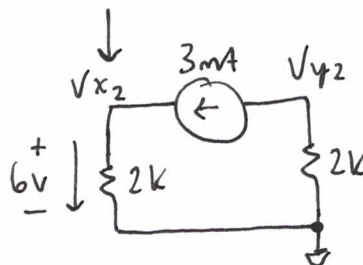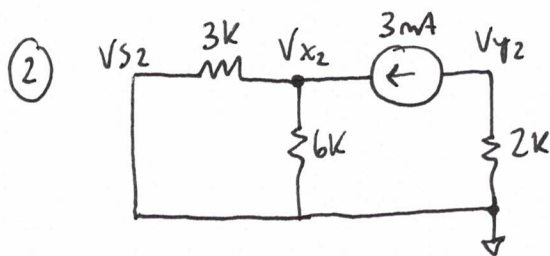
$$V_{x_1} = 6V \cdot \frac{6k}{3k+6k} = 4V$$




$$V_{x_2} = 6V$$

$$\therefore V_x = 4V + 6V = 10V$$

$$\therefore I(R_1) = 10V/6k = 1.667mA$$

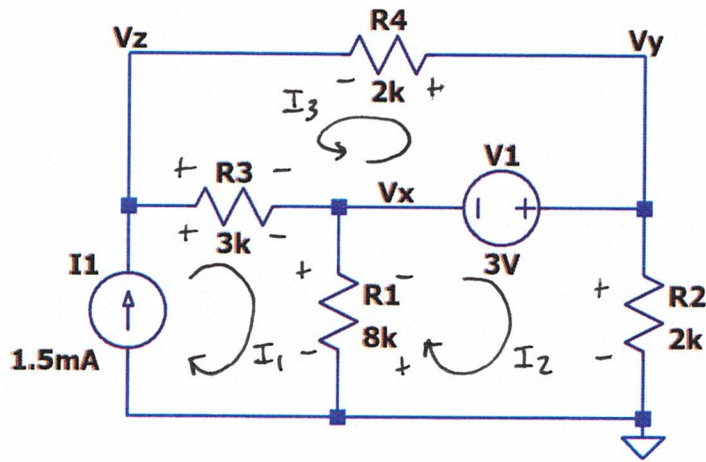3. Determine each of the loop currents in the following circuit **using mesh analysis**. Use the loop currents you find to determine  $V_x$ ,  $V_y$ , and  $V_z$ . (20 points) (9 mins)



$$\textcircled{1} \quad I_1 = 1.5 \text{ mA}$$

$$\textcircled{2} \quad +3\text{V} - I_2 \cdot 2\text{k} - (I_2 - I_1) \cdot 8\text{k} = 0 \rightarrow 3\text{V} - I_2 \cdot 2\text{k} - I_2 \cdot 8\text{k} + (1.5\text{mA} \cdot 8\text{k}) = 0$$

$$\textcircled{3} \quad +3\text{V} - I_3 \cdot 2\text{k} - (I_3 + I_1) \cdot 3\text{k} = 0 \rightarrow 3\text{V} - I_3 \cdot 2\text{k} - I_3 \cdot 3\text{k} - (1.5\text{mA} \cdot 3\text{k}) = 0$$

$$\textcircled{2} \quad 3\text{V} - I_2 \cdot 10\text{k} + 12\text{V} = 0 \rightarrow 15\text{V} = I_2 \cdot 10\text{k}$$

$$\textcircled{3} \quad 3\text{V} - I_3 \cdot 5\text{k} - 4.5\text{V} = 0 \rightarrow -1.5\text{V} = I_3 \cdot 5\text{k}$$

$$\therefore I_2 = 1.5 \text{ mA}$$

$$\therefore I_3 = -0.3 \text{ mA}$$


$$V_x = (I_1 - I_2) \cdot 8\text{k} = 0\text{V}$$

$$V_y = I_2 \cdot 2\text{k} = 3\text{V}$$

$$V_z = V_y - (I_3 \cdot 2\text{k}) = 3.6\text{V}$$

4. Determine  $V_x$  labeled in the circuit below using any method you choose. Then, find the Thevenin and Norton equivalent circuits **when the load resistor ( $R_L$ ) is removed**. Verify that your equivalent circuits are correct by connecting the load resistor across the terminals of your equivalent circuits and comparing the output voltage to your original calculation of  $V_x$ . (20 points)

(9 mins)

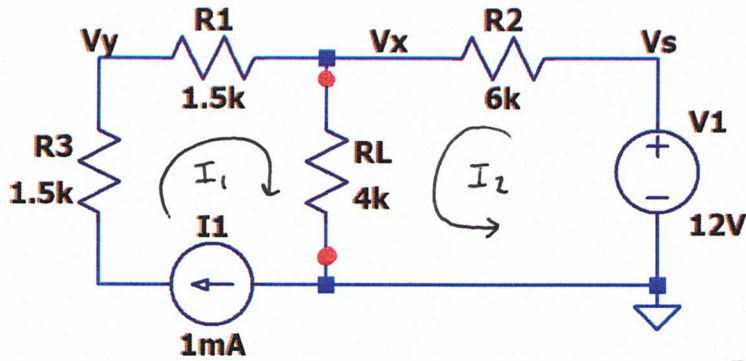


\*  $I_1 = 1\text{mA}$

$\therefore V_x = 1.8\text{mA} \cdot 4\text{k} = 7.2\text{V}$

\*  $12\text{V} - I_2 \cdot 6\text{k} - (I_2 + 1\text{mA}) \cdot 4\text{k} = 0 \rightarrow 12\text{V} - I_2 \cdot 10\text{k} - 4\text{V} = 0$


$I_2 = 0.8\text{mA}$

Thevenin

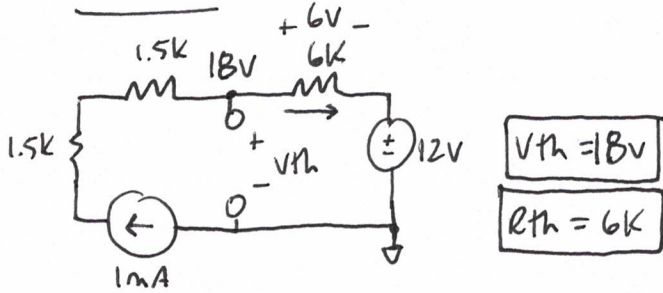


$V_{out, Th} = 18\text{V} \cdot \frac{4\text{k}}{10\text{k}}$

$V_{out, Th} = 7.2\text{V}$

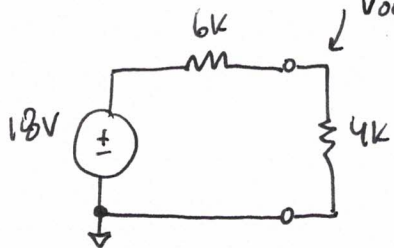

Norton

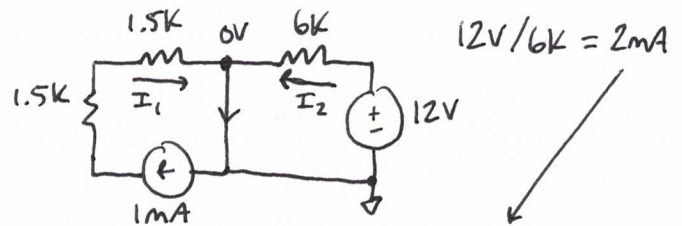


$I_N = I_1 + I_2 = 1\text{mA} + 2\text{mA} = 3\text{mA}$





$R_N = 6\text{k}$

$V_{out, N} = 3\text{mA} \cdot (6\text{k} // 4\text{k})$

$V_{out, N} = 7.2\text{V}$

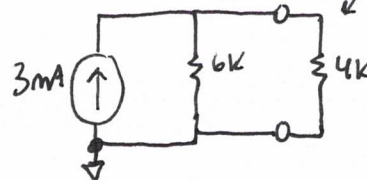

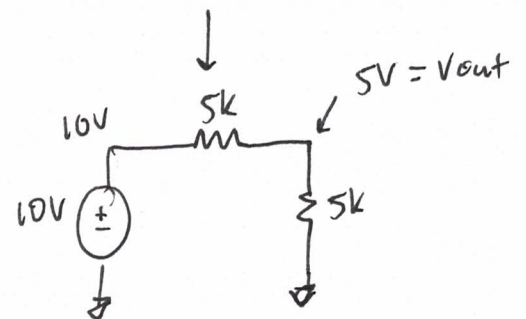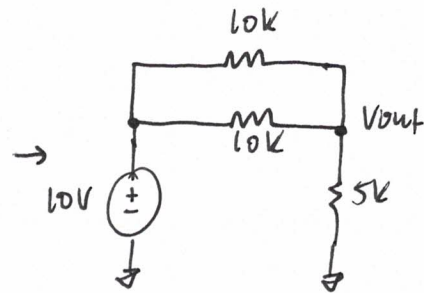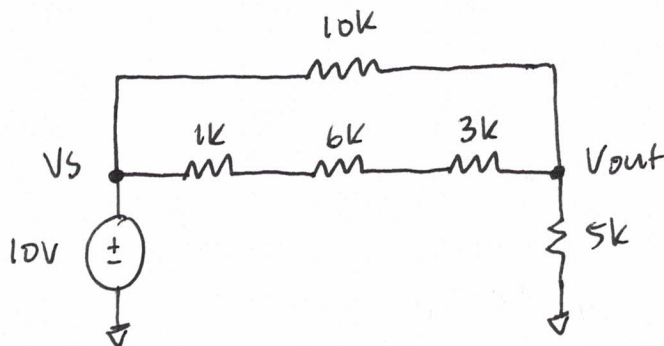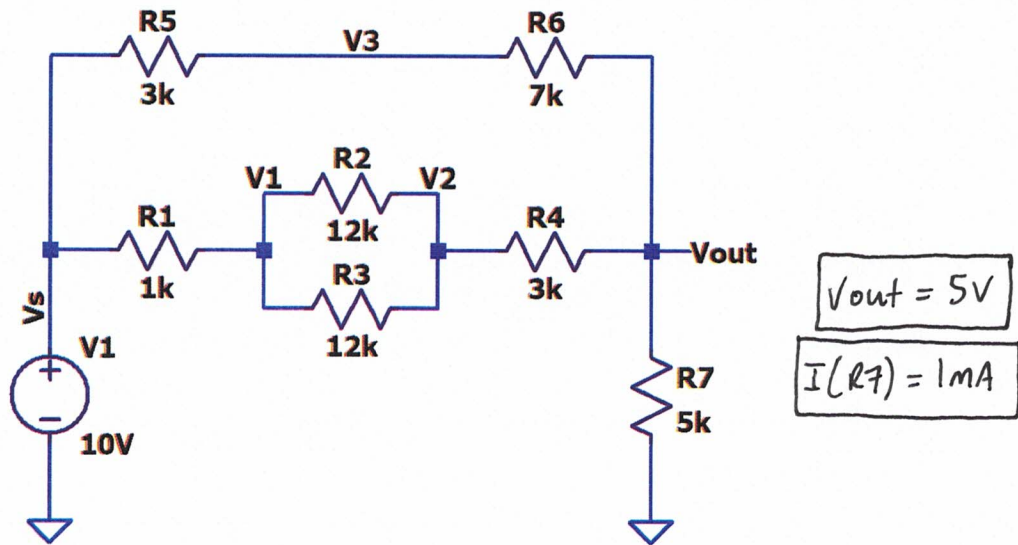
5. Determine  $V_{out}$  in the circuit given below. Also, determine the current that flows through resistor  $R7$ . Note that you can reduce the resistance between  $V_s$  and  $V_{out}$  down to a single equivalent resistor. (15 points) (2 mins)





6. Determine each of the voltages labeled in the circuit below ( $V_s$ ,  $V_w$ ,  $V_x$ ,  $V_y$ ,  $V_z$ ). Do  $R_4$  and  $R_5$  dissipate the same amount of power? Show your power calculations to support your answer. (15 points)

(3 mins)

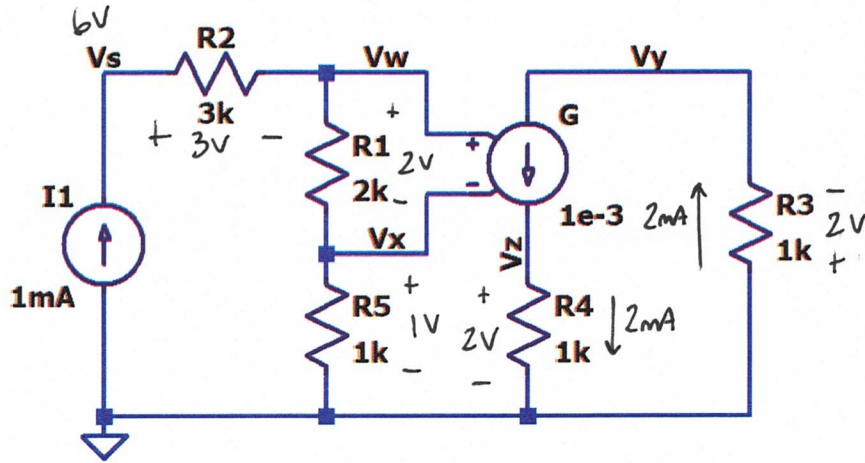

$$V_s = 3V + 2V + 1V = 6V$$

$$V_w = 2V + 1V = 3V$$

$$V_x = 1k \cdot 1mA = 1V$$

$$V_y = 0 - 2V = -2V$$

$$V_z = 2mA \cdot 1k = 2V$$

$$P(R_5) = 1V \cdot 1mA = 1W$$

$$P(R_4) = 2V \cdot 2mA = 4W$$

$\therefore R_4$  dissipates more power than  $R_5$ .